
190100042 - CHIRAG GARG

BOOST CONVERTER

For Board in DCH we have -

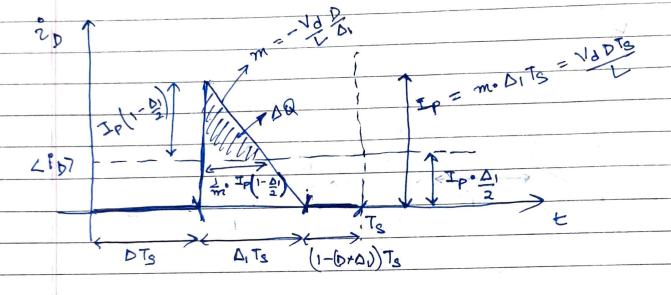


$$\Delta Q = \frac{1}{2} \cdot \left[\frac{I_p \cdot \left(1 - \Delta_1 \right)^2}{2} \right]^2 \cdot \frac{1}{m} = \frac{I_p^2 \left(2 - \Delta_1 \right)^2}{8} \cdot \frac{\Delta_1 L}{V_{aD}}$$

$$\Delta Q = \frac{\Delta_1 L}{V_{dD}} \left(\frac{2-\Delta_1}{8}\right)^2 \cdot \left(\frac{V_{dD}}{L}\right)^2 T_{S}^2 = \frac{V_{dD} T_{S}^2}{8L} \Delta_1 \cdot (2-\Delta_1)^2$$


$$\Rightarrow \Delta V_0 = \Delta Q = \frac{\Delta Q}{C}$$
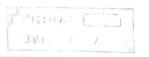
$$\Rightarrow \Delta V_0 = V_0 \cdot D \cdot T_0^2 \cdot \Delta_1 \cdot (2-\Delta_1)^2$$
8LC



BUCK-BOOST CONVERTER

For Buck- Boost in DCM, we have -

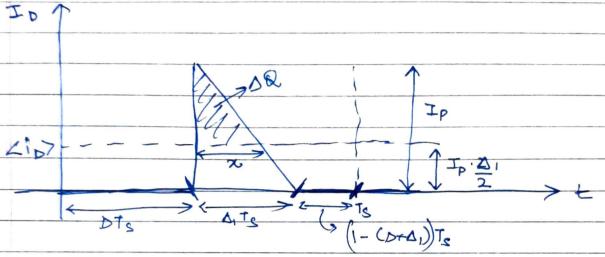

Abo,
$$I_{P}\left(1-\frac{\Delta_{1}}{2}\right) = I_{P} \Rightarrow \chi = \Delta_{1} I_{3} \left(2-\Delta_{1}\right)$$

$$\chi \qquad \Delta_{1} I_{S} \qquad \qquad 2$$

$$\stackrel{=}{=} dQ = \underbrace{1 \cdot \Delta_1 T_2 \left(2 - \Delta_1\right) \cdot J_p \left(\frac{2 - \Delta_1}{2}\right)}_{=} = \underbrace{J_p \cdot \Delta_1 T_2 \left(2 - \Delta_1\right)^2}_{=}$$

$$\Rightarrow \Delta V_0 = \Delta Q = \Delta_1 T_3 \left(2 - \Delta_1 \right)^2 \cdot V_d D \cdot T_3 \left(D + \Delta_1 \right)$$

$$\Delta V_b = V_0 T_3^2 D \cdot \Delta_1 \cdot (D \times \Delta_1) \cdot (2 - \Delta_1)^2$$

$$16L$$