

EE 238

Power Engineering - II

Power Electronics





Lecture 6

Instructor: Prof. Anshuman Shukla

Email: ashukla@ee.iitb.ac.in

Thought process in analyzing basic DC/DC converters

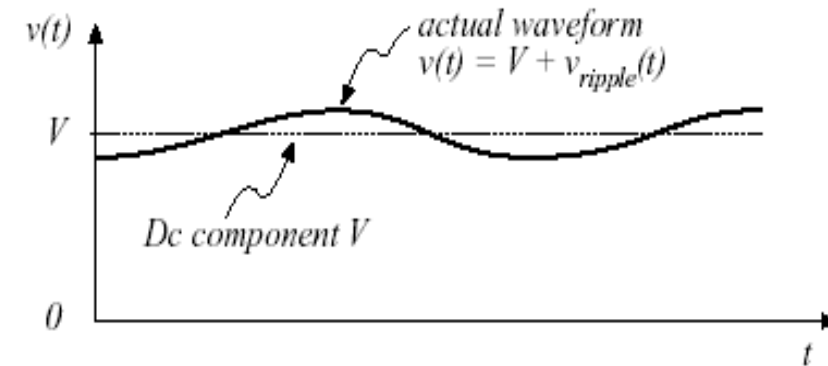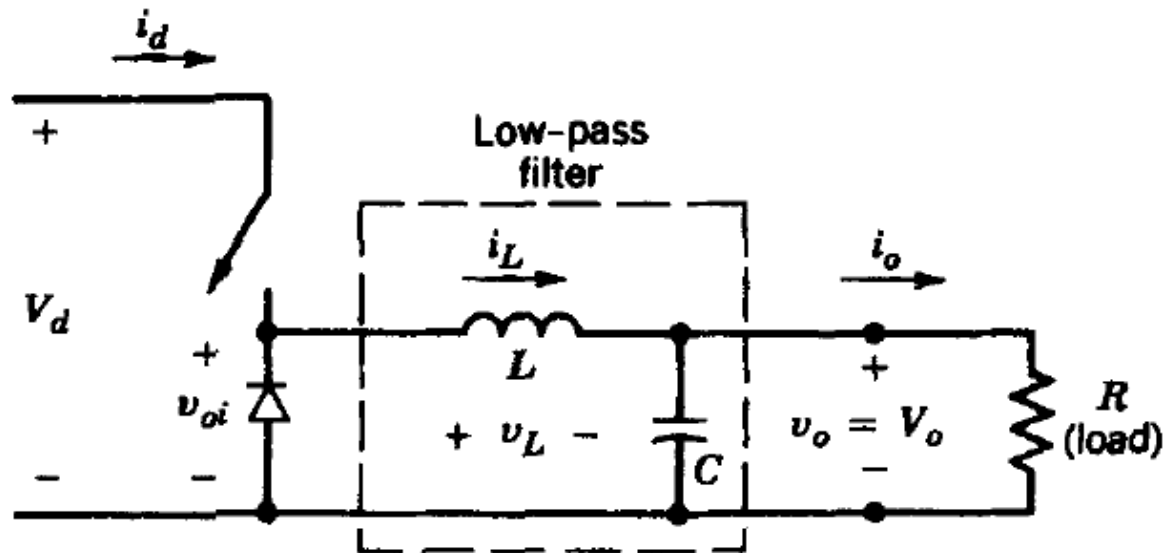- ⊕ Basic operation principle (qualitative analysis)
 - How does current flow during different switching states
 - How is energy transferred during different switching states
- ⊕ Verification of small ripple approximation
- ⊕ Derivation of inductor voltage waveform during different switching states
- ⊕ Quantitative analysis according to inductor volt-second balance or capacitor charge balance



$$|v_{ripple}| \ll V$$



$$v(t) \approx V$$

Steady-state Analysis

DC steady state in power converters



- DC steady state analysis is useful for
 - Thorough understanding of the operation, including various sub-intervals and modes of operation
 - Deriving input-output voltage and current relationships of various converter topologies
 - Design of various components such as inductors, capacitors, transformers
 - Selection of voltage and current ratings of semiconductor devices
 - Loss analysis

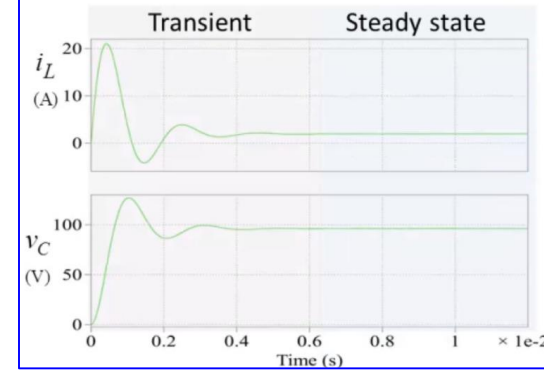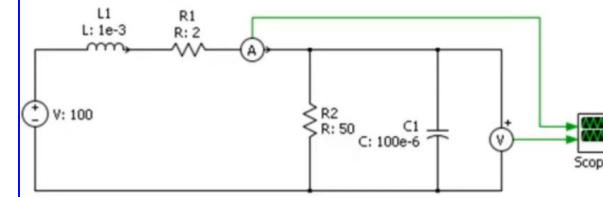DC Steady state in non-switching circuits



In non-switching circuits, DC steady state can be defined as a condition when all the variables (voltages, currents) are **CONSTANT** in time

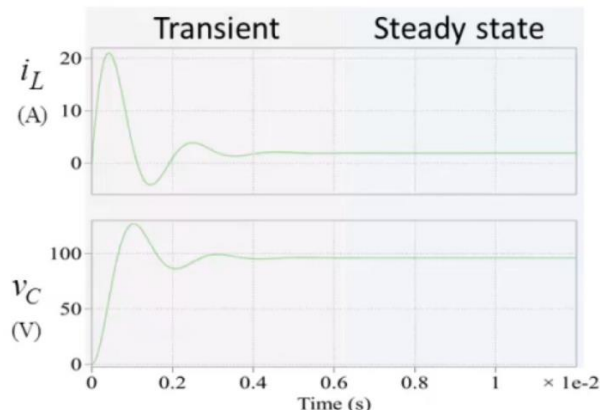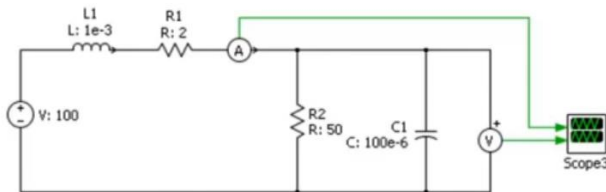DC Steady state in non-switching circuits




- Since,

$$v_L = L \frac{di_L}{dt}$$
 and i_L is constant, $v_L = 0$
 and inductor is considered as a short circuit in dc steady state for non-switching circuits
- Since,

$$i_C = C \frac{dv_C}{dt}$$
 and v_C is constant, $i_C = 0$
 and capacitor is considered as a open circuit in dc steady state

DC steady state in switching converters

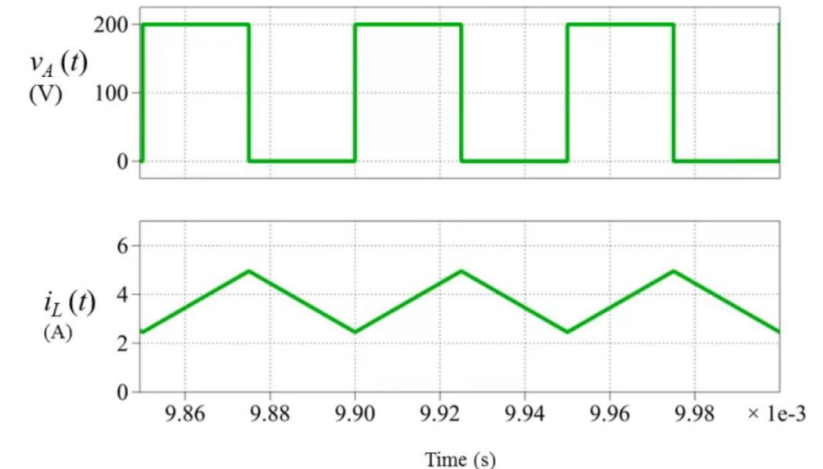- In a switching converter, most of the voltages and currents are always switching or time varying
- Need for a different definition of DC steady state




Concept of DC steady state in switching converters

A switching converter is in DC steady state, if

- ALL waveforms repeat exactly every switching period

Example: $i_A(t) = i_A(t-T_s)$

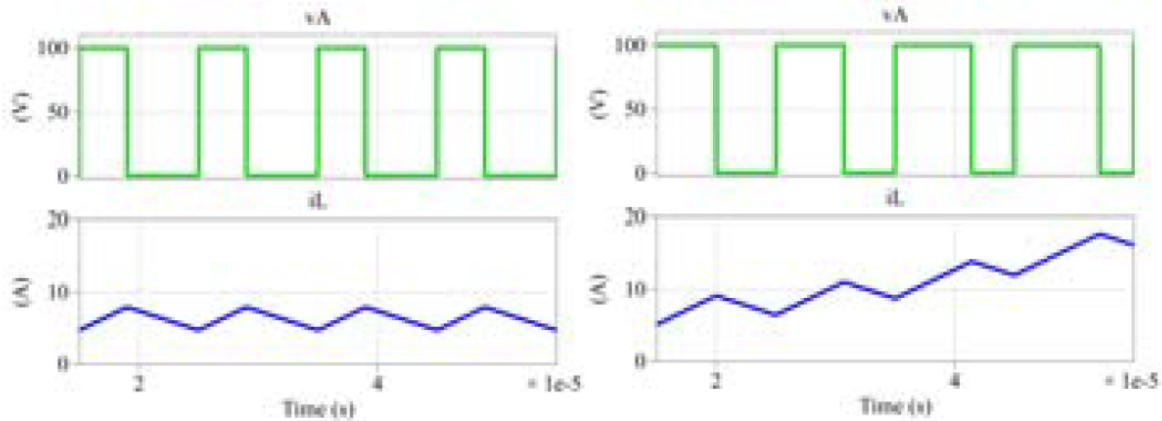


Steady state

Transient

Concept of DC steady state in switching converters


A switching converter is in DC steady state, if

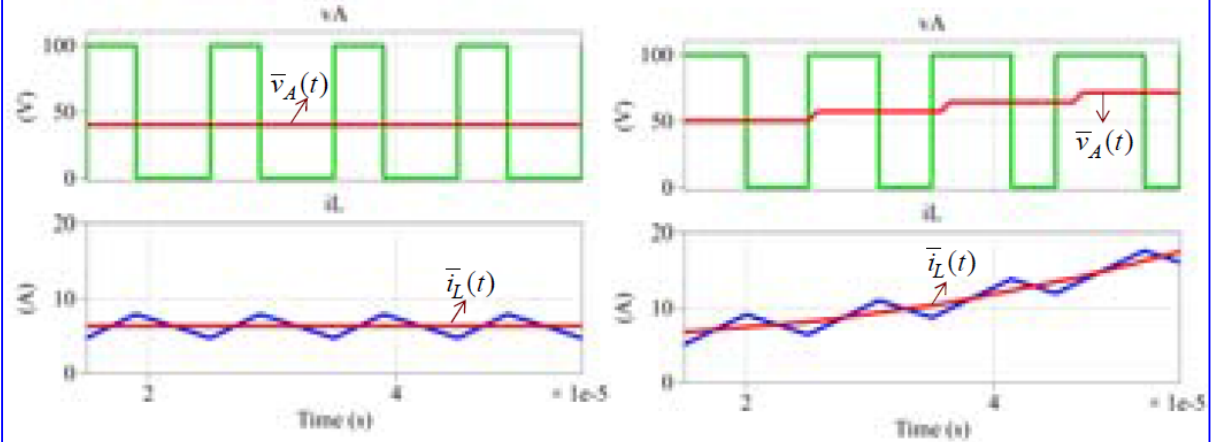- CCA values of **ALL** variables remain constant




Steady state

Transient

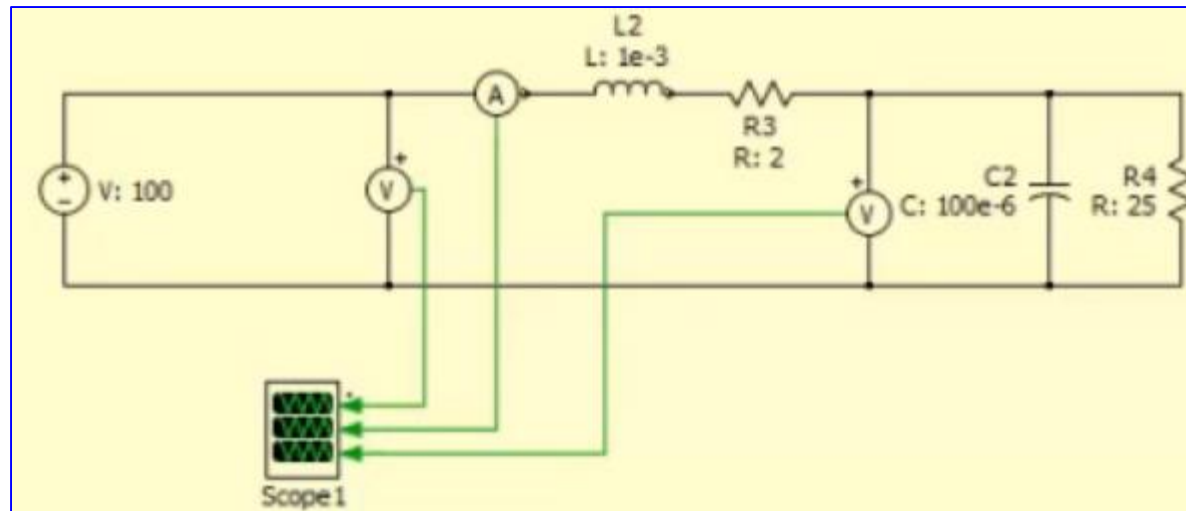

Simulation examples

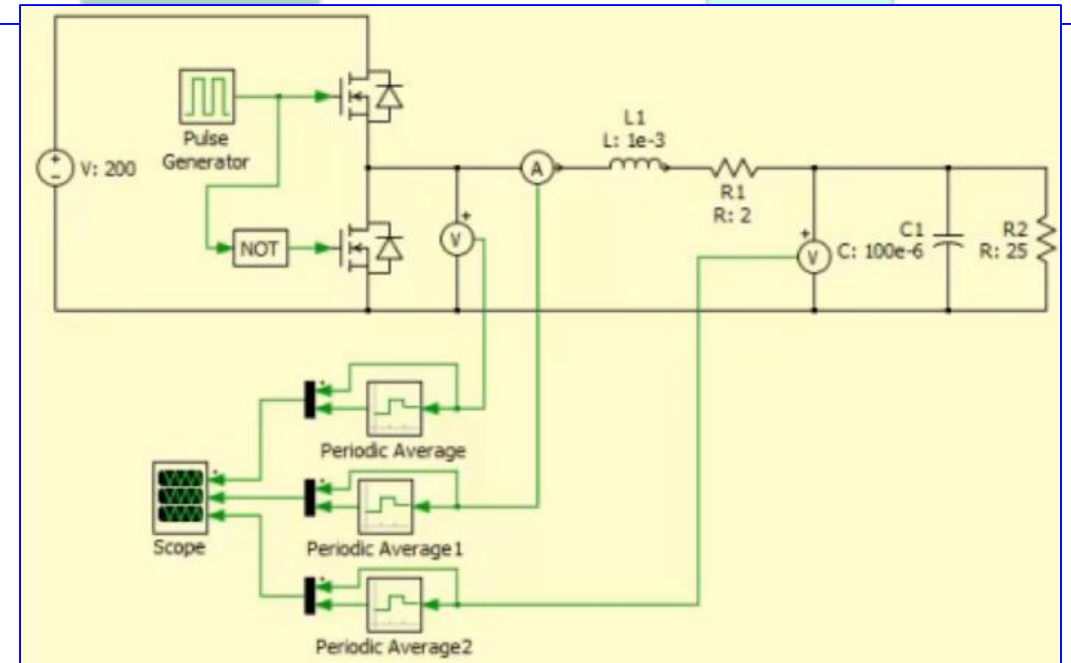

DC steady state characteristics

Non-switching circuits

All instantaneous quantities (voltages, currents) are constant

Instantaneous voltage across an inductor is zero; inductor can be considered a short for analysis and L value has no impact in steady state




Instantaneous current through a capacitor is zero; capacitor can be considered open for analysis and C value has no impact in steady state

Switching circuits


All CCA (cycle-by-cycle) quantities (voltages, currents) are constant

CCA voltage across inductor is zero (volt-sec balance principle); inductance determines the switching frequency current ripple in steady state

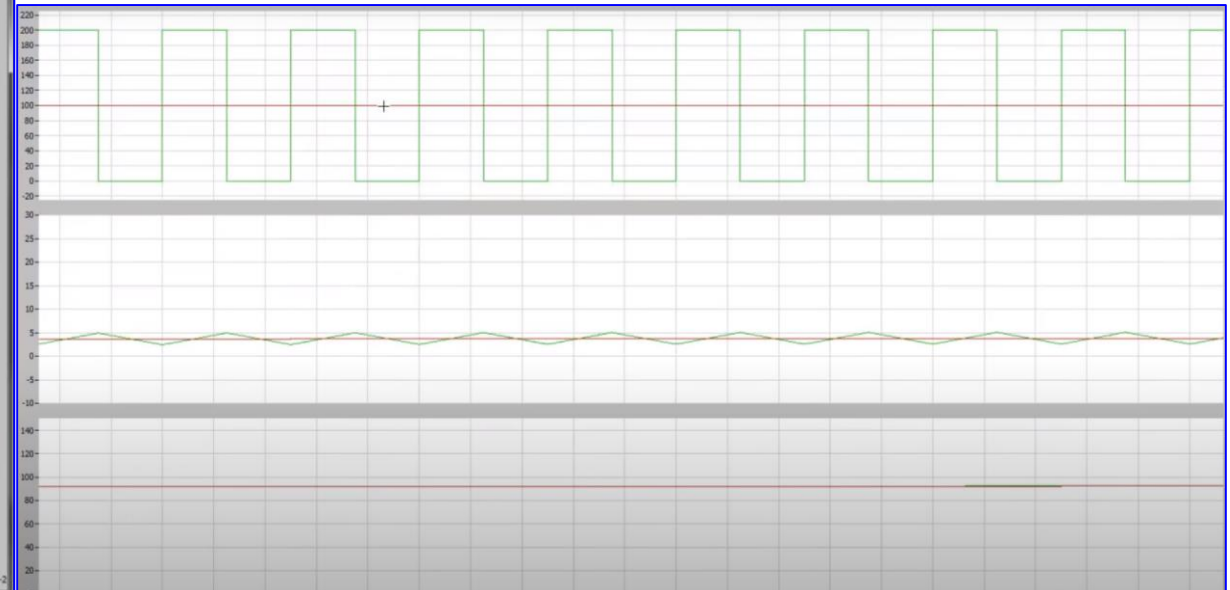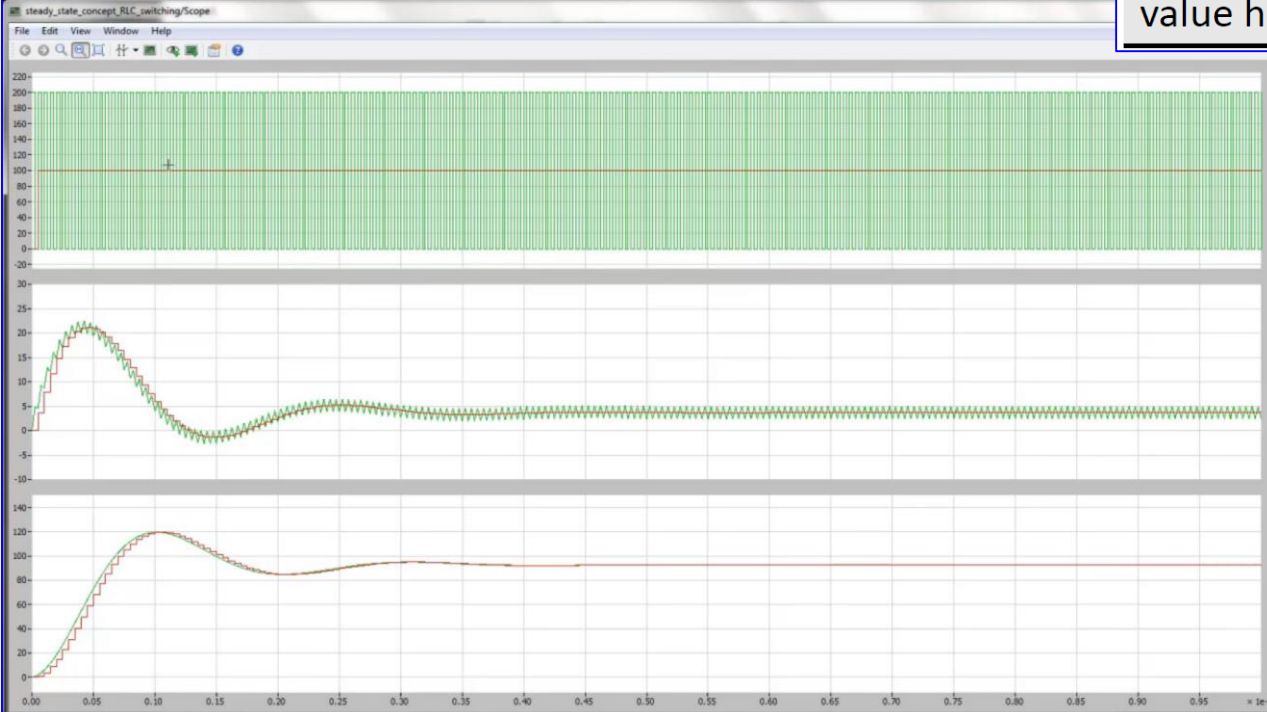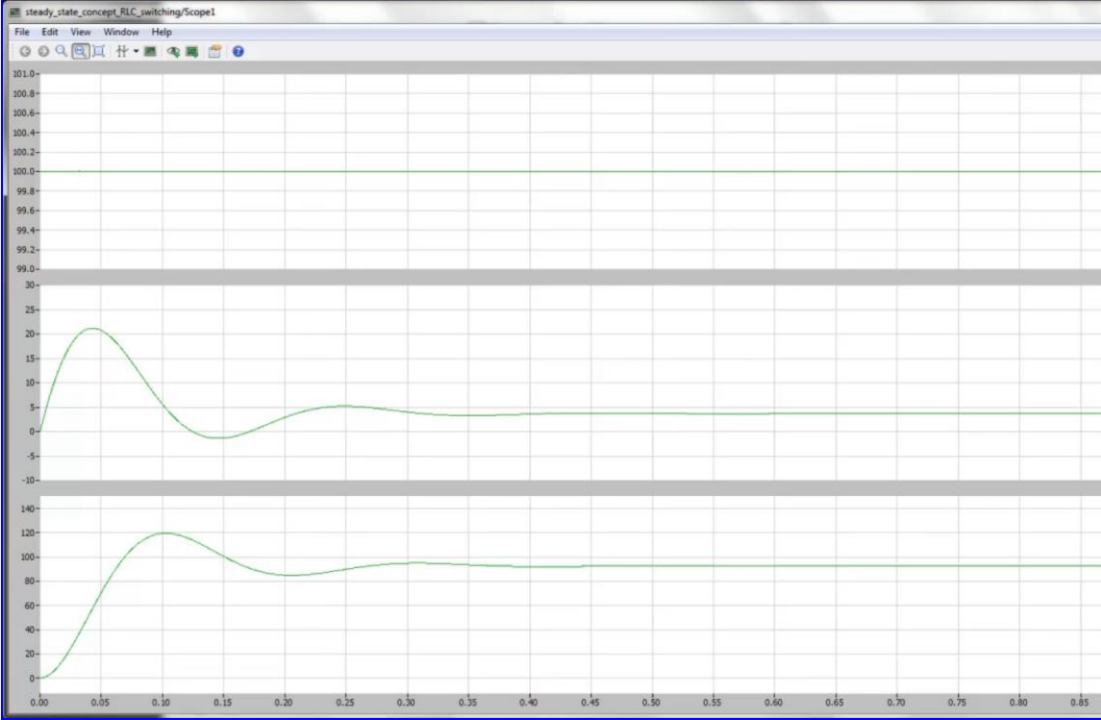
CCA current through a capacitor is zero (current-sec balance principle); capacitance determines the switching frequency voltage ripple in steady state




Buck converter analysis:

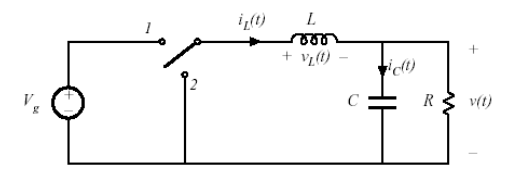

original
converter

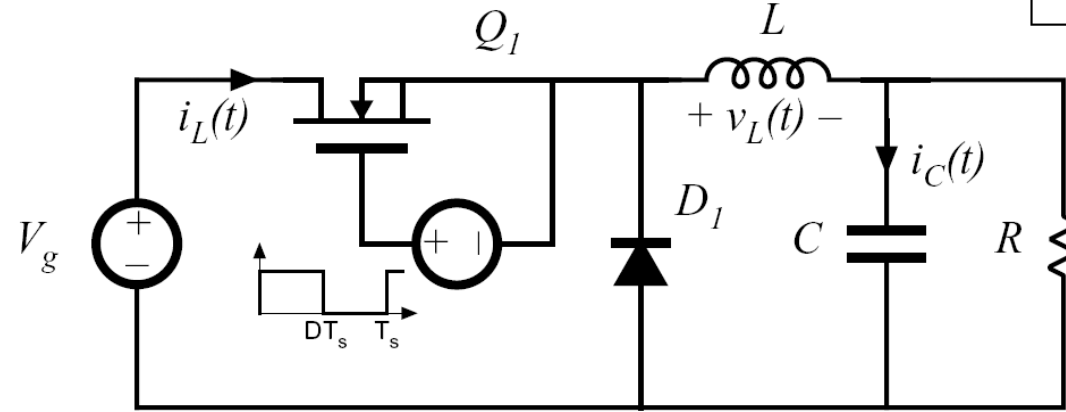


switch in position 1

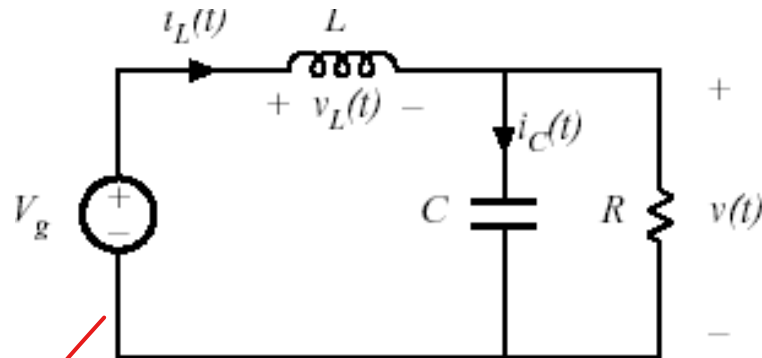

During the interval when the switch is on, the diode becomes reverse biased and the input provides energy to the load as well as to the inductor.

switch in position 2

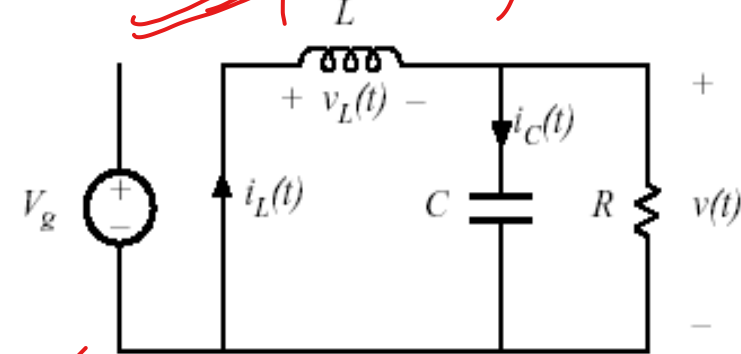


During the interval when the switch is off, the inductor current flows through the diode, transferring some of its stored energy to the load.

$$v_L = L \frac{di}{dt}$$

Inductor voltage and current

Subinterval 1: switch in position 1

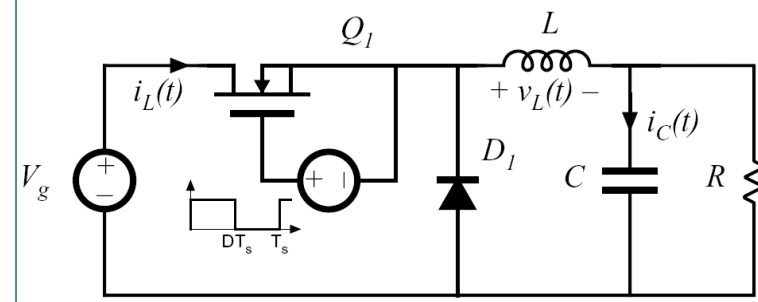


Inductor voltage

$$v_L = V_g - v(t)$$

Small ripple approximation:

$$v_L \approx V_g - V$$

w/o any ripple

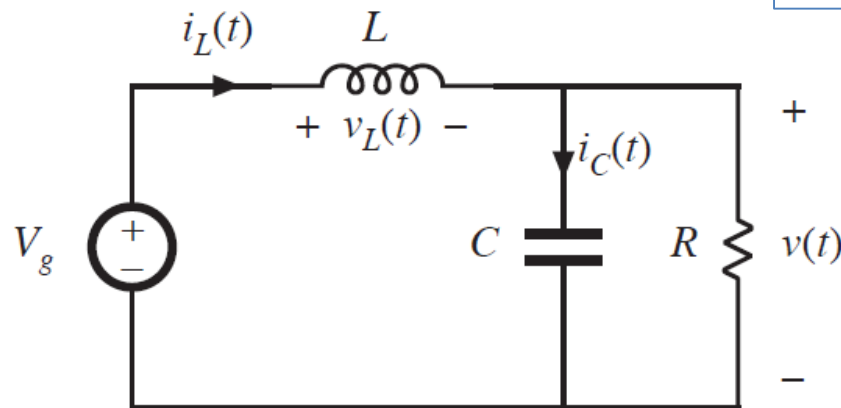

Knowing the inductor voltage, we can now find the inductor current via

$$v_L(t) = L \frac{di_L(t)}{dt}$$


Solve for the slope:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$

\Rightarrow The inductor current changes with an essentially constant slope

Inductor voltage and current

Subinterval 2: switch in position 2

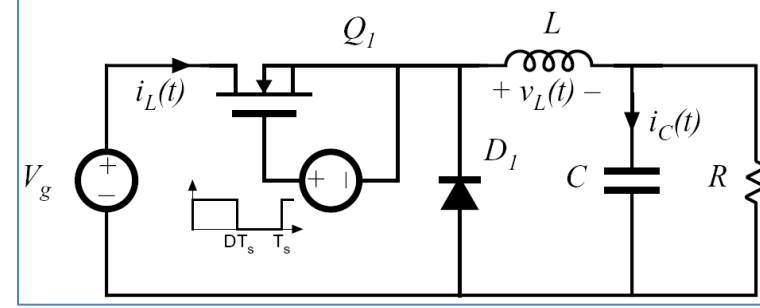


Inductor voltage

$$v_L(t) = -v(t)$$

✓ Small ripple approximation:

$$v_L(t) \approx -V$$

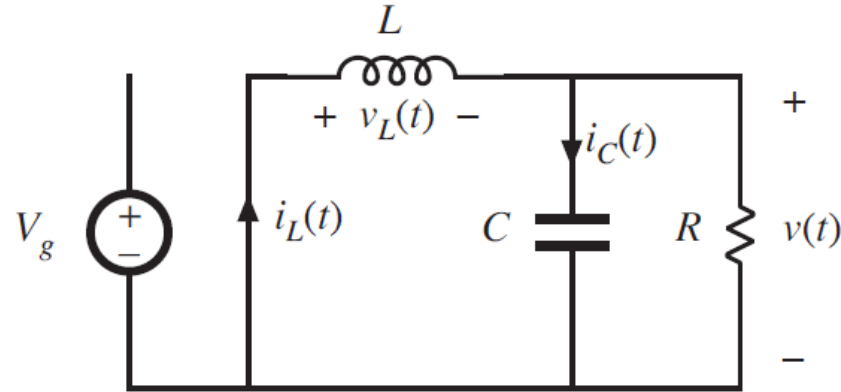

Knowing the inductor voltage, we can again find the inductor current via

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Solve for the slope:

$$\frac{di_L(t)}{dt} \approx -\frac{V}{L}$$



Falling current

⇒ The inductor current changes with an essentially constant slope

Small Ripple Approximation

$$v_o(t) = V_o + v_{o,ripple}(t) \quad \text{Peak-peak } v_{o,ripple} \text{ designed to be less than 1\% of } V_o$$

$$v_o(t) \approx V_o$$

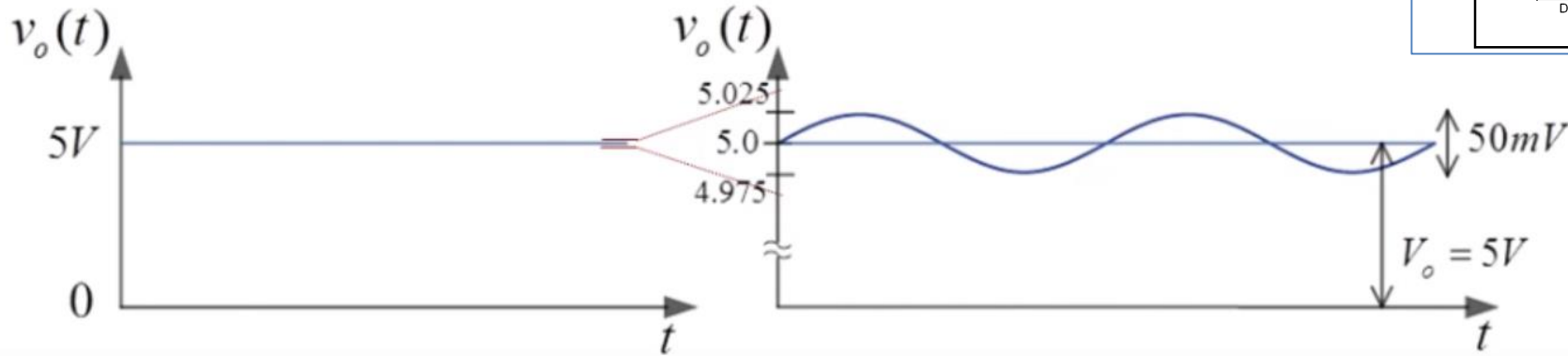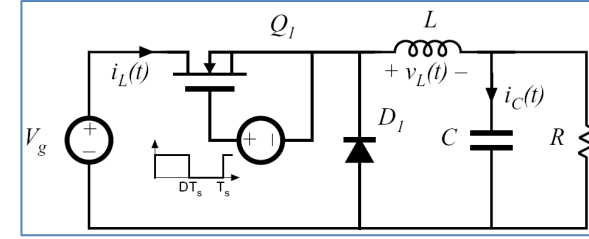


- For resistive loads as considered here initially,

$$i_o(t) \approx I_o$$



i.e., the high frequency component of inductor current flows only in the output capacitor, and negligible amount through the load

Characteristics of practical loads such as processors can be quite different



Inductor voltage and current waveforms

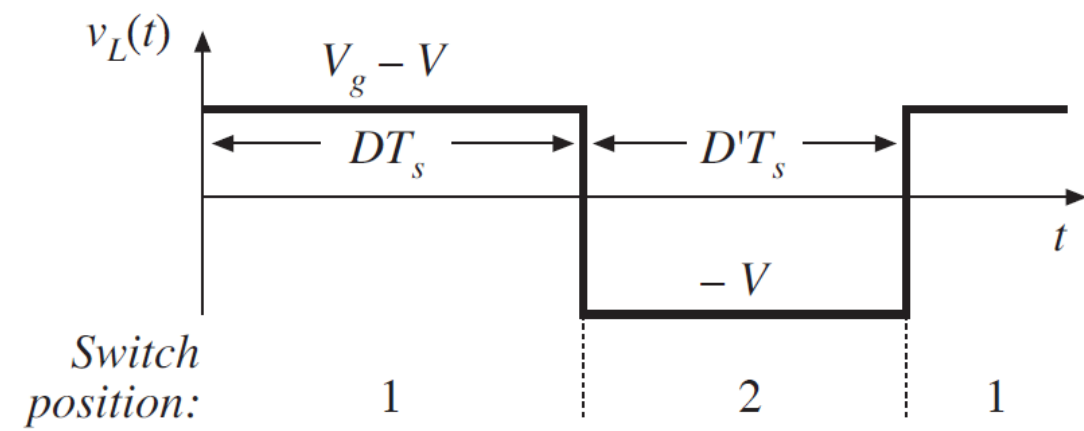

$$v_L(t) = L \frac{di_L(t)}{dt}$$

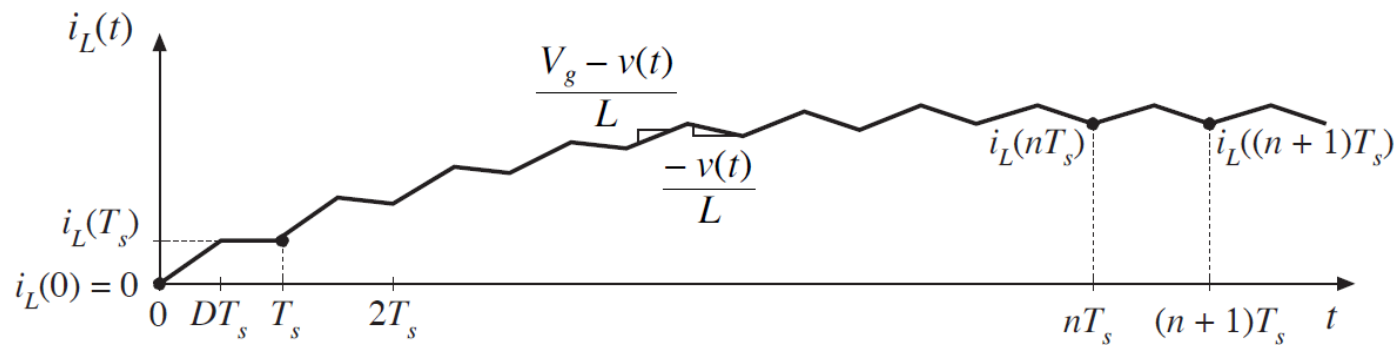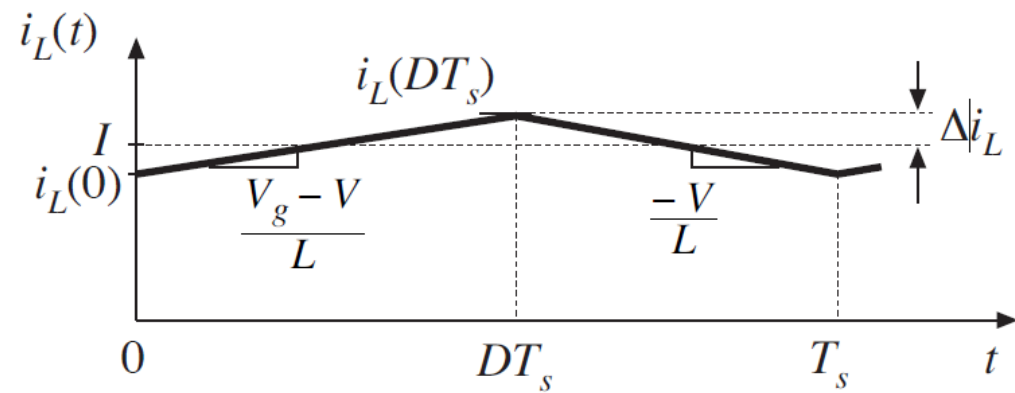

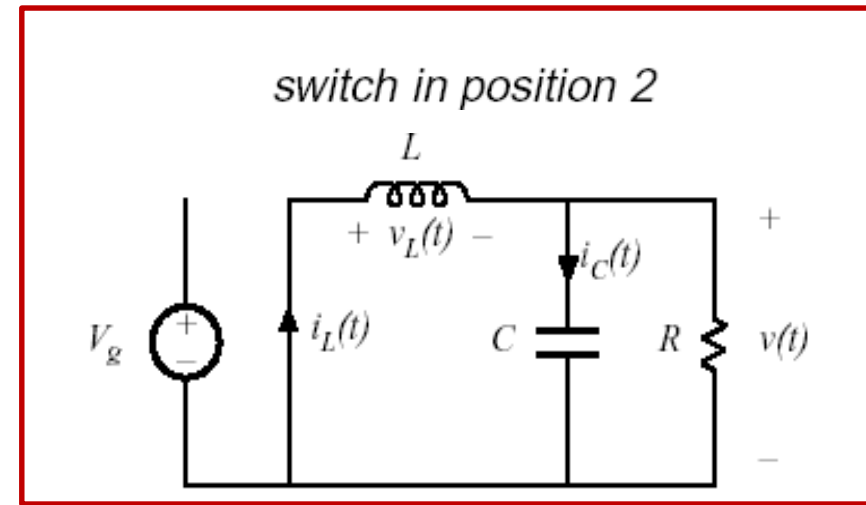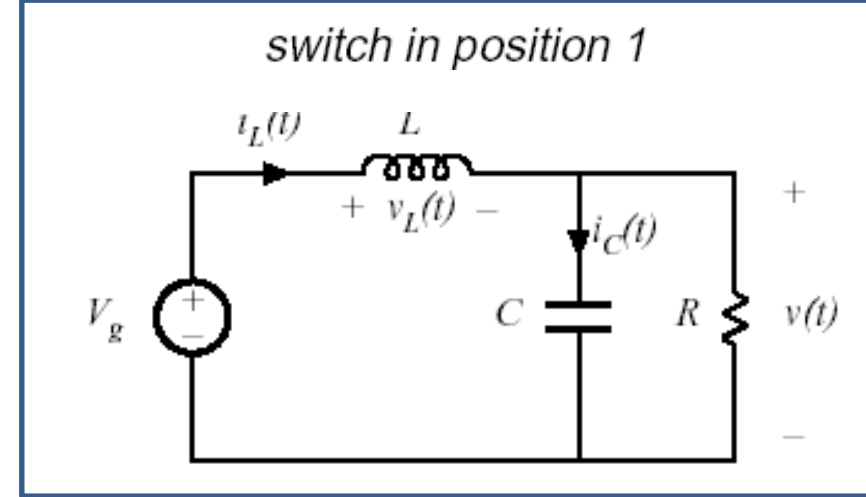When the converter operates in equilibrium: $i_L((n+1)T_s) = i_L(nT_s)$



Buck converter Analysis

When the switch is closed (on) :

$$v_L = V_g - V = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_g - V}{L}$$

Derivative of i_L is a positive constant.
Therefore i_L must increase linearly.

From Figure

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_g - V}{L}$$

$$(\Delta i_L)_{\text{closed}} = \left(\frac{V_g - V}{L} \right) \cdot DT$$


For switch opened,

$$v_L = -V = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{-V}{L}$$


$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{-V}{L}$$
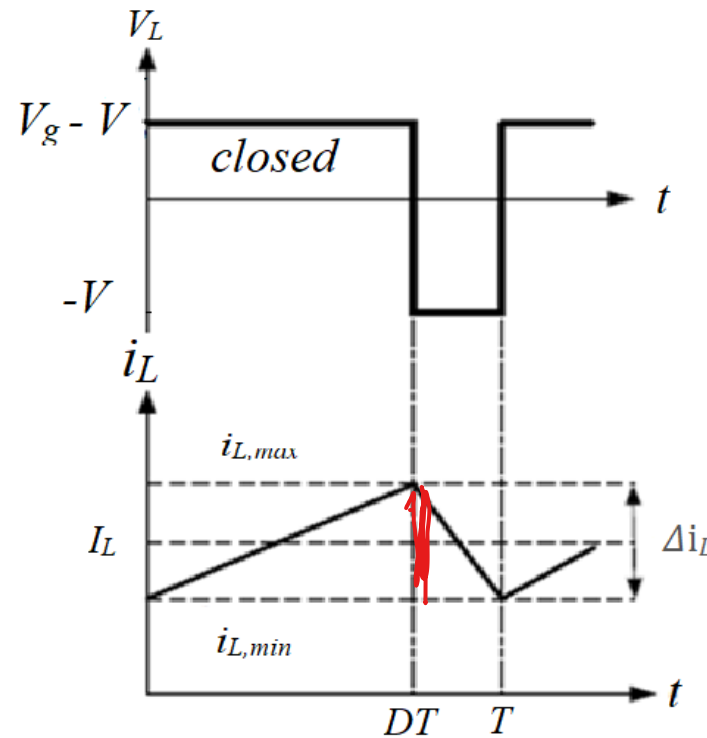
$$(\Delta i_L)_{\text{opened}} = \left(\frac{-V}{L} \right) \cdot (1-D)T$$



(change in i_L) = (slope)(length of subinterval)

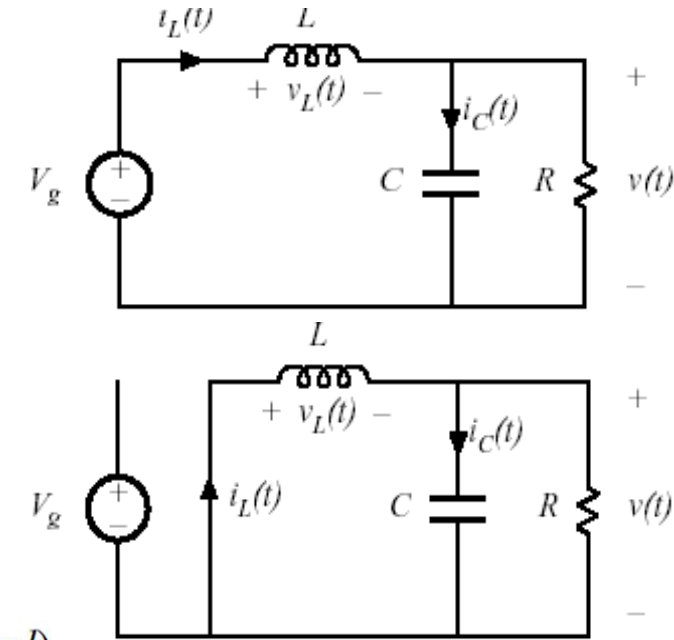Determination of inductor current ripple magnitude




Steady- state operation requires that i_L at the end of switching cycle is the same at the beginning of the next cycle. That is the change of i_L over one period is zero i.e :

$$(\Delta i_L)_{\text{closed}} + (\Delta i_L)_{\text{opened}} = 0$$

$$\left(\frac{V_g - V}{L} \right) \cdot DT_s - \left(\frac{-V}{L} \right) \cdot (1-D)T_s = 0$$

$$V = DV_g$$

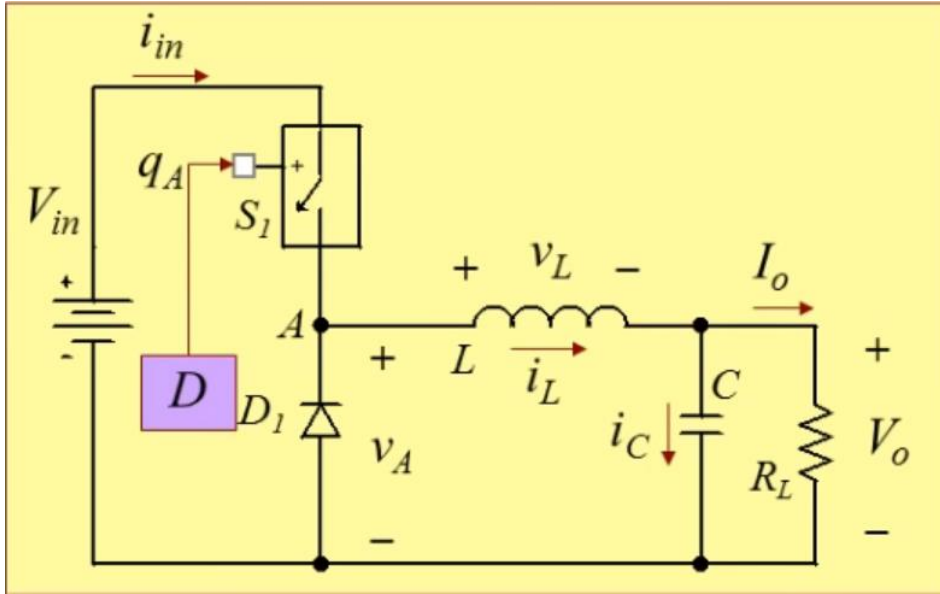

Neglecting power losses, the input power equals the output power.


$$P_d = P_o \Rightarrow V_d I_d = V_o I_o \Rightarrow \frac{I_o}{I_d} = \frac{V_d}{V_o} = \frac{1}{D}$$

$$V_o = D V_{in}$$

$$I_o = \frac{1}{D} I_{in}$$

$$\frac{V_o}{V_{in}} = D$$

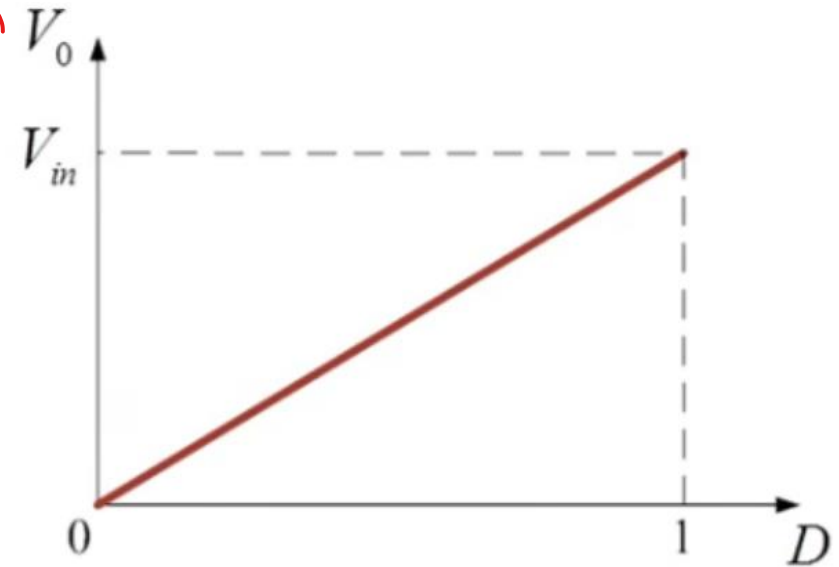
Input-output relationship for Buck converter





Characteristics of inductors and capacitors


Inductor

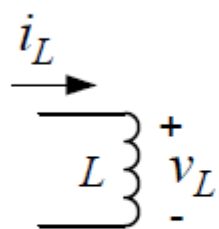

$$v_L(t) = L \frac{di_L(t)}{dt}$$



Capacitor

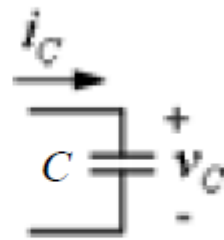

$$i_C(t) = C \frac{dv_C(t)}{dt}$$



Volt-sec balance in inductors

- The **average** (CCA) voltage across an inductor in **DC steady-state** is zero

$$\bar{v}_L = 0$$

**Instantaneous v-i relationship for inductor**

$$v_L(t) = L \frac{di_L(t)}{dt}; \quad i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau \quad \dots (1)$$

Substituting $t = t_0 + T_s$ in (1)

$$i_L(t_0 + T_s) = i_L(t_0) + \frac{1}{L} \int_{t_0}^{t_0 + T_s} v_L(\tau) d\tau \quad \dots (2)$$


In steady state

$$i_L(t_0 + T_s) = i_L(t_0) \quad \dots (3)$$

from (2) and (3)

$$\frac{1}{L} \int_{t_0}^{t_0 + T_s} v_L(t) dt = \frac{T_s}{L} \bar{v}_L = 0$$


$$\bar{v}_L = 0$$
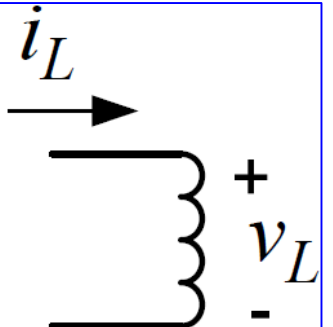
$$\bar{v}_L = L \frac{d\bar{i}_L}{dt} = 0$$

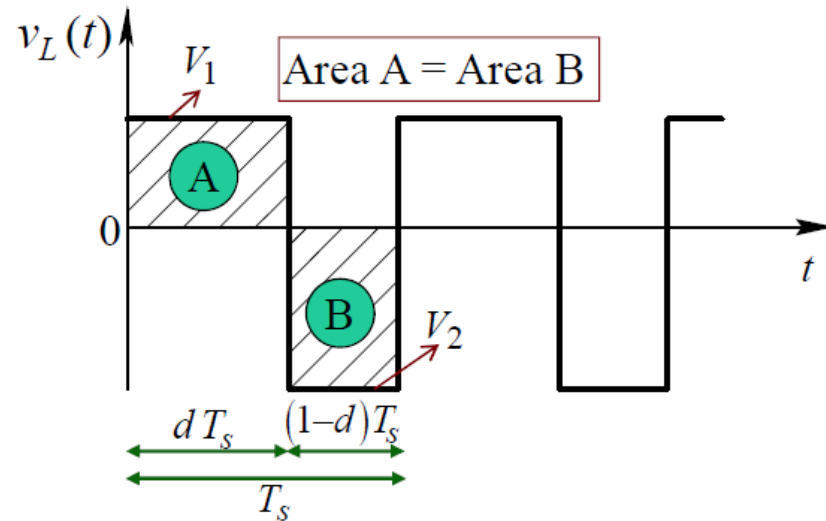
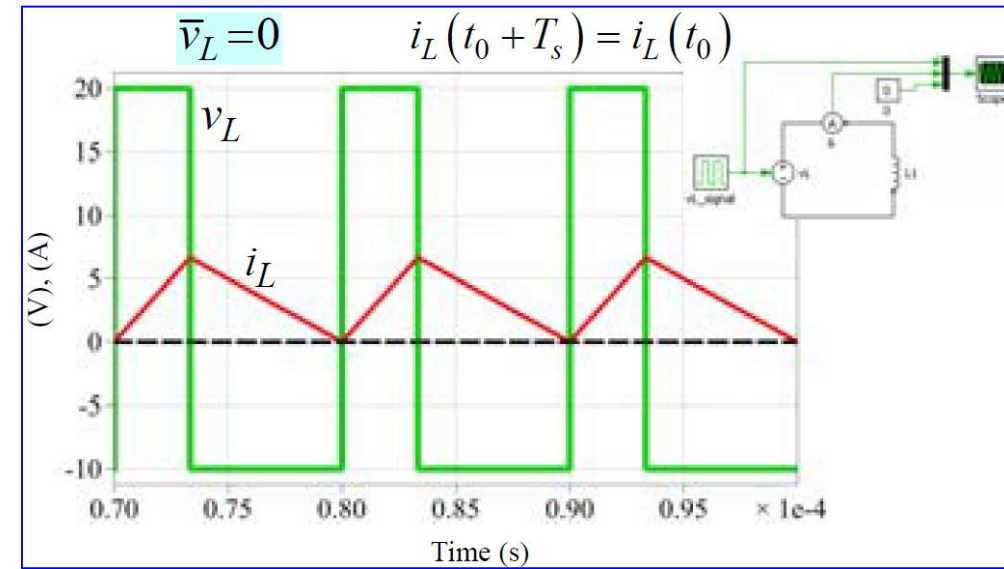
(since, \bar{i}_L should be constant in steady state)

Volt-sec balance in Inductors

$\bar{v}_L = 0$ does not imply that the inductor voltage is zero instantaneously, only the average over a complete period is zero




$$V_1 d + V_2 (1 - d) = 0$$




If volt-sec balance is violated

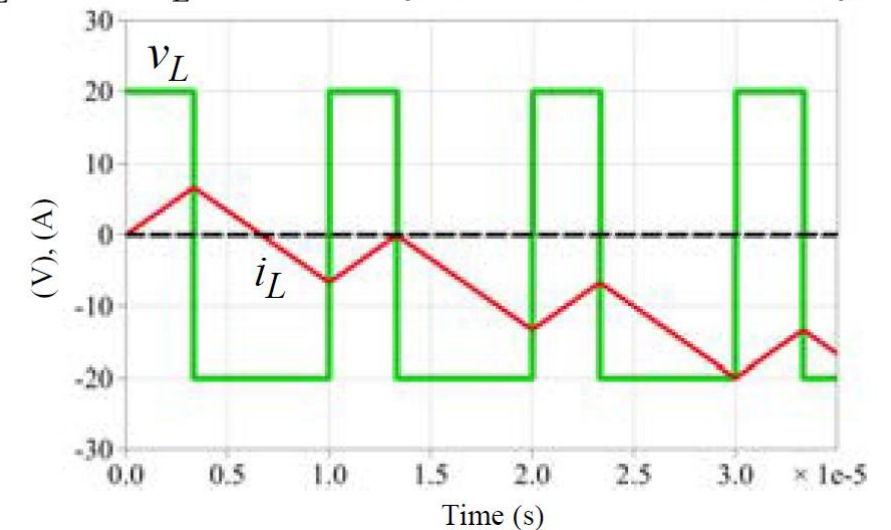$\bar{v}_L < 0 \Rightarrow \bar{i}_L$ continuously decreases \Rightarrow non-steady-state



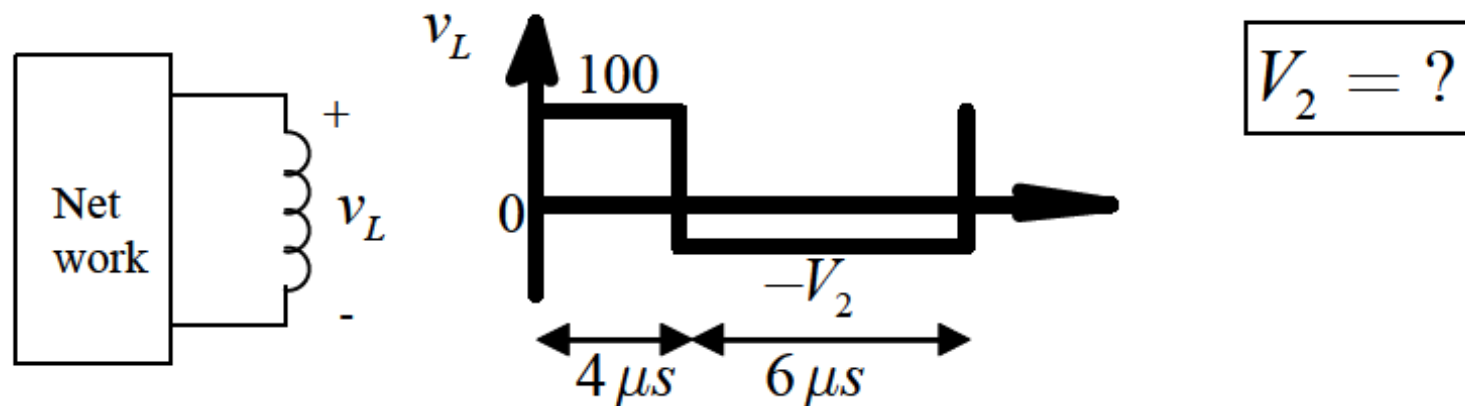
Example

Given that the circuit is in DC steady state, calculate V_2



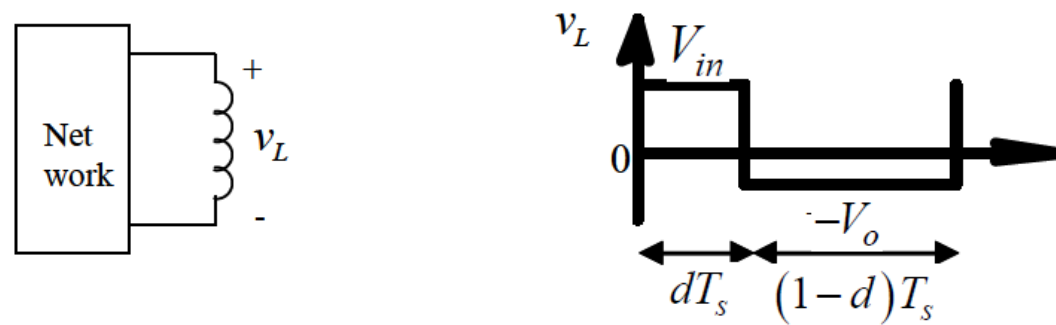
Example

Calculate the input-output relationship for a dc-dc converter, i.e, V_o / V_{in} , in terms of the duty ratio, d given the inductor voltage below



Inductor volt-second balance: Buck converter example

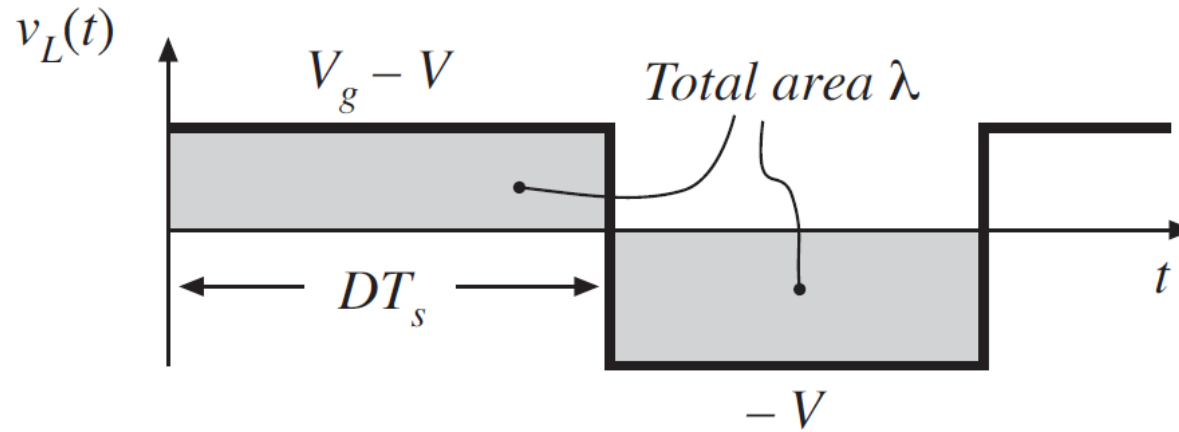Inductor voltage waveform,
previously derived:



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V :

$$0 = DV_g - (D + D')V = DV_g - V \quad \Rightarrow \quad V = DV_g$$

