

EE 238

Power Engineering - II

Power Electronics





Lecture 6

Instructor: Prof. Anshuman Shukla

Email: ashukla@ee.iitb.ac.in

Thought process in analyzing basic DC/DC converters

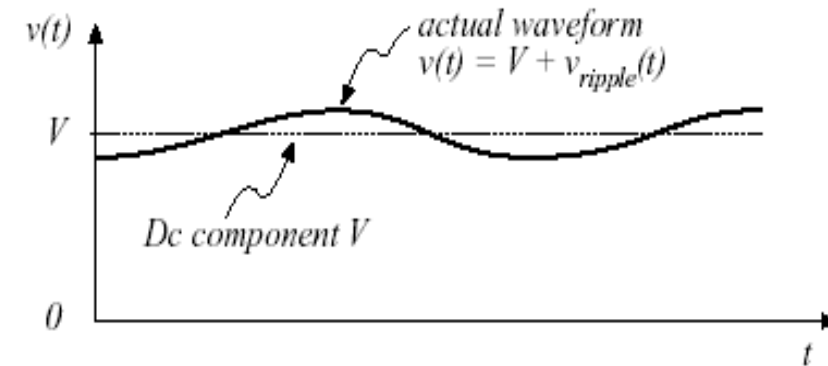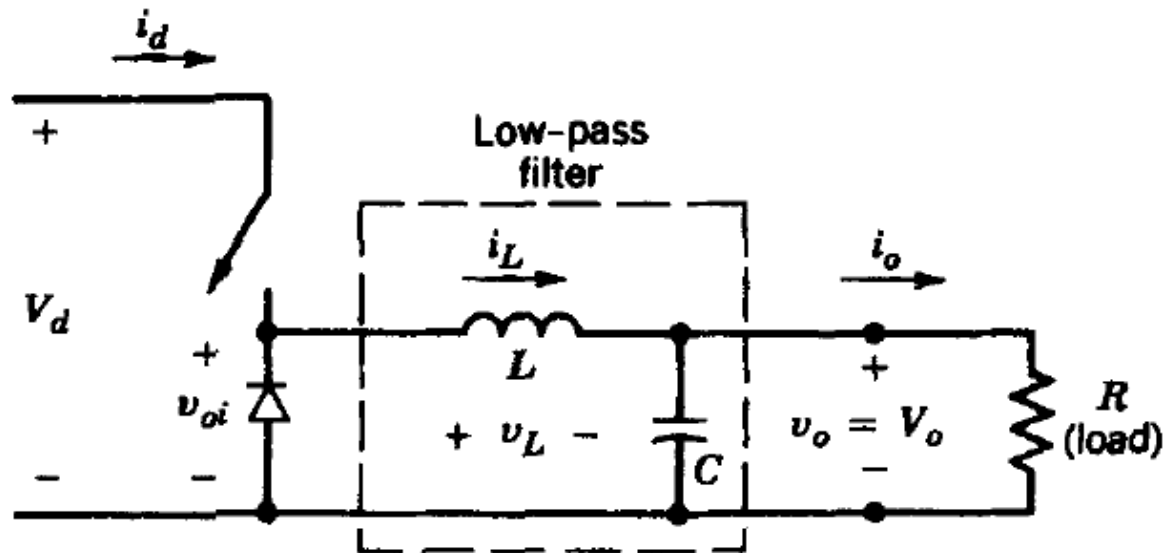- ⊕ Basic operation principle (qualitative analysis)
 - How does current flow during different switching states
 - How is energy transferred during different switching states
- ⊕ Verification of small ripple approximation
- ⊕ Derivation of inductor voltage waveform during different switching states
- ⊕ Quantitative analysis according to inductor volt-second balance or capacitor charge balance





$$|v_{ripple}| \ll V$$
$$v(t) \approx V$$

Steady-state Analysis

DC steady state in power converters



- DC steady state analysis is useful for
 - Thorough understanding of the operation, including various sub-intervals and modes of operation
 - Deriving input-output voltage and current relationships of various converter topologies
 - Design of various components such as inductors, capacitors, transformers
 - Selection of voltage and current ratings of semiconductor devices
 - Loss analysis

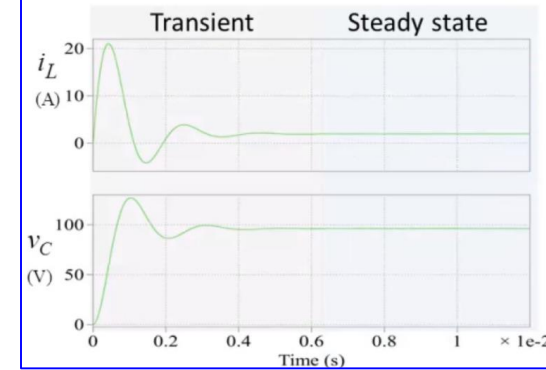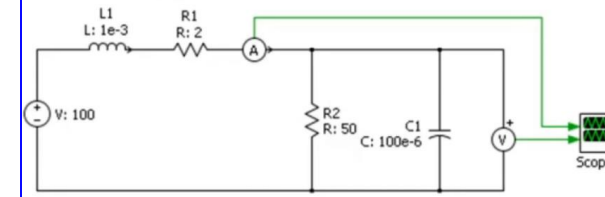DC Steady state in non-switching circuits



In non-switching circuits, DC steady state can be defined as a condition when all the variables (voltages, currents) are CONSTANT in time

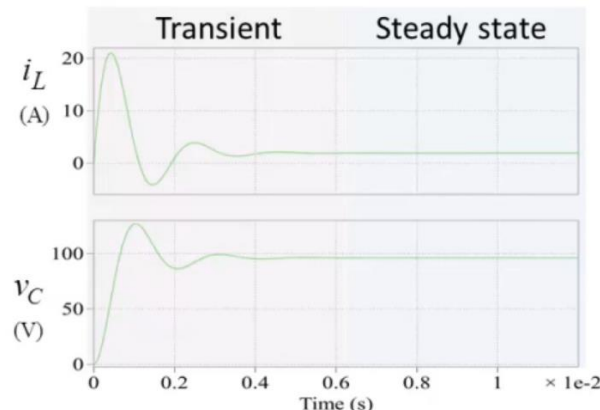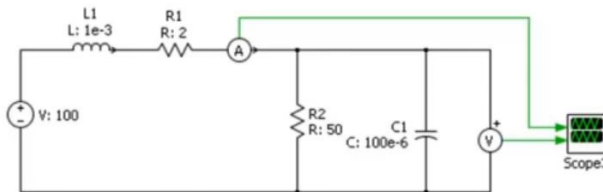DC Steady state in non-switching circuits




- Since,

$$v_L = L \frac{di_L}{dt}$$
 and i_L is constant, $v_L = 0$
 and inductor is considered as a short circuit in dc steady state for non-switching circuits
- Since,

$$i_C = C \frac{dv_C}{dt}$$
 and v_C is constant, $i_C = 0$
 and capacitor is considered as an open circuit in dc steady state

DC steady state in switching converters

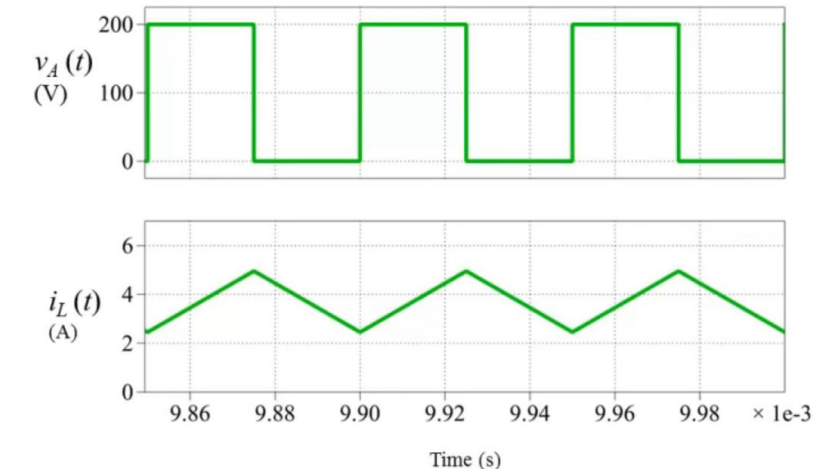- In a switching converter, most of the voltages and currents are always switching or time varying
- Need for a different definition of DC steady state




Concept of DC steady state in switching converters

A switching converter is in DC steady state, if

- ALL waveforms repeat exactly every switching period

Example: $i_A(t) = i_A(t-T_s)$

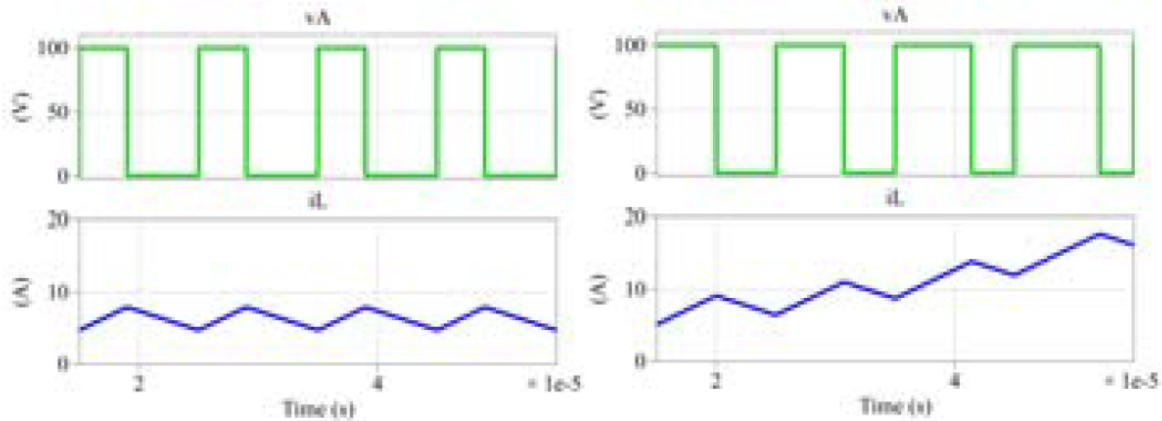


Steady state

Transient

Concept of DC steady state in switching converters


A switching converter is in DC steady state, if

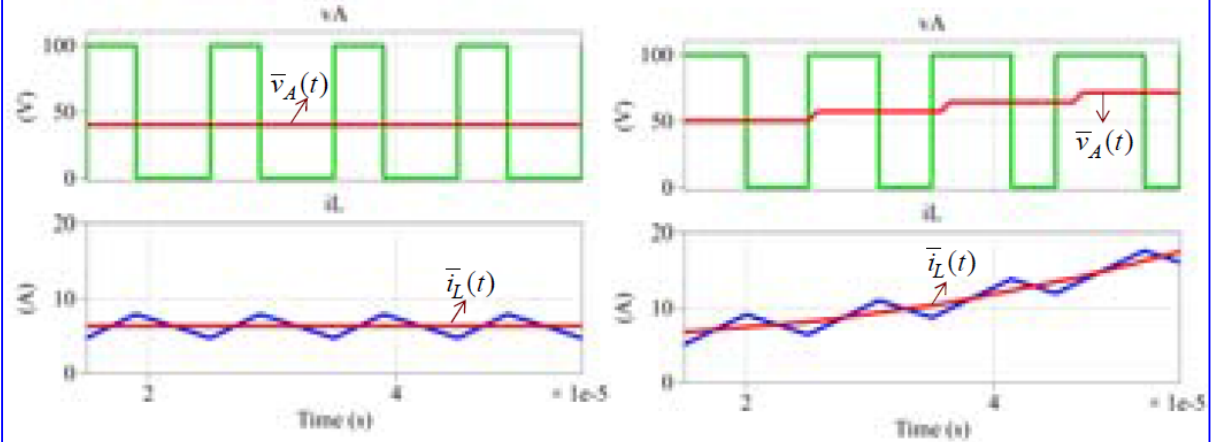- CCA values of **ALL** variables remain constant




Steady state

Transient

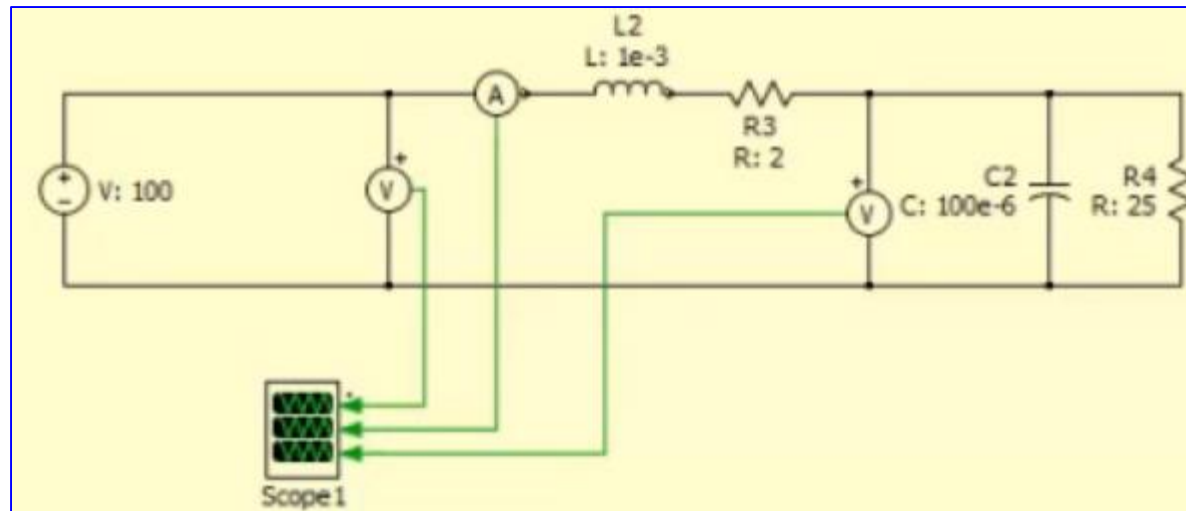

Simulation examples

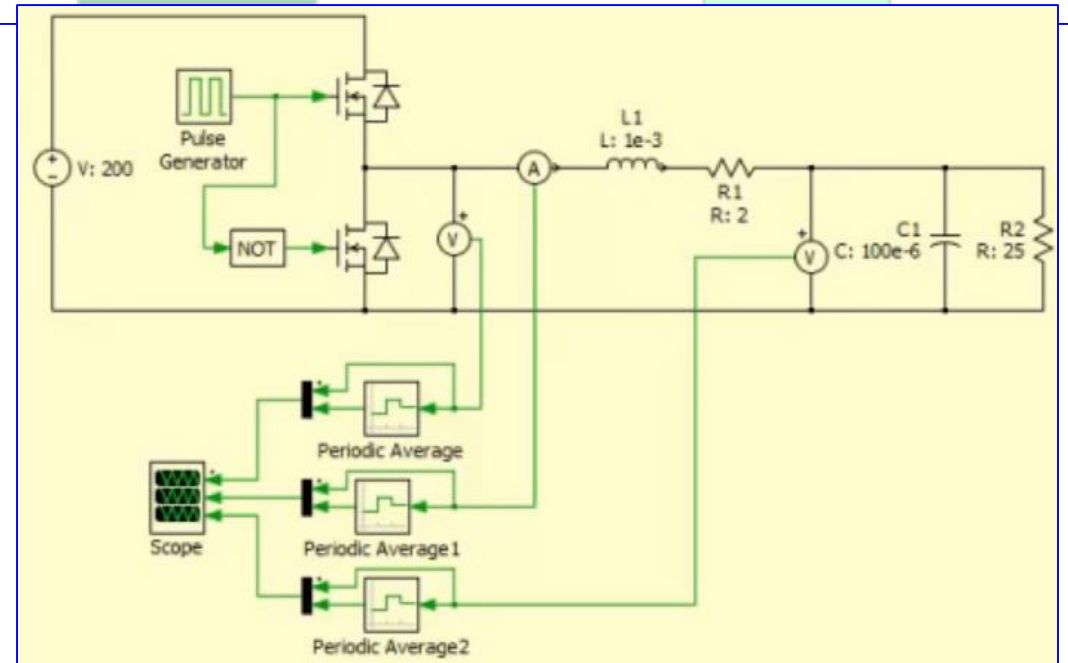

DC steady state characteristics

Non-switching circuits

All instantaneous quantities (voltages, currents) are constant

Instantaneous voltage across an inductor is zero; inductor can be considered a short for analysis and L value has no impact in steady state




Instantaneous current through a capacitor is zero; capacitor can be considered open for analysis and C value has no impact in steady state

Switching circuits



All CCA (cycle-by-cycle) quantities (voltages, currents) are constant

CCA voltage across inductor is zero (volt-sec balance principle); inductance determines the switching frequency current ripple in steady state

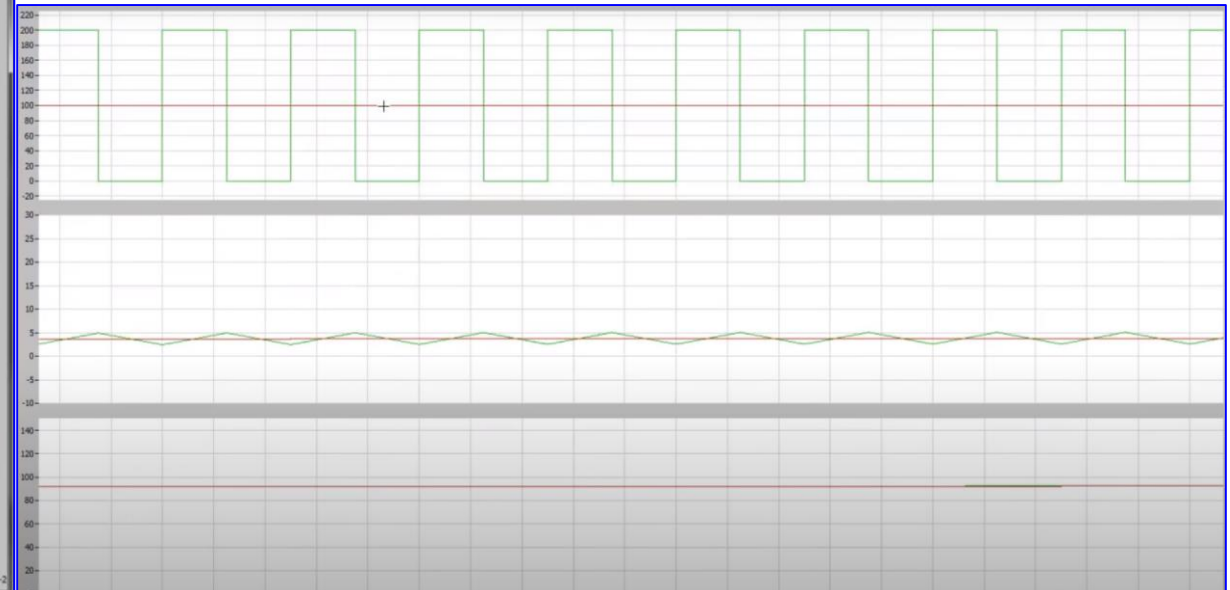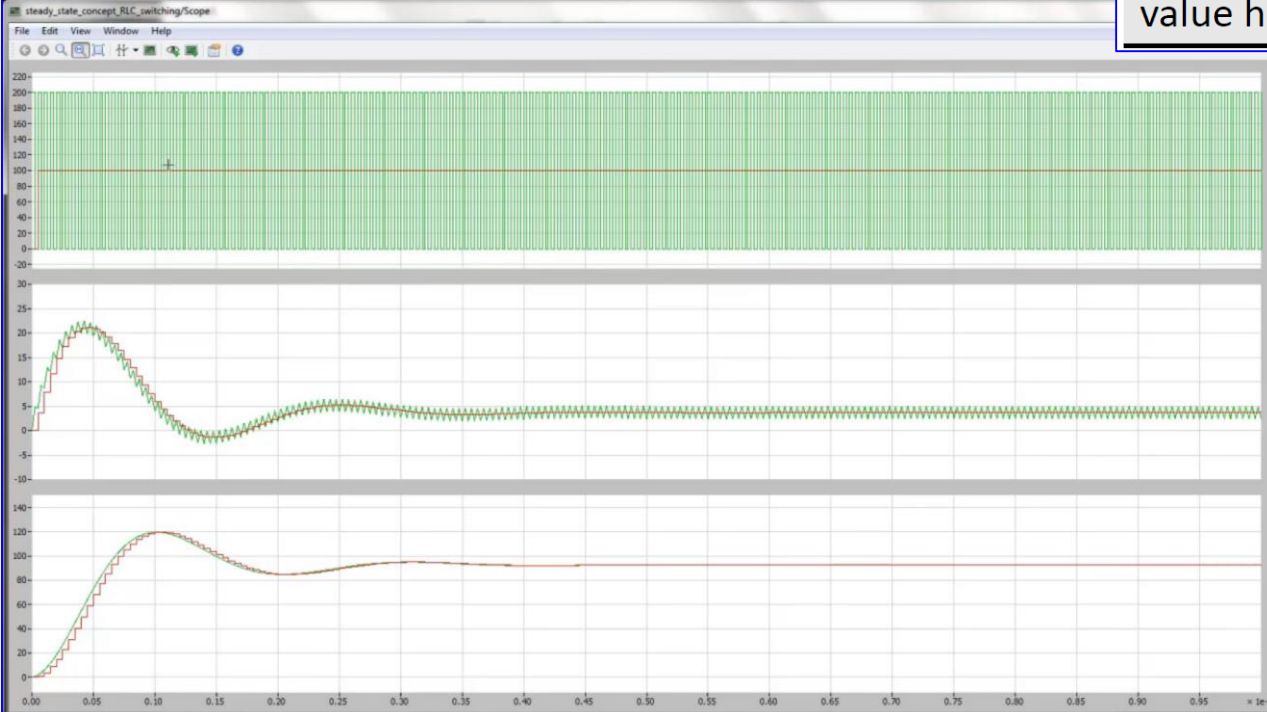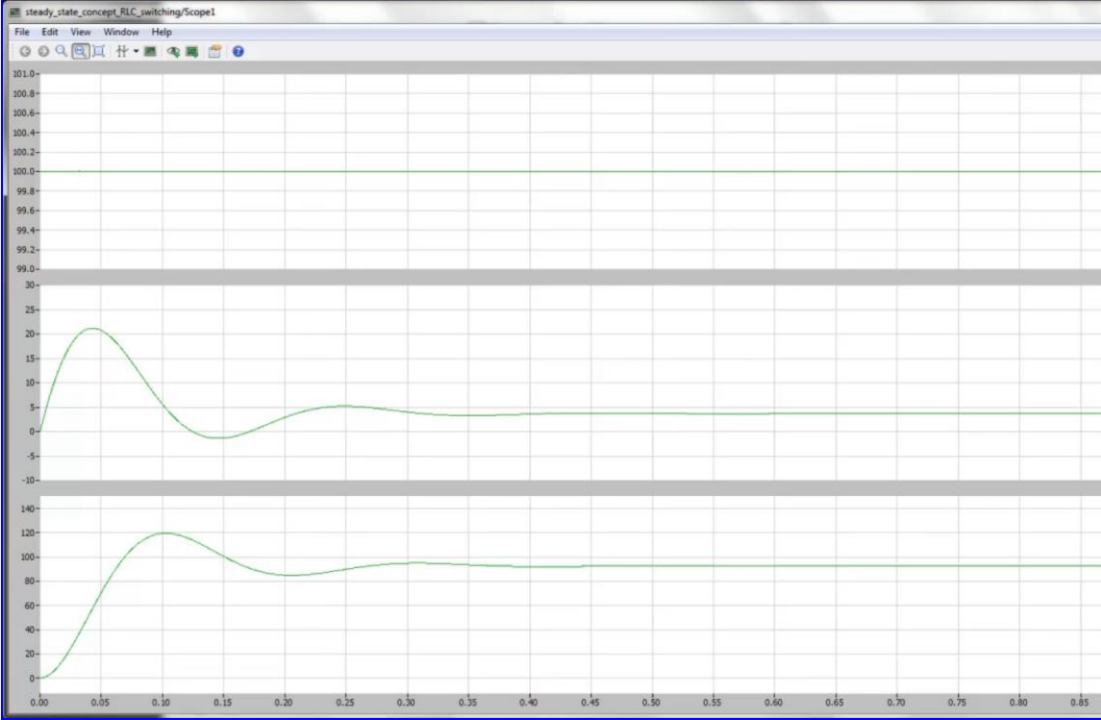
CCA current through a capacitor is zero (current-sec balance principle); capacitance determines the switching frequency voltage ripple in steady state



Buck converter analysis:

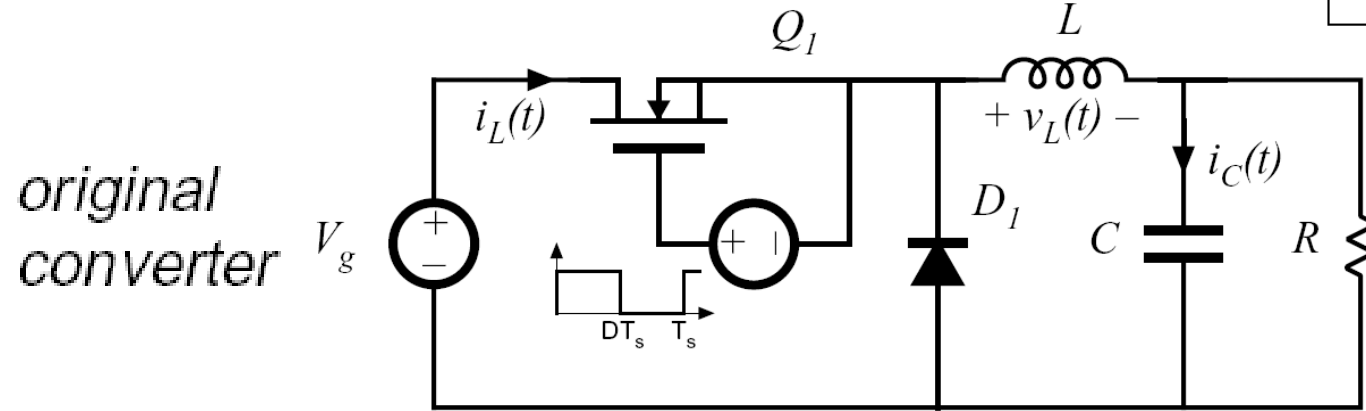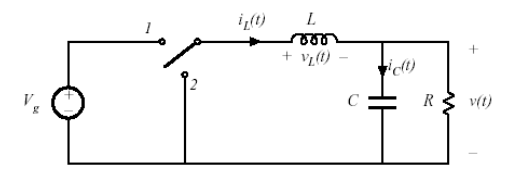


switch in position 1

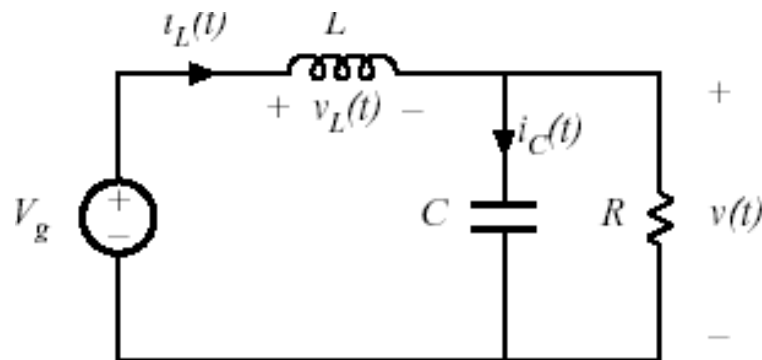

During the interval when the switch is on, the diode becomes reverse biased and the input provides energy to the load as well as to the inductor.


switch in position 2

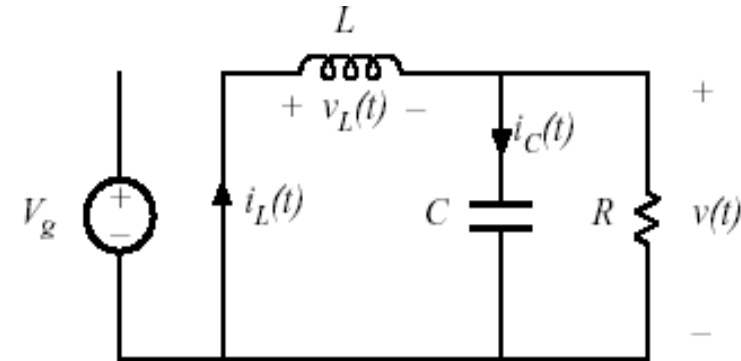

During the interval when the switch is off, the inductor current flows through the diode, transferring some of its stored energy to the load.

Inductor voltage and current

Subinterval 1: switch in position 1

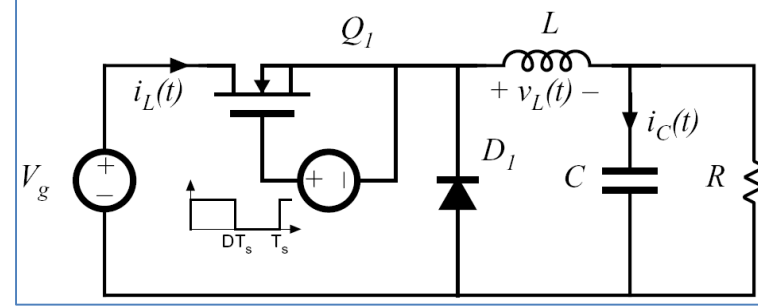


Inductor voltage

$$v_L = V_g - v(t)$$

Small ripple approximation:

$$v_L \approx V_g - V$$

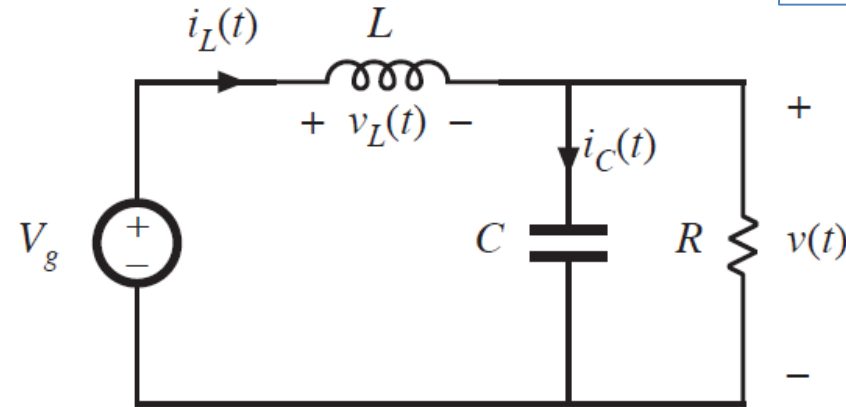

Knowing the inductor voltage, we can now find the inductor current via

$$v_L(t) = L \frac{di_L(t)}{dt}$$


Solve for the slope:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$

\Rightarrow *The inductor current changes with an essentially constant slope*

Inductor voltage and current

Subinterval 2: switch in position 2

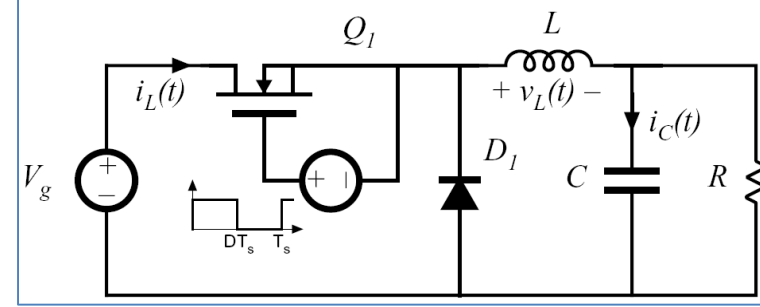


Inductor voltage

$$v_L(t) = -v(t)$$

Small ripple approximation:

$$v_L(t) \approx -V$$

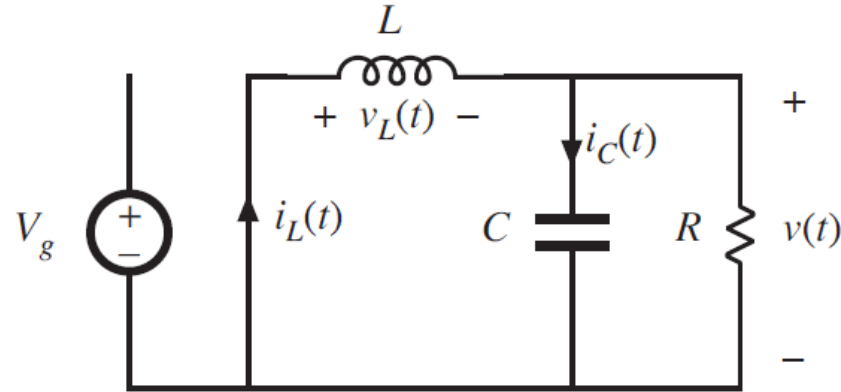

Knowing the inductor voltage, we can again find the inductor current via

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Solve for the slope:



$$\frac{di_L(t)}{dt} \approx -\frac{V}{L}$$

\Rightarrow *The inductor current changes with an essentially constant slope*

Small Ripple Approximation

$$v_o(t) = V_o + v_{o,ripple}(t) \quad \text{Peak-peak } v_{o,ripple} \text{ designed to be less than 1\% of } V_o$$

$$v_o(t) \approx V_o$$

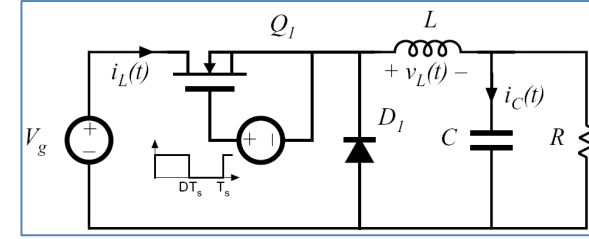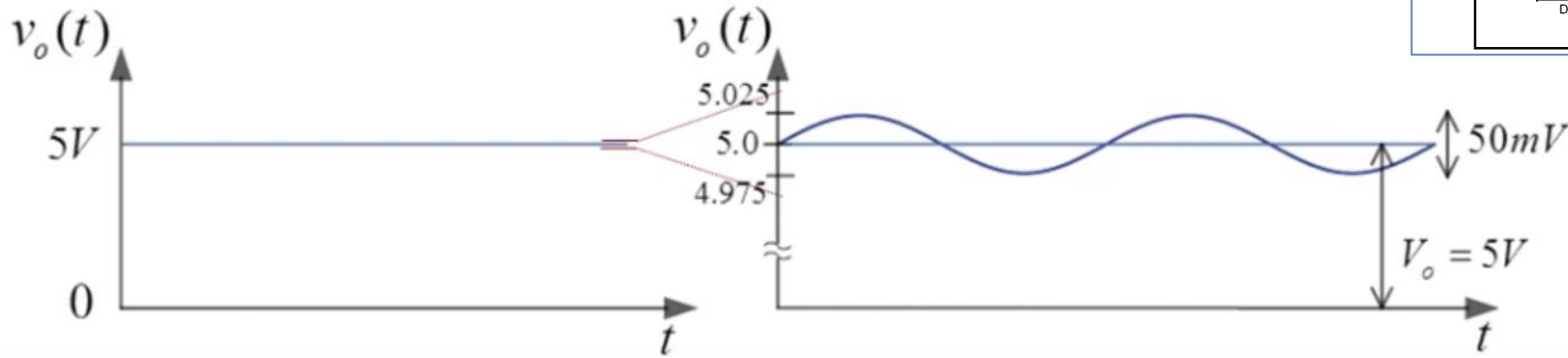


- For resistive loads as considered here initially,

$$i_o(t) \approx I_o$$



i.e., the high frequency component of inductor current flows only in the output capacitor, and negligible amount through the load

- Characteristics of practical loads such as processors can be quite different



Inductor voltage and current waveforms

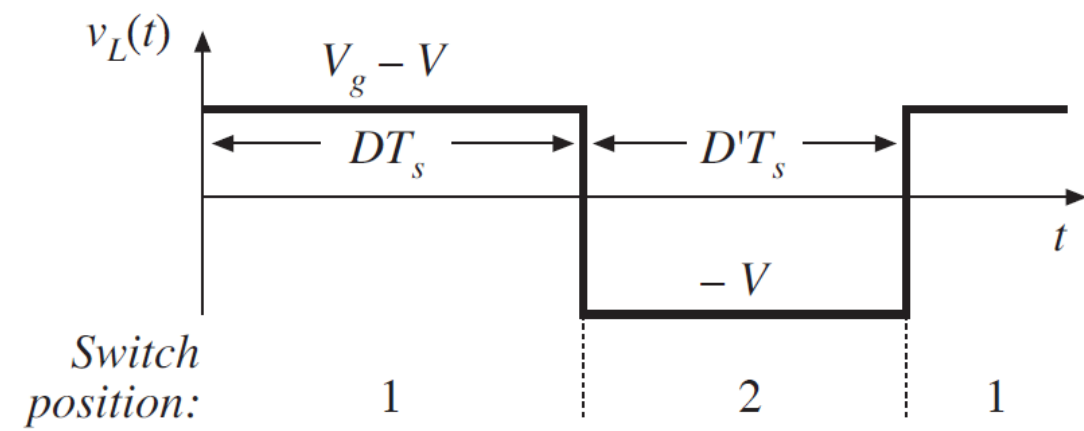

$$v_L(t) = L \frac{di_L(t)}{dt}$$

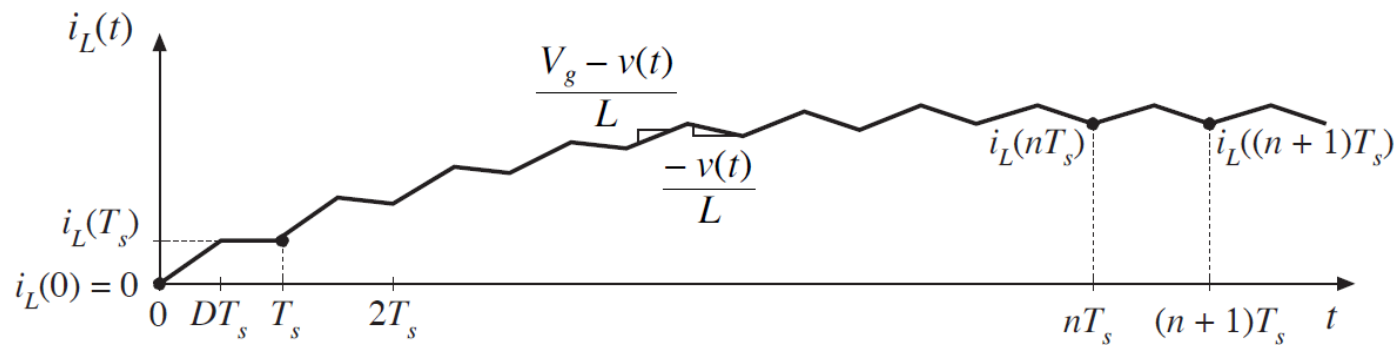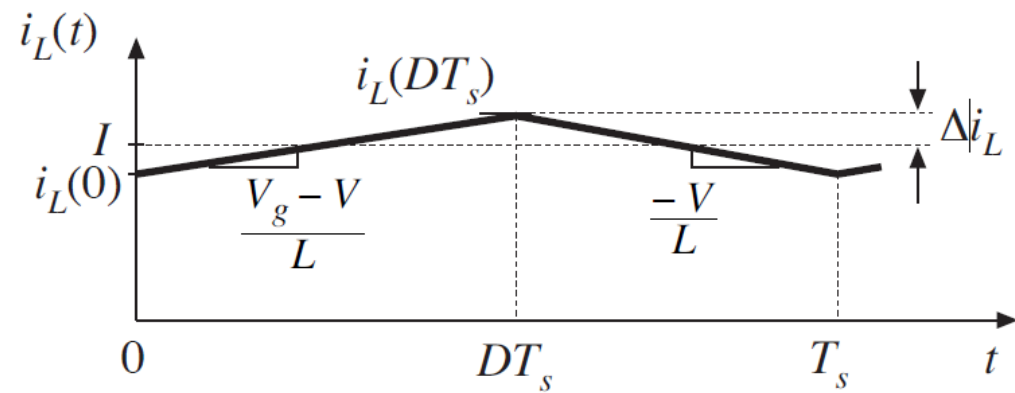

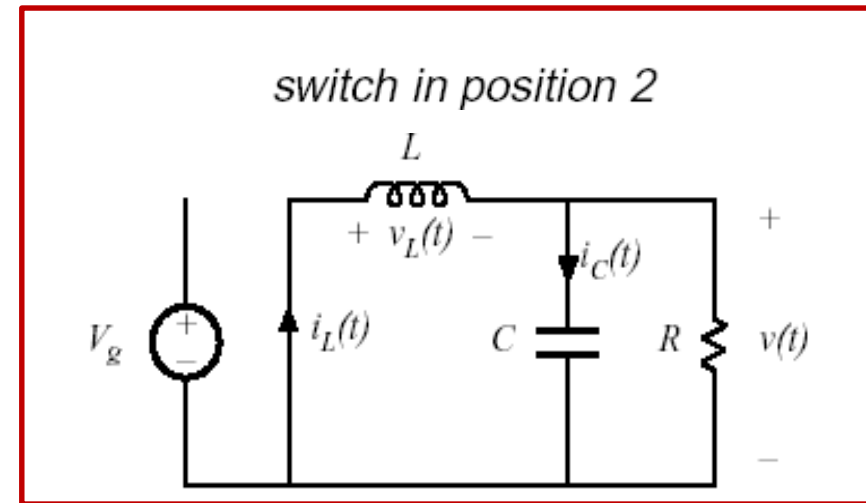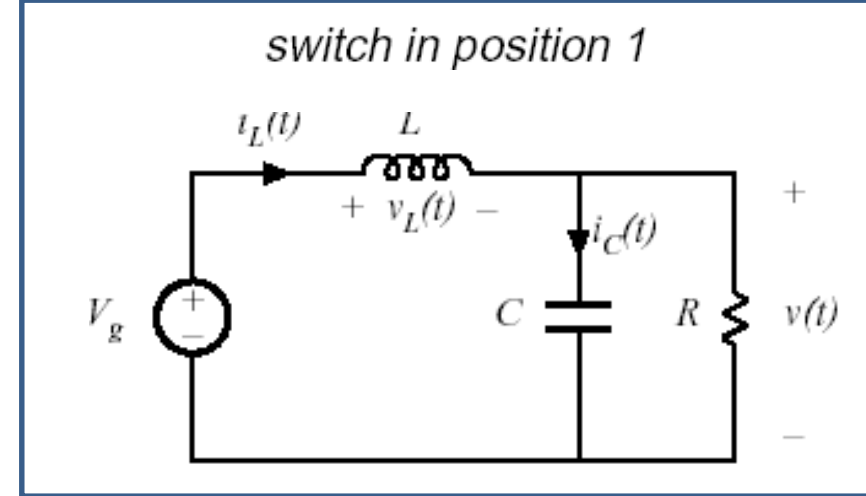When the converter operates in equilibrium: $i_L((n+1)T_s) = i_L(nT_s)$



Buck converter Analysis

When the switch is closed (on) :

$$v_L = V_g - V = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{V_g - V}{L}$$

Derivative of i_L is a positive constant.
Therefore i_L must increase linearly.

From Figure

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_g - V}{L}$$

$$(\Delta i_L)_{\text{closed}} = \left(\frac{V_g - V}{L} \right) \cdot DT$$


For switch opened,

$$v_L = -V = L \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{-V}{L}$$


$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{-V}{L}$$
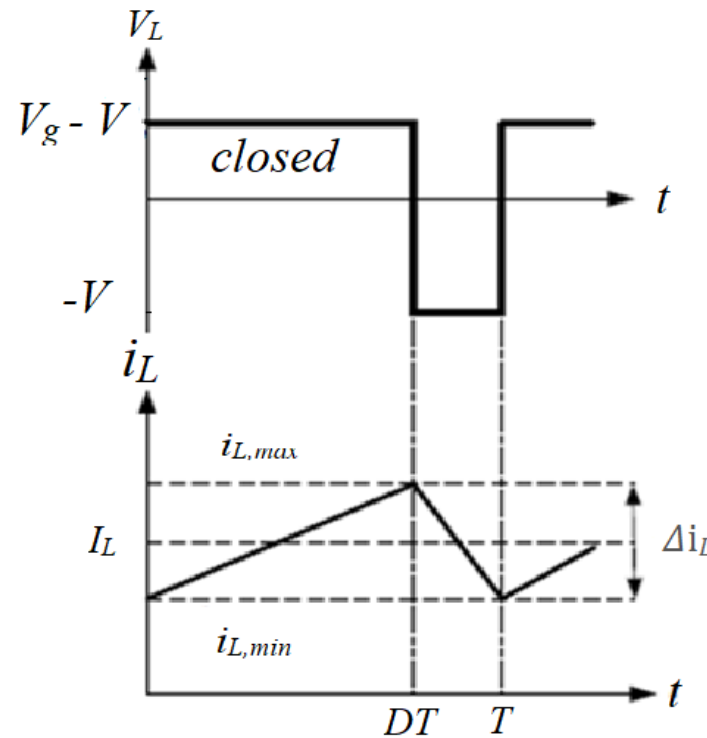
$$(\Delta i_L)_{\text{opened}} = \left(\frac{-V}{L} \right) \cdot (1-D)T$$



(change in i_L) = (slope)(length of subinterval)

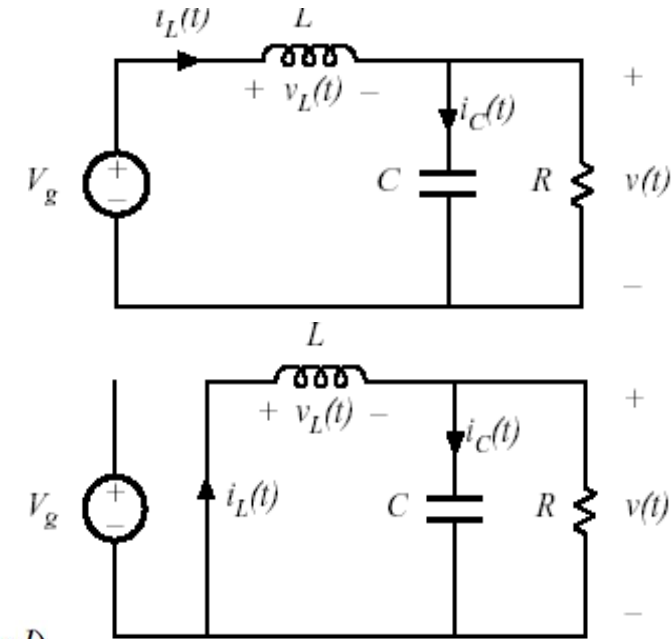Determination of inductor current ripple magnitude




Steady- state operation requires that i_L at the end of switching cycle is the same at the beginning of the next cycle. That is the change of i_L over one period is zero i.e :

$$(\Delta i_L)_{\text{closed}} + (\Delta i_L)_{\text{opened}} = 0$$


$$\left(\frac{V_g - V}{L} \right) \cdot DT_s - \left(\frac{-V}{L} \right) \cdot (1-D)T_s = 0$$

$$V = DV_g$$

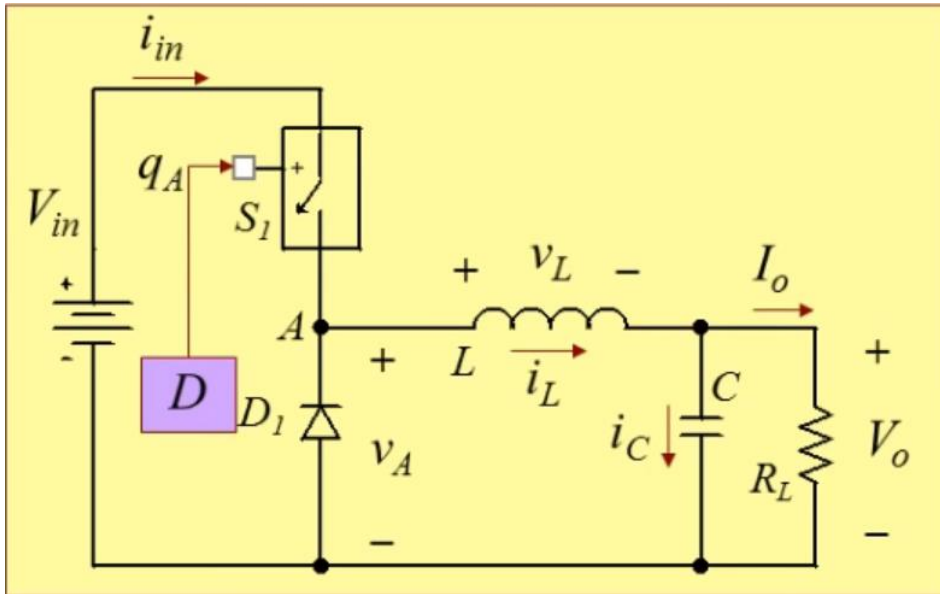

$$\frac{V_o}{V_{in}} = D$$

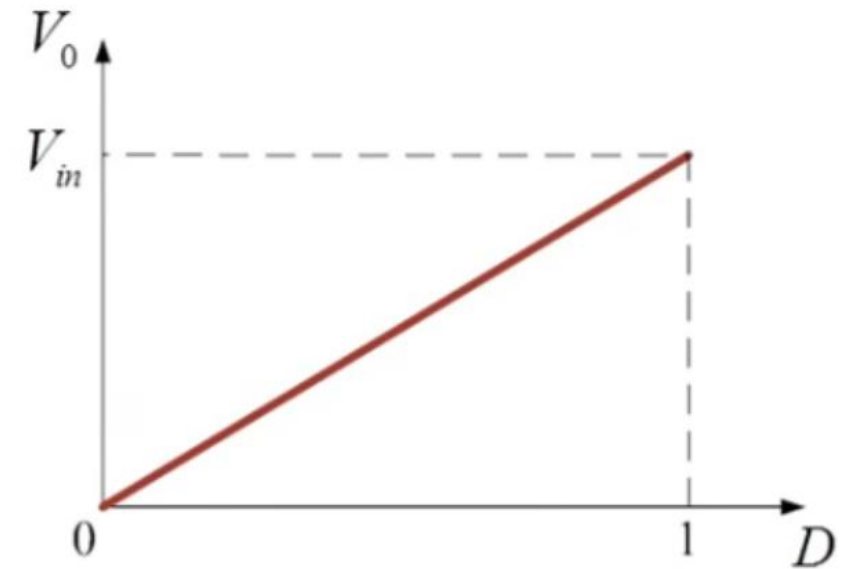Input-output
relationship for
Buck converter




Neglecting power losses, the input
power equals the output power.

$$P_d = P_o \Rightarrow V_d I_d = V_o I_o \Rightarrow \frac{I_o}{I_d} = \frac{V_d}{V_o} = \frac{1}{D}$$

Characteristics of inductors and capacitors


Inductor

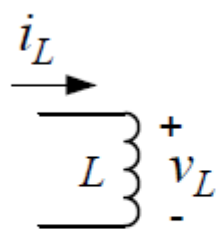

$$v_L(t) = L \frac{di_L(t)}{dt}$$



Capacitor

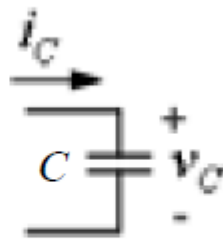

$$i_C(t) = C \frac{dv_C(t)}{dt}$$



Volt-sec balance in inductors

- The **average** (CCA) voltage across an inductor in **DC steady-state** is zero

$$\bar{v}_L = 0$$

Instantaneous v-i relationship for inductor

$$v_L(t) = L \frac{di_L(t)}{dt}; \quad i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau \quad \dots (1)$$

Substituting $t = t_0 + T_s$ in (1)

$$i_L(t_0 + T_s) = i_L(t_0) + \frac{1}{L} \int_{t_0}^{t_0 + T_s} v_L(\tau) d\tau \quad \dots (2)$$


In steady state

$$i_L(t_0 + T_s) = i_L(t_0) \quad \dots (3)$$

from (2) and (3)

$$\frac{1}{L} \int_{t_0}^{t_0 + T_s} v_L(t) dt = \frac{T_s}{L} \bar{v}_L = 0$$


$$\bar{v}_L = 0$$
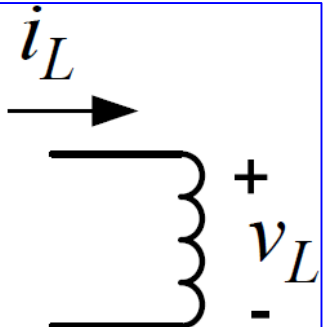
$$\bar{v}_L = L \frac{d\bar{i}_L}{dt} = 0$$

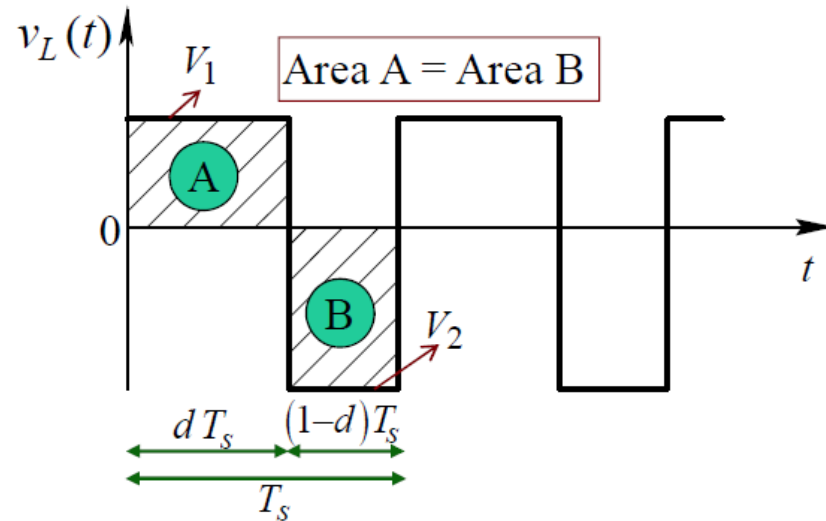
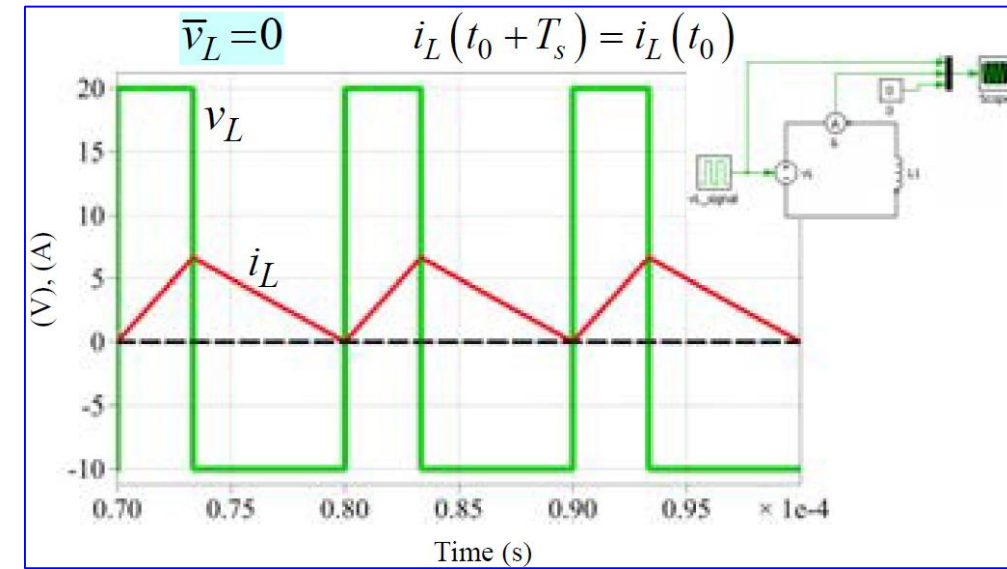
(since, \bar{i}_L should be constant in steady state)

Volt-sec balance in Inductors

$\bar{v}_L = 0$ does not imply that the inductor voltage is zero instantaneously, only the average over a complete period is zero




$$V_1 d + V_2 (1 - d) = 0$$




If volt-sec balance is violated

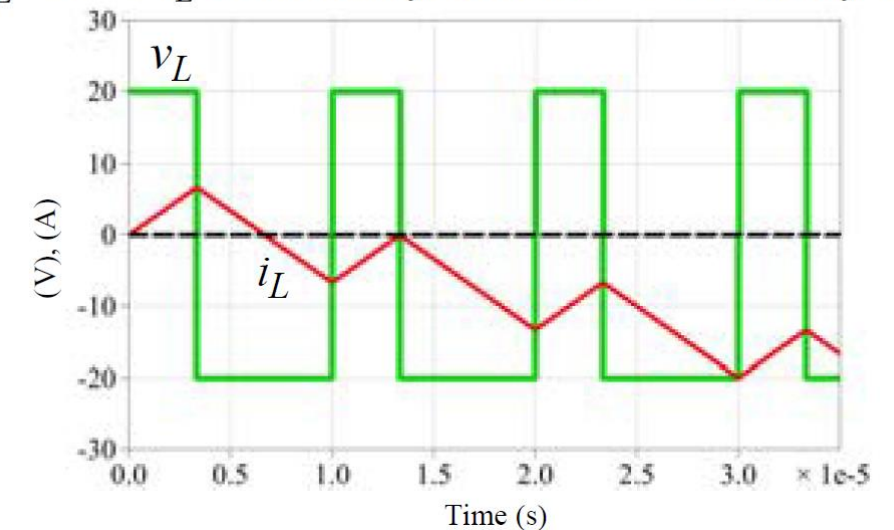$\bar{v}_L < 0 \Rightarrow \bar{i}_L$ continuously decreases \Rightarrow non-steady-state



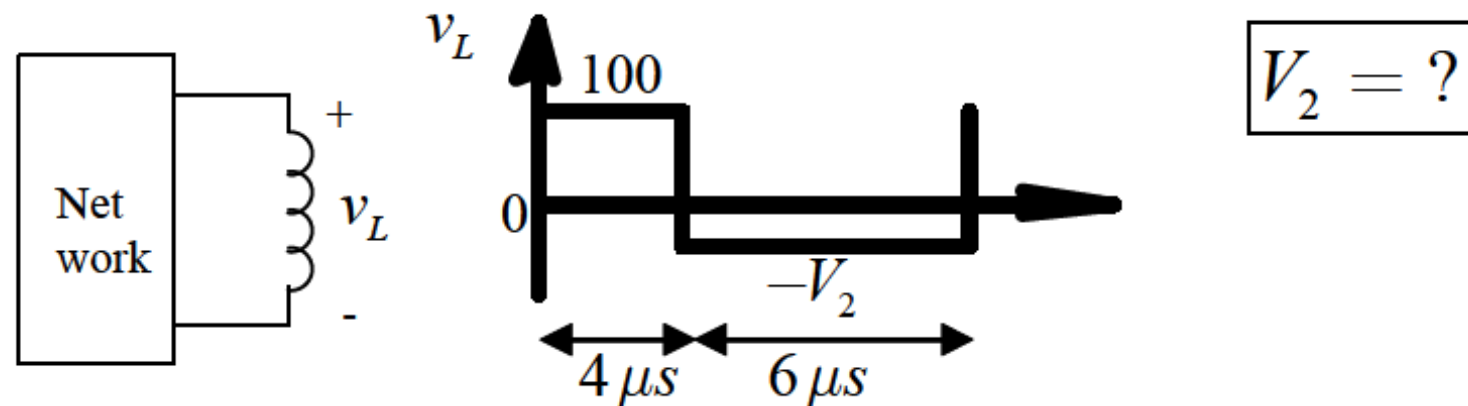
Example

Given that the circuit is in DC steady state, calculate V_2



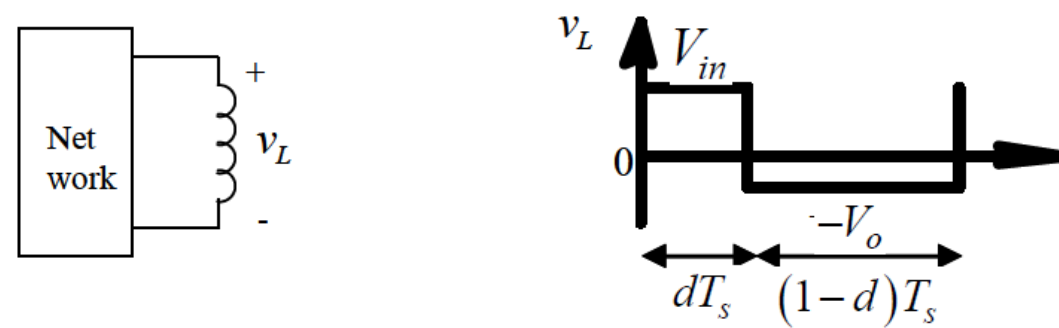
Example

Calculate the input-output relationship for a dc-dc converter, i.e, V_o / V_{in} , in terms of the duty ratio, d given the inductor voltage below



Inductor volt-second balance: Buck converter example

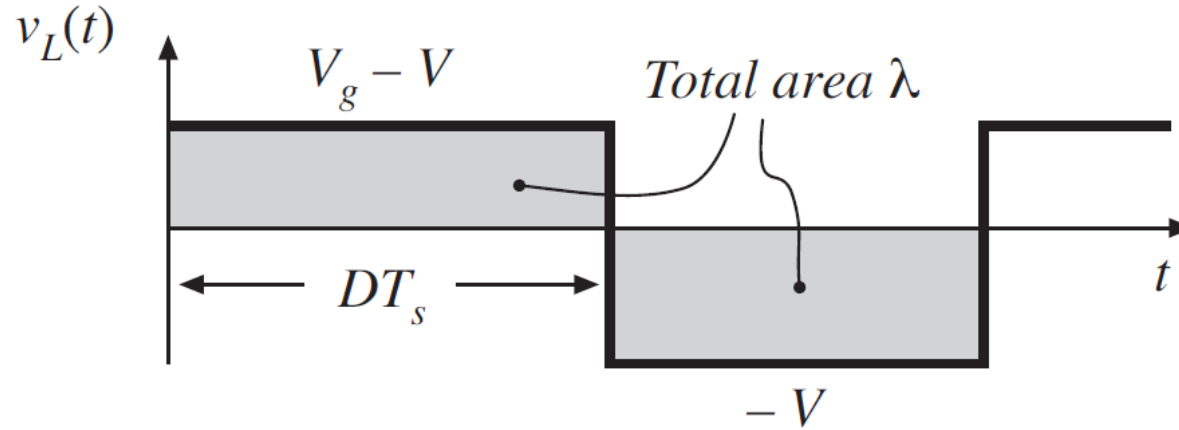Inductor voltage waveform,
previously derived:



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V :

$$0 = DV_g - (D + D')V = DV_g - V \quad \Rightarrow \quad V = DV_g$$

