

Department of Electrical Engineering  
 Indian Institute of Technology Bombay, Powai  
 EE238 : Power Engineering II  
 Solution to Assignment 1

1. Slip  $= \frac{50-1.5}{50} = 0.03$ . Synchronous speed  $N_s = \frac{120 \times 50}{8} = 750$  r.p.m.  
 Rotor speed  $N = (1 - s)N_s = 750 \times (1 - 0.03) = 727.5$  r.p.m.
2. Rotor frequency  $f_r = \frac{90}{60} = 1.5$  Hz. Rotor speed  $N = \frac{120 \times (50-1.5)}{6} = 970$  r.p.m.  
 Output power  $P = \omega_m \times T = \frac{2\pi \times 976}{60} \times 162 = 16455.7$  W.  
 B.H.P  $= \frac{16455.7}{746} = 22.1$   
 Mechanical power developed  $P_m = (162 + 13.5) \times 2\pi \frac{970}{60} = 17826.9$  W  
 Rotor Cu losses  $= \frac{P_m s}{1-s} = 550$  W where  $s = \frac{1.5}{50} = 0.03$   
 Input  $= 17826.98 + 550 + 750 = 19.2$  kW. Efficiency  $= 85.71$  %.
3. Assume star connected stator.  $V_{ph} = 500/\sqrt{3} = 289$  V.  $X_m = 289/36 = 8\Omega$ .  
 $R_c = V^2/P_c = 166.71\Omega$   
 Input Impedance  $= ((0.062 + \frac{0.062}{0.02}) + j(0.21 + 0.21)) || \frac{jX_m R_c}{jX_m + R_c} = 2.8 \angle 27.66^\circ$   
 Stator current  $I_s = \frac{288.86}{2.8 \angle 27.66^\circ} = 103.1 \angle -27.66^\circ$   
 Power factor  $= \cos(28^\circ) = 0.89$  lag  
 Rotor current  $= \frac{288.68}{(0.062+0.062/2)+j(0.21+0.21)} = 90.52 \angle -7.57^\circ$   
 Rotor input per phase  $= P_e = (90.52)^2 \frac{0.062}{0.02} = 25402.2$  W  
 Mech. power output per phase  $= P_m = 25402.2 \times (1 - 0.02) = 24894$  W  
 Output  $= 3 \times 24894 - 750 = 73932$  W = 99 h.p  
 Input power  $= \sqrt{3} \times 500 \times 103 \times 0.89 = 79465$  W  
 Efficiency  $= \frac{73932}{79465} = 93\%$

4. Output =  $50 \times 746 = 37300$  W. Input =  $37300/0.9 = 41444$  W. Total loss = 4144 W.

Let iron loss =  $W_i$ , Stator copper loss = Rotor copper loss =  $W_c$

No load loss = Iron loss + Windage + Friction loss.

$3 \times$  Mech. losses =  $W_i$  + Mech loss. Therefore, Mech loss =  $\frac{W_i}{2}$

Total loss = Stator Cu. loss + Rotor Cu. loss + Iron loss + Mech loss

$$4144 = W_i + W_i + W_i + W_i/2$$

Therefore  $W_i = 1184$  W

Rotor input = Stator input - Stator Cu loss - Iron loss = 39076 W

$$\% \text{ Slip} = \frac{\text{Rotor Cu loss}}{\text{Rotor Input}} = \frac{1184}{39076} \times 100 = 3.03\%$$

5. Synchronous speed = 1000 r.p.m. Slip = 0.05,  $P_m = 30 \times 746 = 22350$  W

$$\text{Rotor Cu loss} = \frac{22380 \times 0.05}{1-0.05} = 1178 \text{ W}$$

$$\text{Input} = \frac{22380}{1-0.05} + 2000 = 25.6 \text{ kW}$$

$$\% \text{ Efficiency} = \frac{(30-2) \times 746}{25600} \times 100 = 82\%$$

$$I_L = \frac{25600}{\sqrt{3} \times 550 \times 0.08} = 30.48 \text{ A}$$

Rotor frequency =  $s f_s = 0.05 \times 50 \times 60 = 150$  cycles per min.

6. Rotor resistance referred to stator =  $R'_r = 0.1 \times 1.75^2 = 0.306 \Omega$

Rotor reactance referred to stator =  $X'_r = 2.576 \Omega$

$$\text{Rotor current } I'_r = \frac{220/\sqrt{3}}{\sqrt{(\frac{0.306}{0.05})^2 + (2.576)^2}} = 18.72 \text{ A}$$

Total rotor input (airgap power) =  $3 I'^2_r \frac{R'_r}{s} = 6574.3$  W

Total torque =  $T = \frac{P_2}{2\pi n_s}$  where  $n_s = \frac{1500}{60}$  which gives T = 41.9 Nm

Rotor losses are not given, assume zero.

$$\text{HP} = \frac{6574 \times (1-0.05)}{746} = 8.37$$

Slip at max. torque =  $\frac{R'_r}{X'_r} = 0.111$

$$\text{Max torque} = \frac{3V^2}{4\pi n_s X'_r} = 56 \text{ Nm}$$

Speed at max. torque =  $N_s \times (1 - 0.111) = 1333$  rpm

7.  $s = \frac{1000-975}{1000} = 0.025$ . Rotor input =  $40 - 1 = 39$  kW.

Rotor Cu loss =  $s P_2 = 0.025 \times 39 \times 10^3 = 975$  W

$P_m = 39 \times (1 - 0.025) = 38.03$  kW. Shaft HP =  $\frac{38.03 \times 10^3}{0.746} = 48.3$

$$\% \text{ Efficiency} = \frac{36.025}{40} = 90\%$$

8.  $N_s = \frac{120 \times 50}{12} = 500$  r.p.m.

Total resistance of the machine =  $\frac{100 \times 10^3}{2 \times 250^2} = 0.53 \Omega$

Rotor equivalent resistance =  $0.27\Omega$

$$T = \frac{3I_r'^2 R_r'}{2\pi N_s \times s}$$

$$\text{Starting torque} = \frac{3I_r'^2 R_r'}{2\pi N_s} = 955 \text{ Nm}$$

$$9. s_{max} = \frac{750-630}{750} = 0.16, s_{max} = \frac{R_r'}{X_r'}$$

$$X_r' = 0.4375\Omega. s_{max} \text{ should be equal to 1 implies that } X_r' = R_r' + R_{ext}$$

$$R_{ext} = 0.37\Omega$$

$$10. \text{ Core loss} = 4.2 \text{ kW. No load p.f} = \frac{4200}{\sqrt{3} \times 460 \times 40} = 0.13$$

$$R_o = \frac{460/\sqrt{3}}{40 \times 0.13} = 51\Omega$$

$$X_m = R_o / \tan \theta = 6.7\Omega, R_{eq} = \frac{8 \times 10^3}{3 \times 140^2} = 0.136\Omega$$

$$Z_{eq} = \frac{100}{\sqrt{3} \times 140} = 0.412\Omega, X_{eq} = 0.389\Omega \text{ so } X_r' = 0.19\Omega$$

$$R_s = R_r' = 0.068\Omega, N_s = 900 \text{ rpm, } s = \frac{900-873}{900} = 0.03, \frac{R_r'}{s} = 2.27\Omega$$

$$Z_{eq} = [(2.27 + 0.068) + j0.389] || \frac{j51 \times 6.7}{51 + j6.7} = 2.04 \angle 27^\circ$$

$$I_1 = \frac{460}{\sqrt{3} \times 2.04 \angle 27^\circ} = 130 \angle -27^\circ \text{ A}$$

$$\text{Power input} = 3 \times \frac{460}{\sqrt{3}} \times 130 \times \cos -27^\circ = 92.42 \text{ kW}$$

$$\text{Stator Cu loss} = 3 \times 130^2 \times 0.068 = 3458 \text{ W, Air gap power} = 92.42 - 3.458 - 4.2 = 84.76 \text{ kW}$$

$$\text{Rotor Cu loss} = 84760 \times 0.03 = 2543 \text{ W, } P_m = 82217 \text{ W}$$

$$\text{Power output} = 82217 - 1000 = 81217 \text{ W.}$$

$$\% \text{Efficiency} = \frac{81217}{92420} = 87.8\%$$

$$11. \text{ Starting current taken from the supply with DOL} = \sqrt{3} \times \frac{500}{\sqrt{3}} = 248 \text{ A}$$

$$\text{Star-delta starting, phase voltage} = \frac{500}{\sqrt{3}}, \text{ starting current} = \frac{289}{3.5} = 82.5 \text{ A}$$

$$12. I_r' = \frac{230}{\sqrt{(\frac{1}{2})^2 + 1}}, \text{ Total } P_m = \frac{3(1-s) \times 230^2 s^2}{s(1+s^2)}$$

$$\text{Total load torque} = 33.68 \times \frac{N}{N_s} \text{ where } N = N_s(1-s)$$

$$\text{With mechanical loss neglected, } \frac{P_m}{2\pi N_s(1-s)/60} = \text{Total load torque}$$

$$\text{Solving for s gives, } s = 0.063 \text{ and } N = 3000(1-s) = 2810 \text{ rpm}$$

$$13. \text{ kVA} = 15, \text{ p.f} = 0.6, \sin \phi = 0.8$$

$$\text{Real power} = 9 \text{ kW, Reactive power} = 12 \text{ kVAR}$$

$$\text{Improvement of power factor leaves } P \text{ unchanged. } Q \text{ reduces to } Q_1.$$

$$\text{Reduction in } Q = 12 - \frac{9 \times 0.6}{0.8} = 5.25 \text{ kVAR}$$

Per phase reduction in  $Q = \frac{5.25}{3} = 1750$  VAR  
 $\frac{V^2}{X_c} = 1750$  with  $V = 230\text{V}$ , value of  $C$  is  $105\mu\text{F}$