

EE 238

Power Engineering - II

Power Electronics




Lecture 5

Instructor: Prof. Anshuman Shukla


Email: ashukla@ee.iitb.ac.in

Constant switching frequency

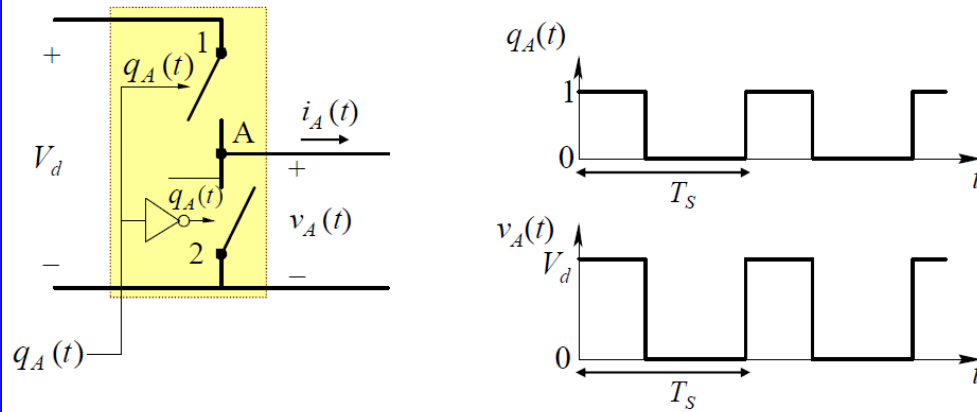


Example:
Switching frequency, $f_s = 200 \text{ kHz}$
↓
Period, $T_s = 1/f_s = 5 \text{ us}$

Pulse width modulation

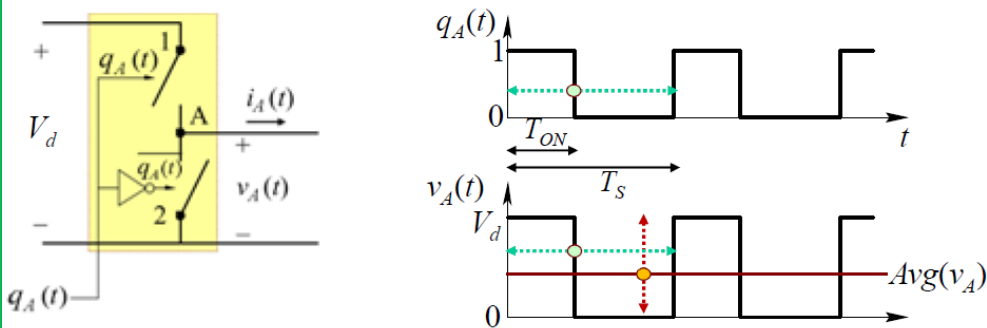

- PWM: Control of average (CCA) quantity by controlling (modulating) the pulse width in a switching cycle (duty ratio control)
- Normally constant switching frequency

Duty ratio

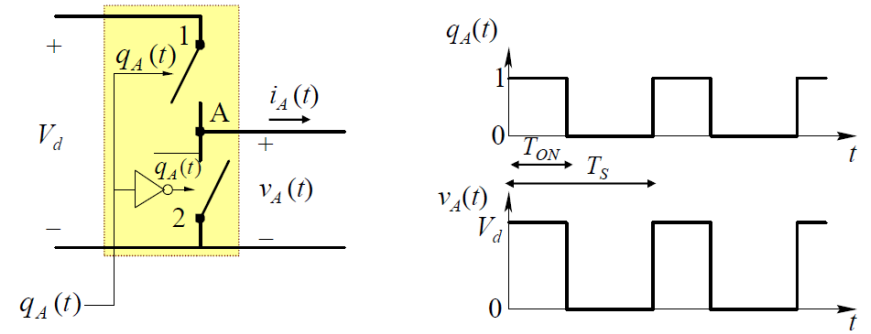

Example:
Frequency, $f_s = 200 \text{ kHz}$
Period, $T_s = 1/f_s = 5 \text{ us}$

Given $T_{ON} = 2 \text{ us}$
 $d = 0.4$



• T_{ON} : duration for which $q_A = 1$ in T_s

$$\text{duty ratio, } d_A = \frac{T_{ON}}{T_s}$$


• Duty ratio is the main control variable

PWM example



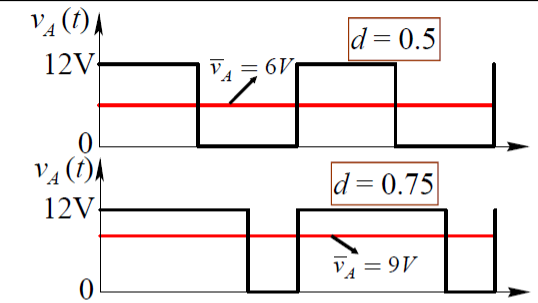
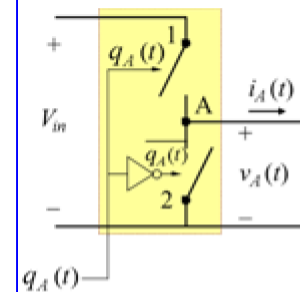
Different output voltages with a fixed input



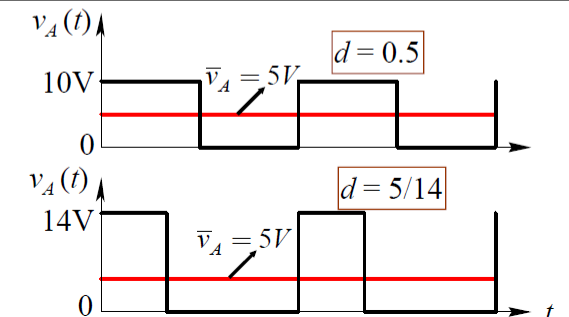Constant output voltage with varying input



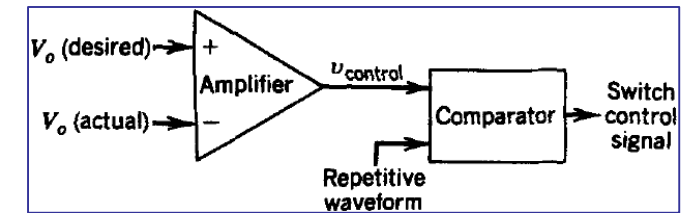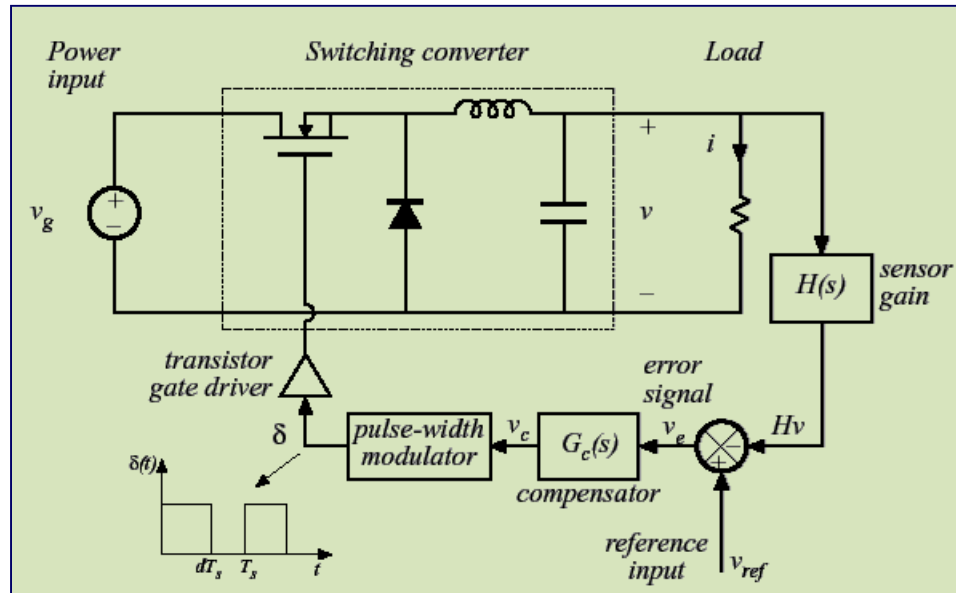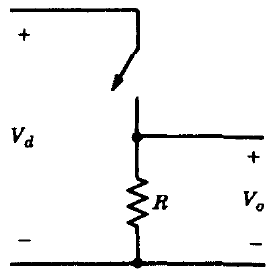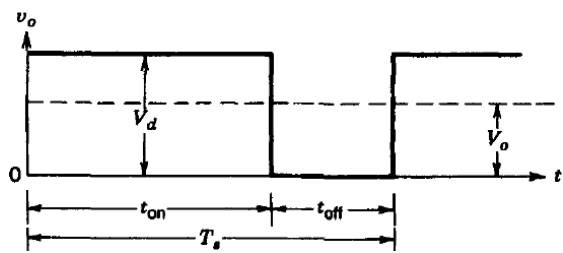
CONTROL OF dc-dc CONVERTERS: PWM Implementation



$$D = \frac{t_{on}}{T_s} = \frac{v_{\text{control}}}{\hat{V}_{st}}$$

PWM switching:


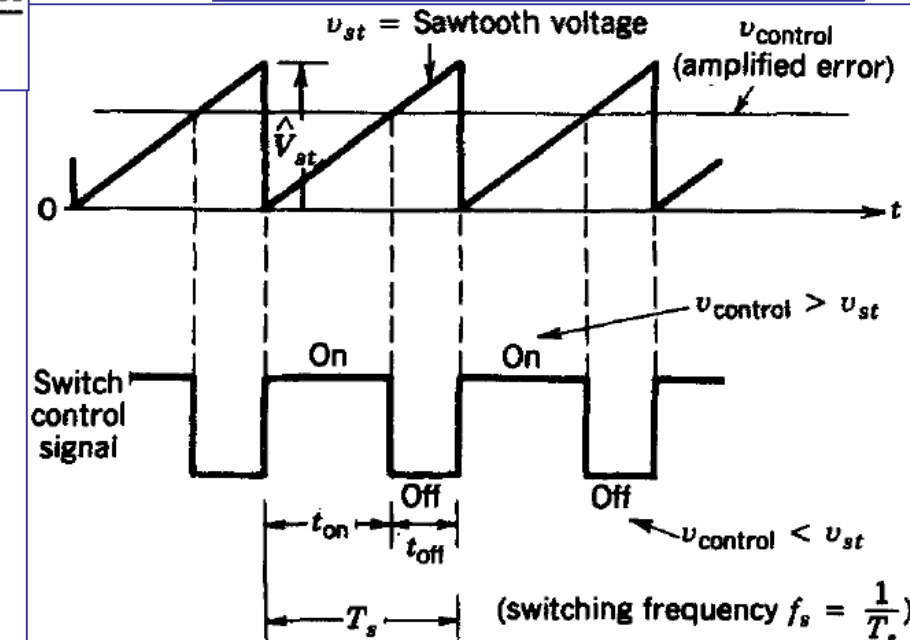
- the switch control signal is generated by comparing a signal-level control voltage v_{control} , with a repetitive waveform.
- v_{control} is obtained by amplifying the error.
- The frequency of the repetitive waveform with a constant peak establishes f .
- f is chosen to be in a few kilohertz to a few hundred kilohertz range.



A CHOPPER

Assuming ideal switch, constant V_d , and a purely resistive load R .

The average output voltage:

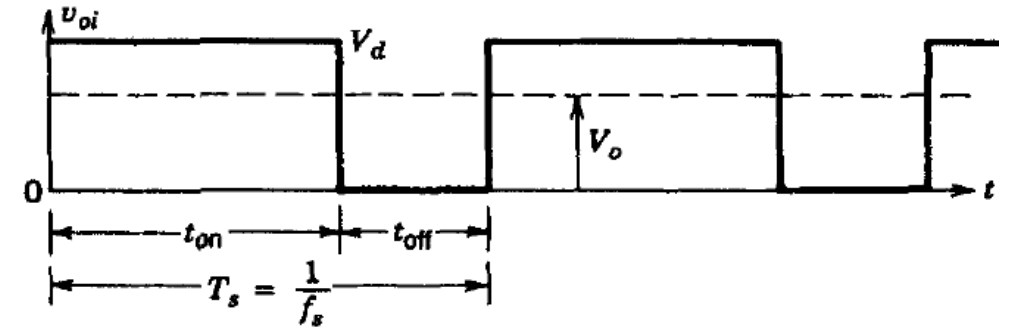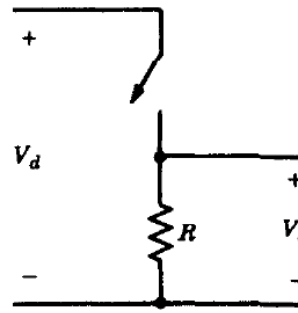

IMP
Slide

$$V_o = \frac{1}{T_s} \int_0^{T_s} v_o(t) dt = \frac{1}{T_s} \left(\int_0^{t_{on}} V_d dt + \int_{t_{on}}^{T_s} 0 dt \right) = \frac{t_{on}}{T_s} V_d = DV_d$$



$$D = \frac{t_{on}}{T_s} = \frac{v_{control}}{\hat{V}_{st}}$$

$$V_o = \frac{V_d}{\hat{V}_{st}} v_{control} = k v_{control}$$



$$k = \frac{V_d}{\hat{V}_{st}} = \text{constant}$$

By varying D of the switch, V_o can be controlled.

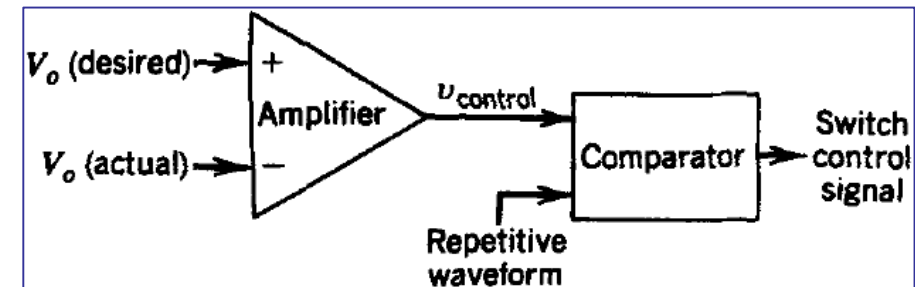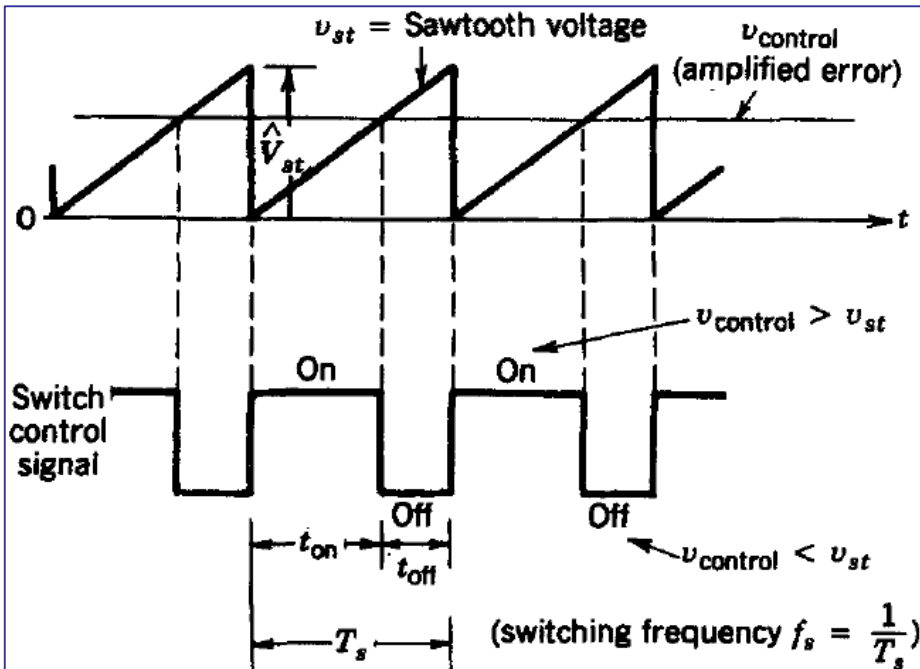The average output volt. V_o varies linearly with the $v_{control}$.




A CHOPPER

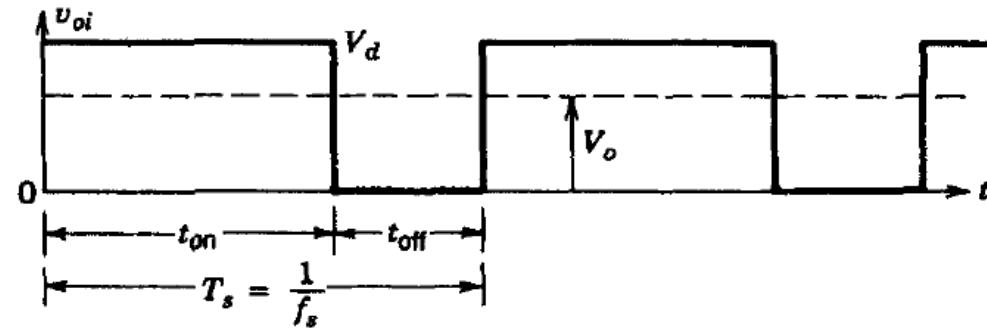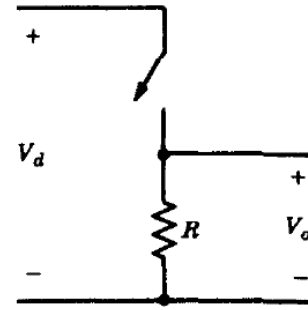

In actual applications, the foregoing circuit has two drawbacks:

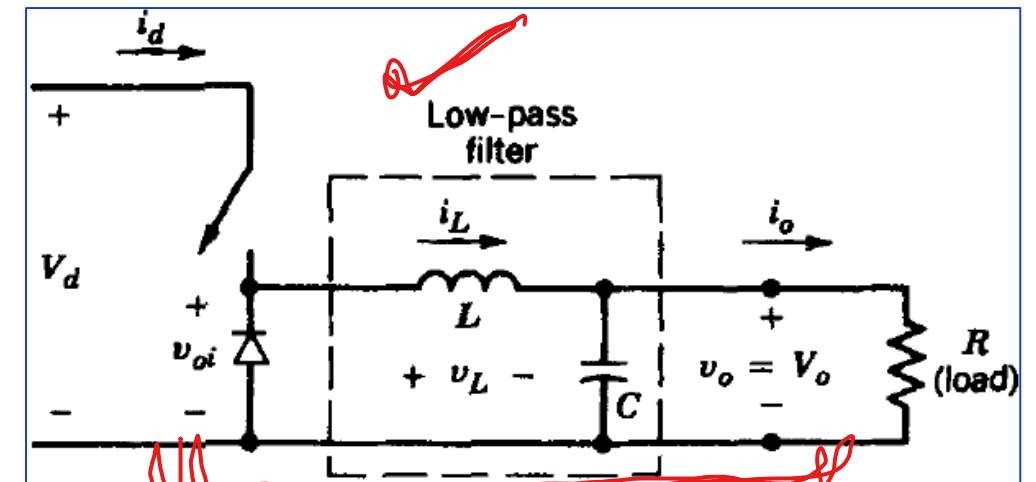
- (1) In practice the load would be inductive. Even with a resistive load, there would always be certain associated stray inductance. This means that the switch would have to absorb (or dissipate) the inductive energy and therefore it may be destroyed.
- (2) The output voltage fluctuates between zero and V_d , which is not acceptable in most applications.

- ✓ The problem of stored inductive energy is overcome by using a diode.
- ✓ The output voltage fluctuations are very much diminished by using a low-pass filter, consisting of C & L.



Step-down converter example

CCA

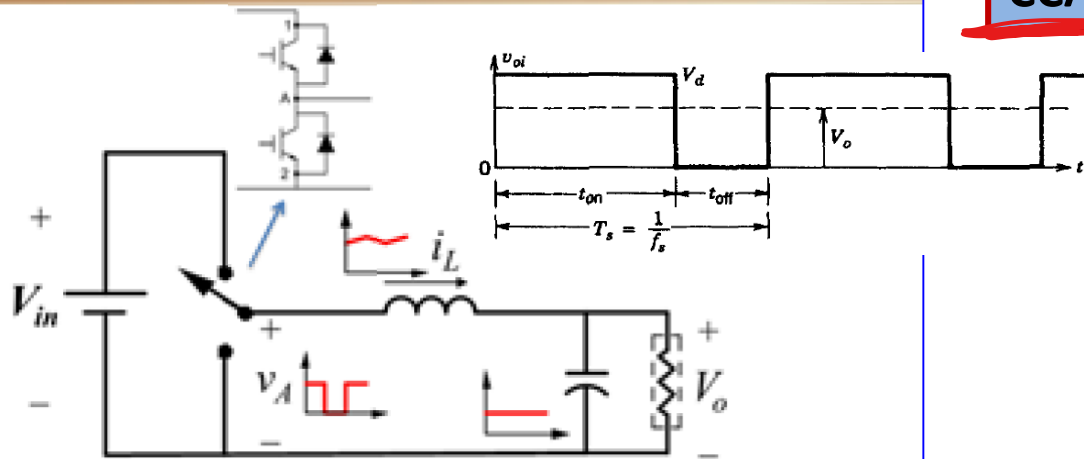

- By controlling the ON/OFF durations of the switches, we control the **periodic average** of bi-positional switch output, and in turn the average values of other quantities
- Most quantities have switching waveforms or high-frequency content, but for most control purposes we are only interested in average value


Cycle-by-cycle averaging (CCA)

- Average over a switching period referred to as **cycle-by-cycle average (CCA)**
- Control objectives achieved essentially by **controlling the CCA value** of different quantities
- Average models, steady-state analysis & controller design use CCA quantities

- Average over a switching period


- CCA values denoted by a bar (-) on top, like \bar{v}_{AN} , \bar{i}_d
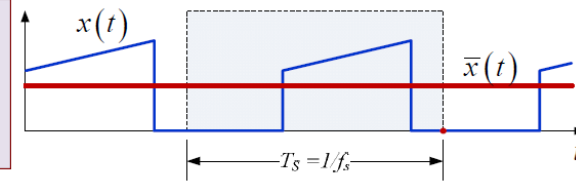
$$\bar{x}(t) = \frac{1}{T_s} \int_{t-T_s}^t x(\tau) d\tau$$



- CCA quantities can be time varying

CCA value of q_A and v_{AN}

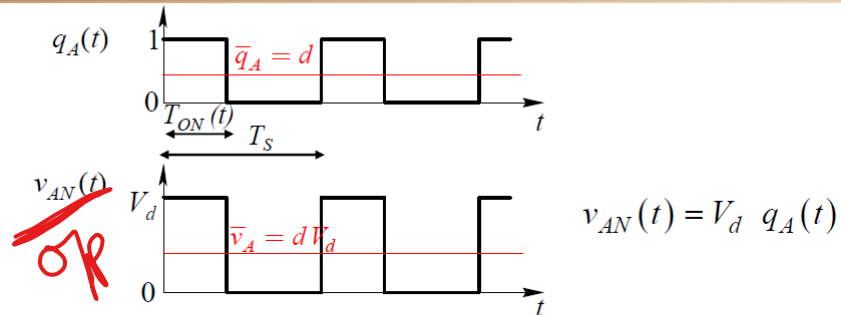

$$v_{AN}(t) = V_d q_A(t)$$

Some properties of CCA

- Just like instantaneous quantities, KCL and KVL apply for CCA quantities too

KCL	KVL
$\sum_k \bar{i}_k = 0$	$\sum_k \bar{v}_k = 0$
At a node	Around a loop

Instantaneous

$$v(t) = R i(t)$$

$$v_L(t) = L \frac{d}{dt} i_L(t)$$

$$i_C(t) = C \frac{d}{dt} v_C(t)$$

CCA

$$\bar{v}(t) = R \bar{i}(t)$$

$$\bar{v}_L(t) = L \frac{d}{dt} \bar{i}_L(t)$$

$$\bar{i}_C(t) = C \frac{d}{dt} \bar{v}_C(t)$$

Integrating both sides and dividing by T_s

$$\frac{1}{T_s} \int_{t-T_s}^t i_1(t) dt + \frac{1}{T_s} \int_{t-T_s}^t i_2(t) dt + \frac{1}{T_s} \int_{t-T_s}^t i_3(t) dt = 0$$


$$\therefore \bar{i}_1 + \bar{i}_2 + \bar{i}_3 = 0$$

- CCA can be used in both **steady-state and transient analysis**

- Simulations based on CCA models are sometimes **orders of magnitude faster**
- Since the process of CCA removes the switching frequency component and its harmonics, phasor analysis can be applied (at fundamental frequency) in sinusoidal applications
- CCA analysis cannot be used for studying switching frequency ripple, switch stress and other high frequency effects

STEP-DOWN (BUCK) CONVERTER

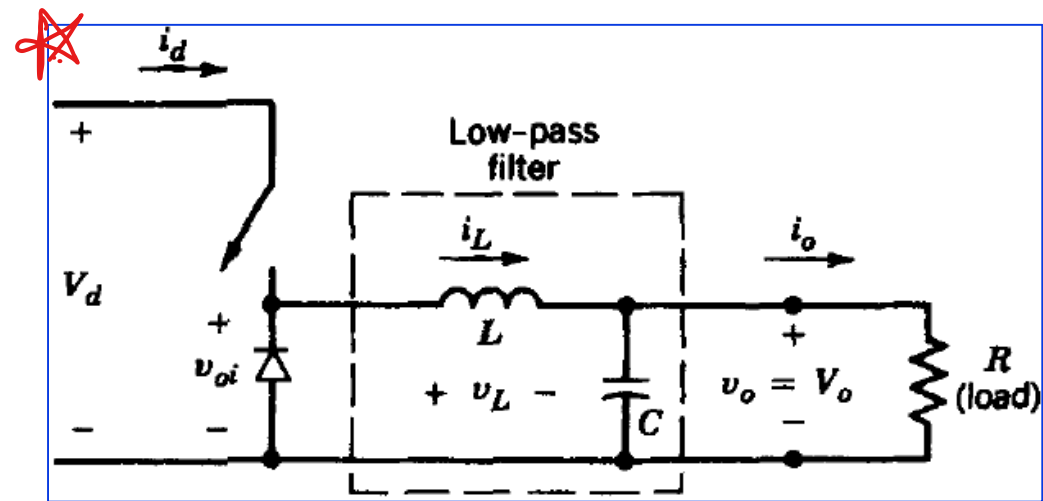- The converters are analyzed in steady state.
- The switches are treated as being ideal, and the losses in L and C are neglected.



- A small filter is treated as an integral part in the output stage of the converter
 - The output is assumed to supply a load that can be represented by an equivalent resistance. A dc motor load (the other application of these converters) can be represented by a dc voltage in series with the motor winding resistance and inductance.
-
- The dc input voltage to the converters is assumed to have zero internal impedance. It could be a battery source.
 - However, in most cases, the input is a diode rectified ac line voltage with a large filter capacitance to provide a low internal impedance and a low-ripple dc voltage source.

BUCK CONVERTER APPLICATIONS

POL Converter for PCs and Laptops



Solar Chargers



USB On-The-Go



Battery Chargers




Quadcopters





The buck is widely used in low power consumption small electronics to step-down from 24/12V down to 5V. They are sold as a small finish product chip for well less than US\$1 having about 95% efficiency.


STEP-DOWN (BUCK) CONVERTER

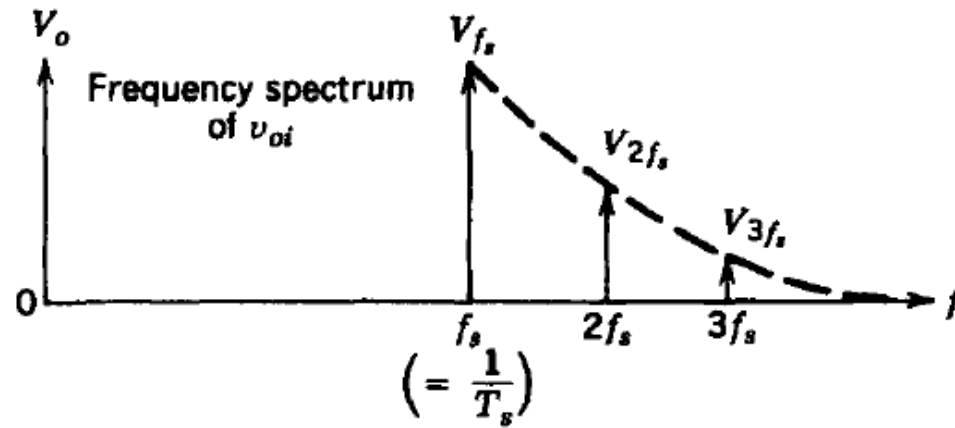

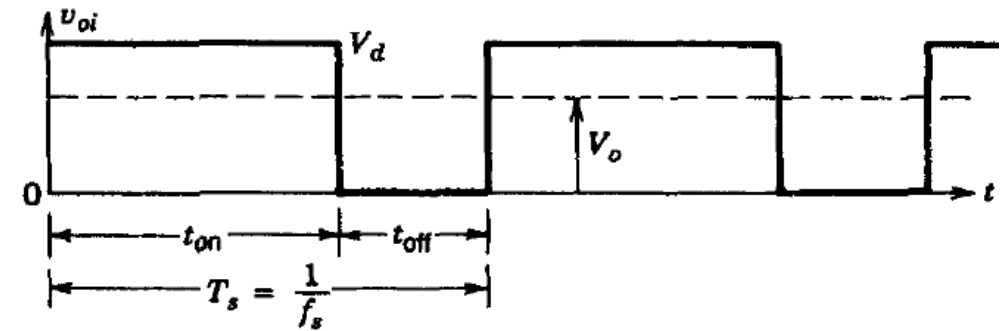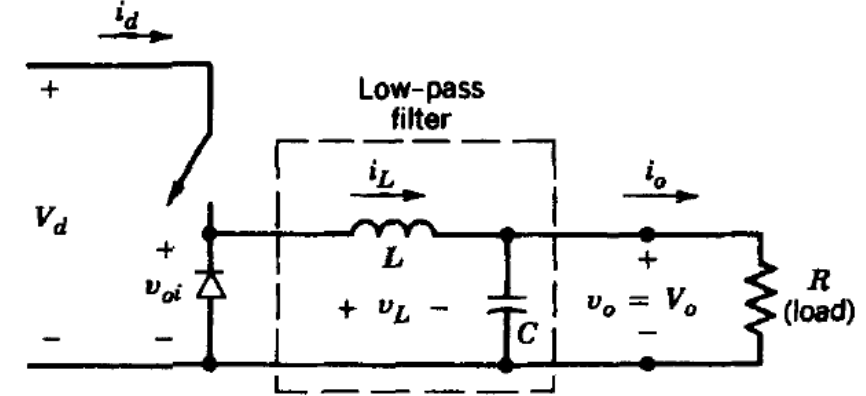A dc component V_o , and the harmonics at the switching frequency f_s and its multiples,



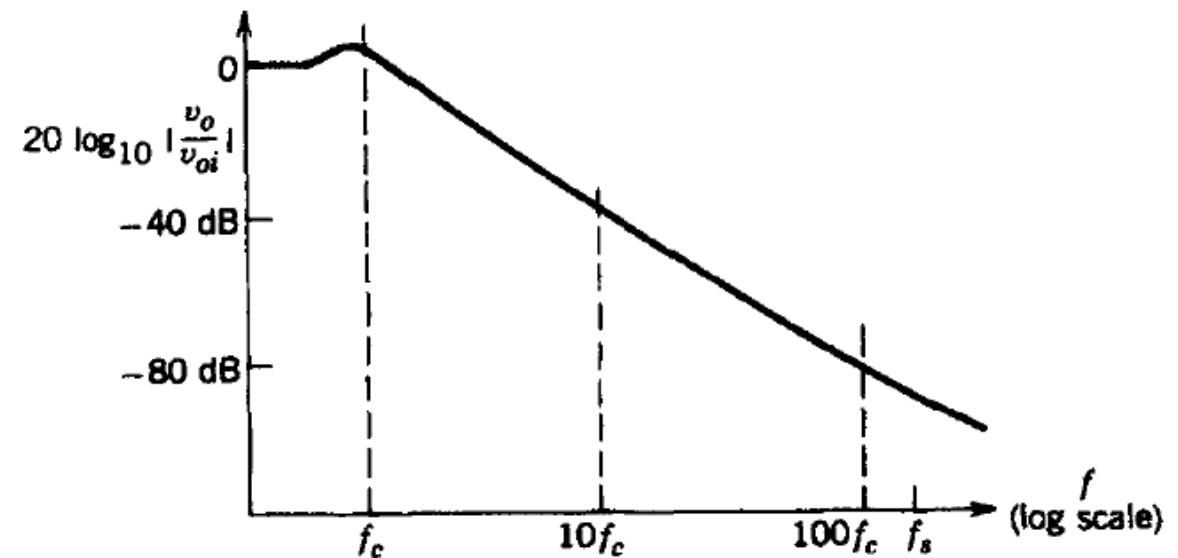The corner frequency f_c of the low-pass filter is selected to be much lower than the switching frequency, thus essentially eliminating the switching frequency ripple in the output voltage.



The low-pass filter characteristic

Thought process in analyzing basic DC/DC converters



✦ Basic operation principle (qualitative analysis)

- How does current flow during different switching states
- How is energy transferred during different switching states

✦ Verification of small ripple approximation

✦ Derivation of inductor voltage waveform during different switching states

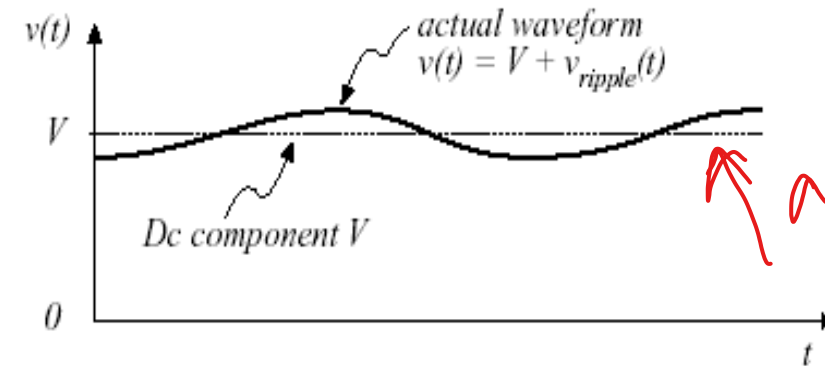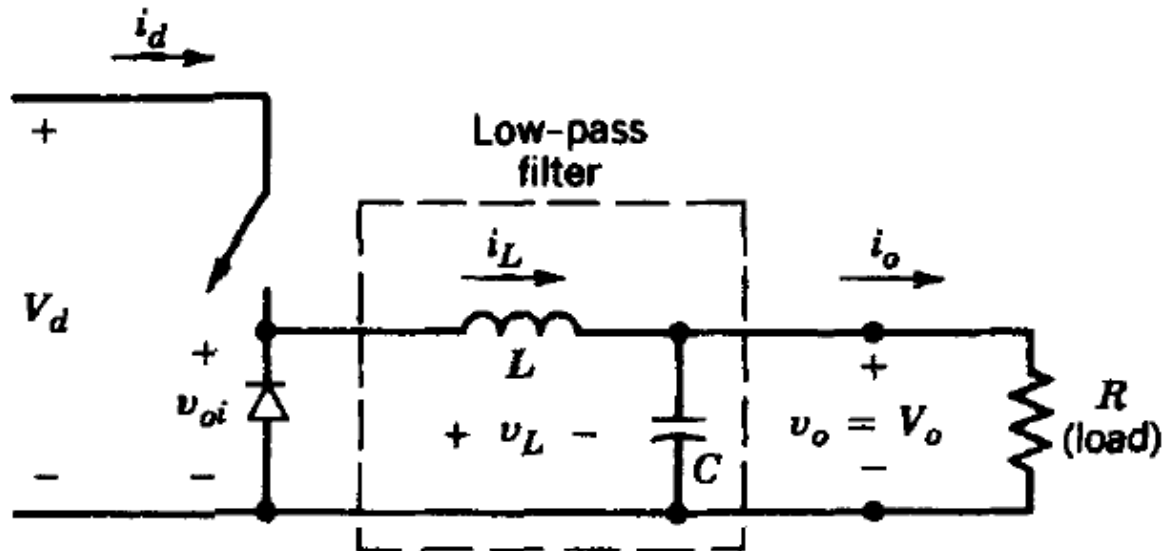✦ Quantitative analysis according to inductor volt-second balance or capacitor charge balance




assumed negligible

$$|v_{ripple}| \ll V$$

$$v(t) \approx V$$



$$\frac{dI}{dt} = \frac{V}{L}$$

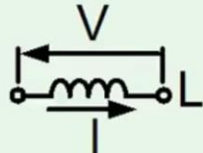







In most Power Electronics cases
V=constant over time period of interest

$$\frac{\Delta I}{\Delta t} = \frac{V}{L};$$

$$\Delta I = \frac{V}{L} \Delta t;$$

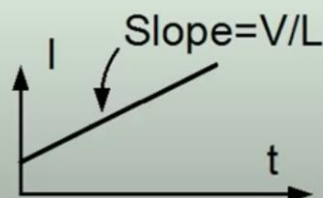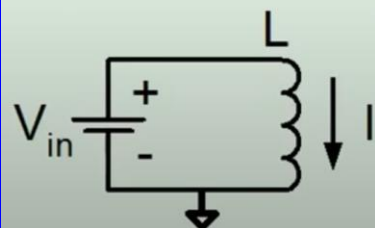


Inductor in Switched-mode Converters

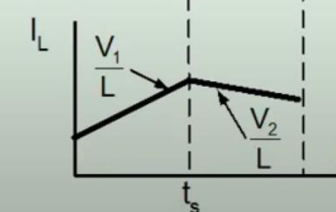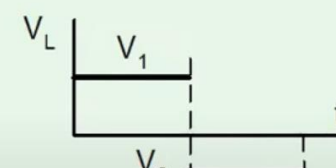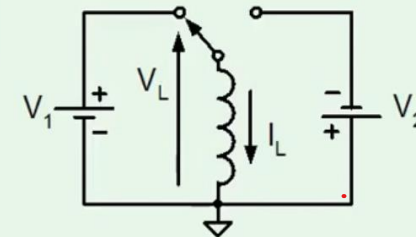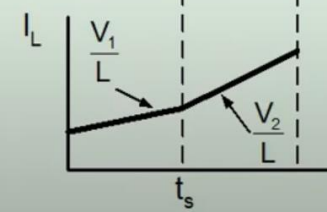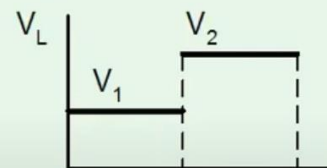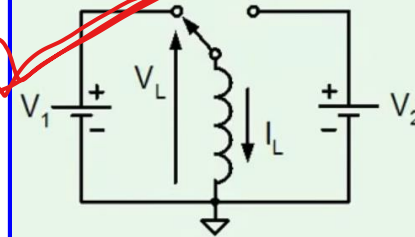

Average Signals

Most important equation in Power Electronics: $\frac{dI}{dt} = \frac{V}{L}$

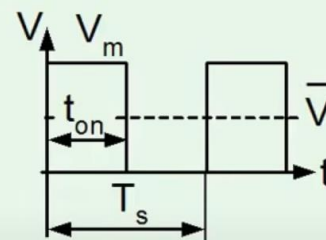
Correct for average too: $\frac{d\bar{I}}{dt} = \frac{\bar{V}}{L}$









$$\bar{X} = \frac{1}{T} \int_0^T X dt$$

\bar{X} - average
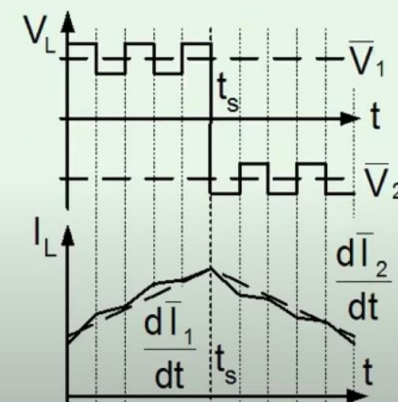
$$\bar{V} = \frac{V_m \cdot t_{on}}{T_s} = V_m D_{on}$$



real case

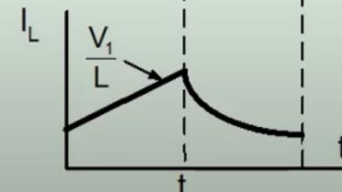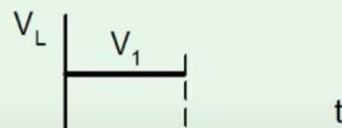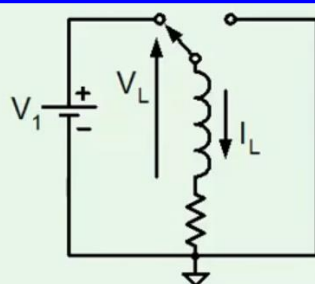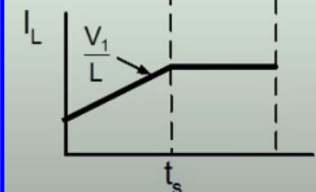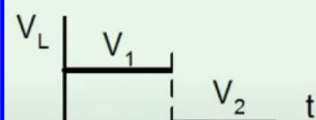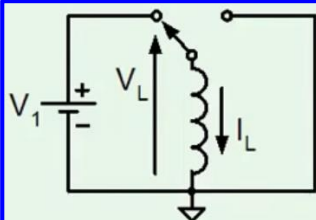

Implication

For any practical system in steady state:
Average voltage on inductor $\bar{V}_L = 0$

Proof:

If $\bar{V}_L \neq 0$ then $\bar{I}_L \rightarrow \infty$




That is:

System must be designed such that:

$$\bar{V}_L = 0$$

Inductor in Switched- mode Converters


Inductor current interruption

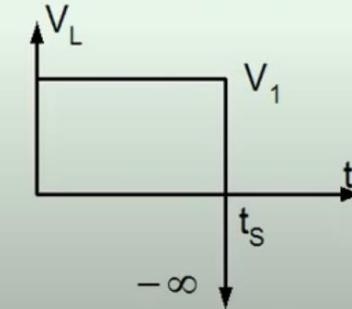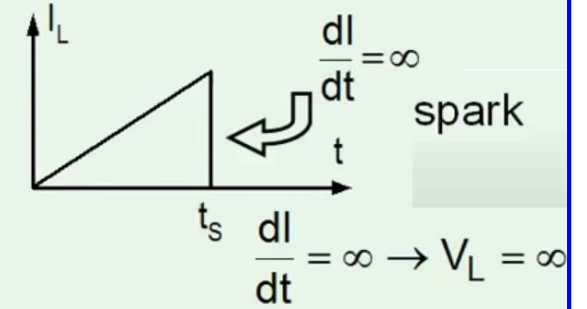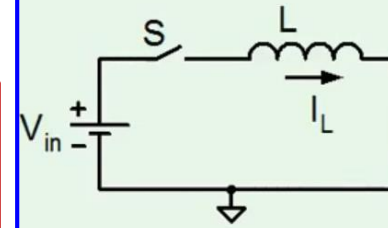

Inductor current interruption

What is the polarity?

The imaginary resistor method

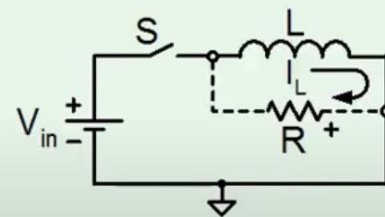

Current continuity

