

EE 238

Power Engineering - II

Power Electronics




Lecture 14

Instructor: Prof. Anshuman Shukla

Email: ashukla@ee.iitb.ac.in

Conversion of electric power

Power Electronics Converters

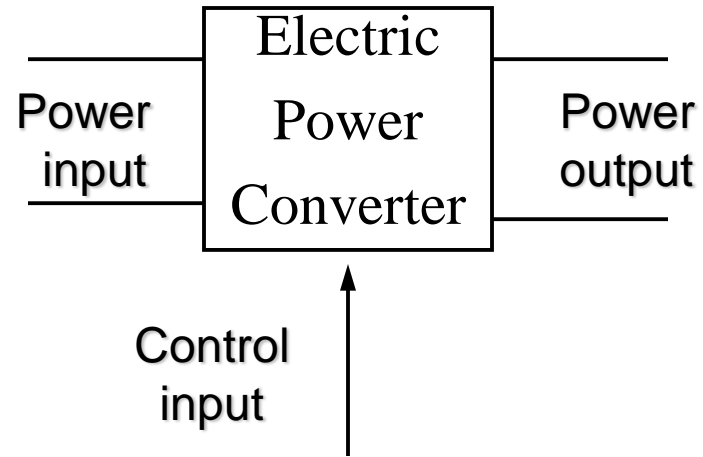

Other names for electric power converter:

- Power converter
- Converter
- Switching converter
- Power electronic circuit
- Power electronic converter

| Two types of electric power | Changeable properties in conversion |
|-----------------------------|--|
| DC(Direct Current) | Magnitude |
| AC (Alternating Current) | Frequency, magnitude, number of phases |


Inverters Classification

Voltage Source Inverter

The input is from a dc source and the ac output functions as a voltage source.


The input dc voltage may be from the rectified output of an ac power supply, in which case it is called a 'dc link' inverter.

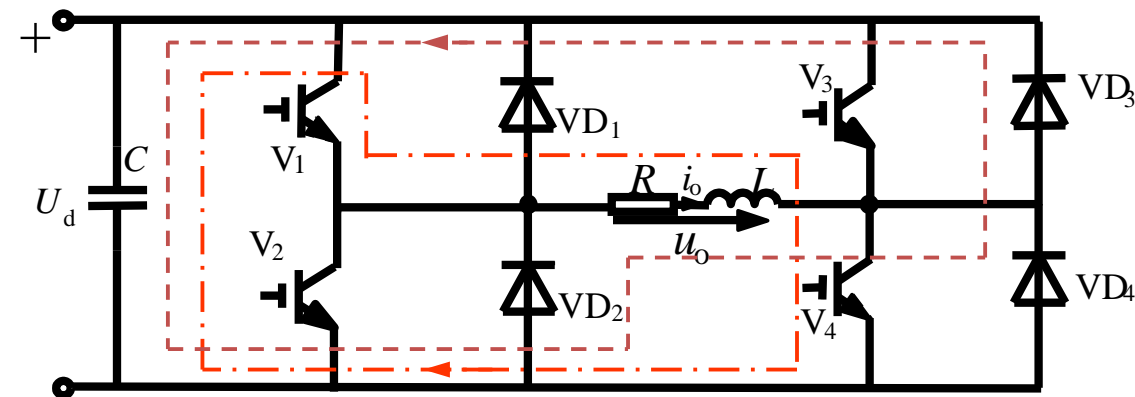Alternatively, the input dc may be from an independent source such as a battery.



Full-bridge Inverter: Most commonly used topology.

Current Source Inverter

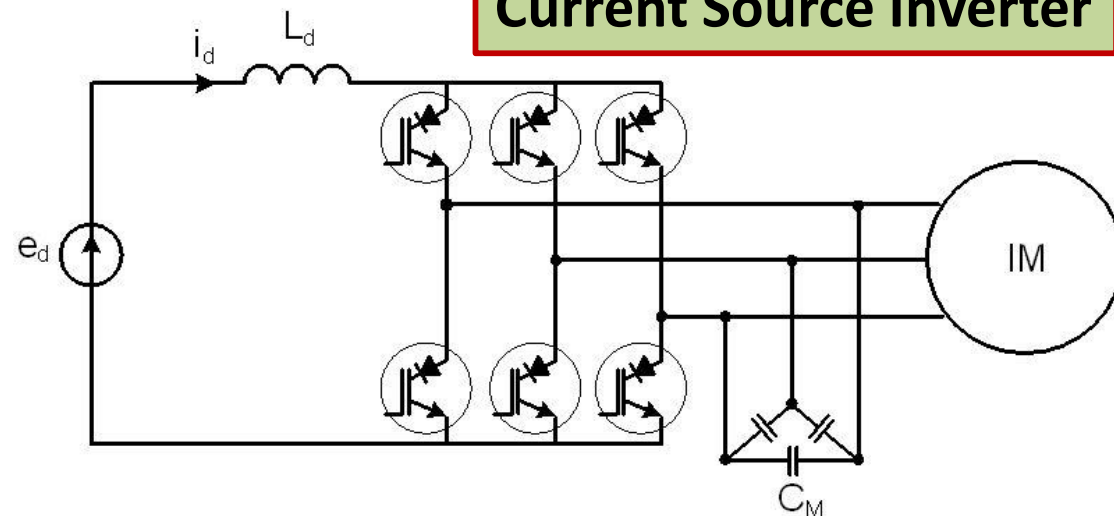

On the output side, CSI functions as an ac current source.

This is also a dc link inverter but in this case the dc link functions like a dc current source.

VSI: modulation methods


1. *Pulse-width-modulated inverters*

- V_{dc} is essentially constant in magnitude.
- PWM is used to control the magnitude and frequency of the ac output voltages.
- There are various PWM schemes to shape the output ac voltages to be as close to a sine wave as possible.

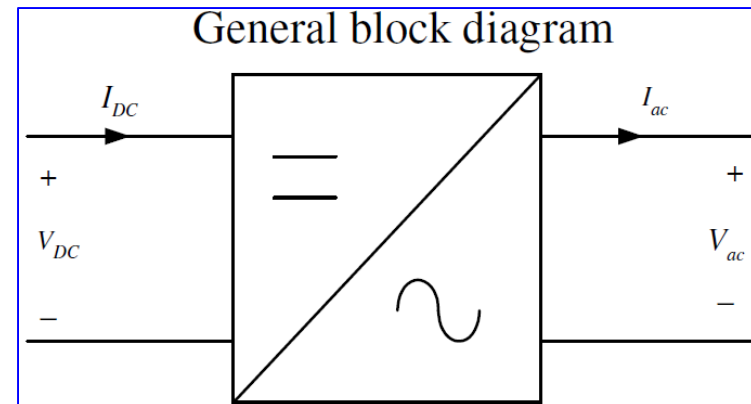2. *Square-wave inverters.*



- V_{dc} is controlled in order to control the magnitude of the output ac voltage.
- The inverter has to control only the frequency of the output voltage.
- The output ac voltage has a waveform similar to a square wave.

Inverters can be of single-phase or three-phase configurations.




BASIC CONCEPTS OF SWITCH-MODE INVERTERS

With filters and lagging load:

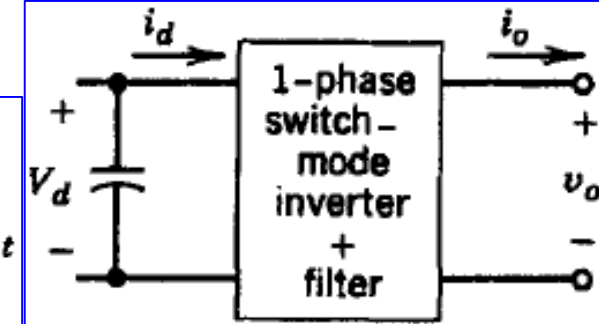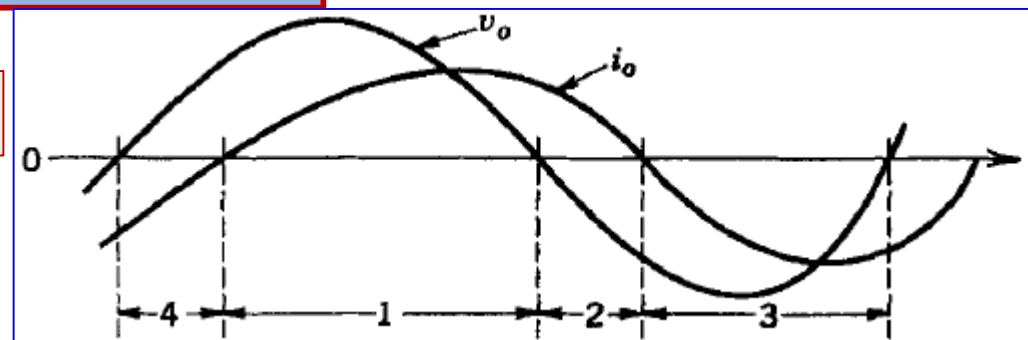


During intervals 1 & 3, the instantaneous power flow $po (=v_o i_o)$ is from the dc to ac side, corresponding to an inverter mode of operation.

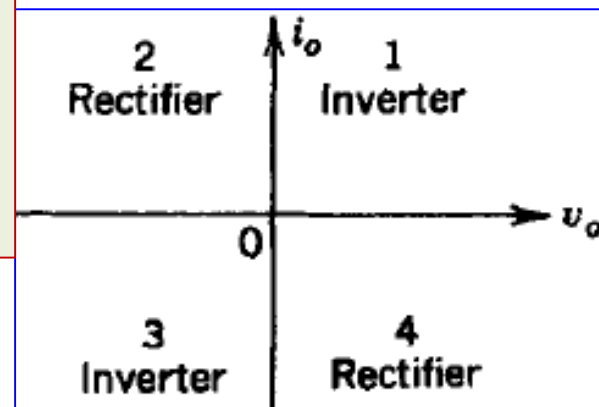In contrast, v_o and i_o are of opposite signs during intervals 2 and 4, and therefore po flows from the ac to dc side, corresponding to a rectifier mode of operation.




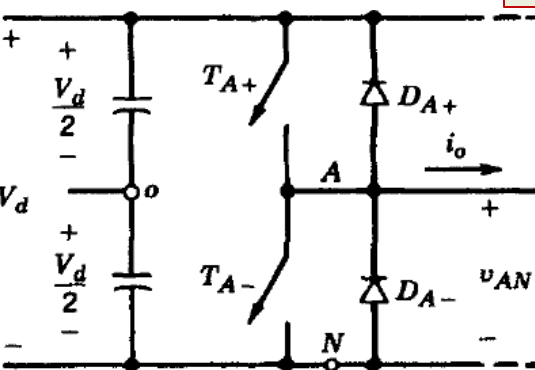Therefore, the inverter must be capable of operating in all four quadrants of the i_o - v_o plane during each cycle of the ac output.




Basic
Building
Block

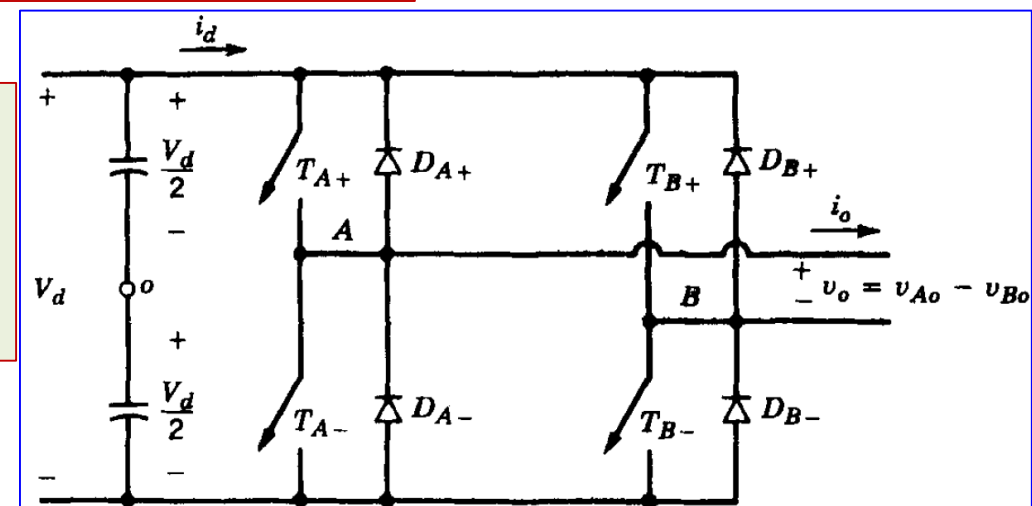The full-bridge
converter meets the
switch-mode inverter
requirements.



Most of the inverter topologies are derived from the one-leg converter.


THE HALF-BRIDGE INVERTER

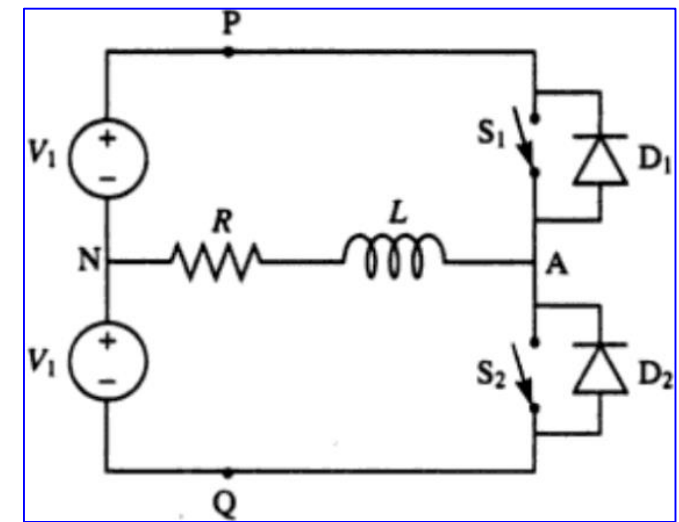

Common point of the DC capacitors should be made available.

The input dc to the half-bridge has to be a split power supply. If the midpoint is not available then two identical capacitors are connected in series across the dc source.

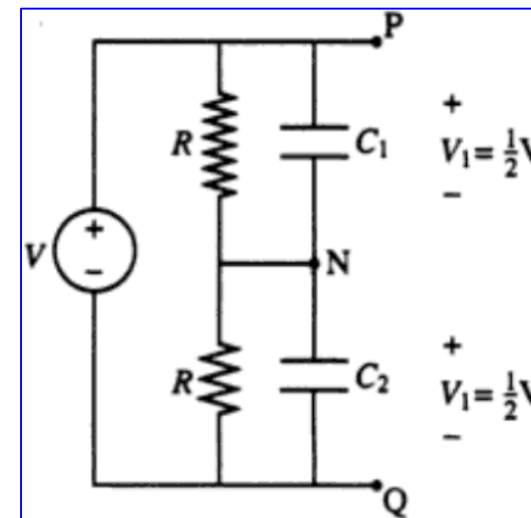Two large and equal resistors may be connected to ensure correct voltage division. They also enable the capacitors to discharge when the DC supply is switched off.



THE HALF-BRIDGE INVERTER WITH INDUCTIVE LOAD

Let us assume zero initial current in L and S_1 is turned ON at $t = 0$.

$$L \frac{di}{dt} + Ri = V_1 \quad i = \frac{V_1}{R} (1 - e^{-t/\tau}) \quad \tau = L/R \quad T = 1/f$$

At $t = T/2$, the first half-period ends and the circuit configuration changes as S_1 is turned OFF.

At this instant, $I_{01} = \frac{V_1}{R} (1 - e^{-T/2\tau})$

The second half-period commences at $t = T/2$ when S_2 is turned ON.





What will happen if, after turning OFF S_1 , we do not instantly turn ON S_2 , but delay this by a short 'dead time'?

The induced e.m.f. due to L will cause D_2 to become forward-biased and turn ON. Therefore, it'll not make any difference to the voltage across the load, or the current through it, if we delay the turn-ON of S_2 , as long as this delay does not exceed the time it takes for the current to fall to zero.

Take a new reference zero for t , at the commencement of the second half-period,


$$L \frac{di}{dt} + Ri = -V_1 \quad i = I_{01} \quad \text{at } t = 0$$
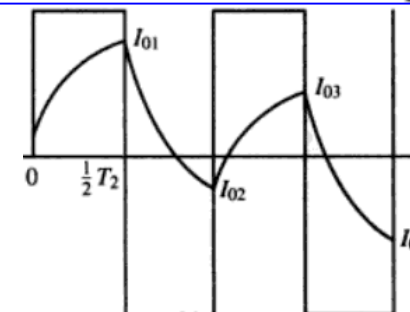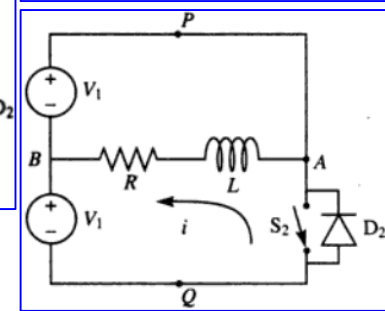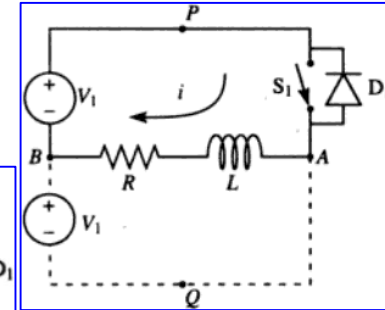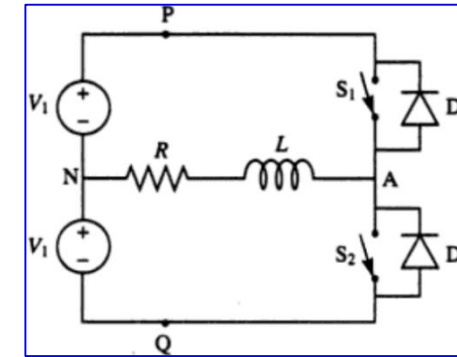
$$i = -\frac{V_1}{R} (1 - e^{-t/\tau}) + I_{01} e^{-t/\tau}$$



THE HALF-BRIDGE INVERTER WITH INDUCTIVE LOAD

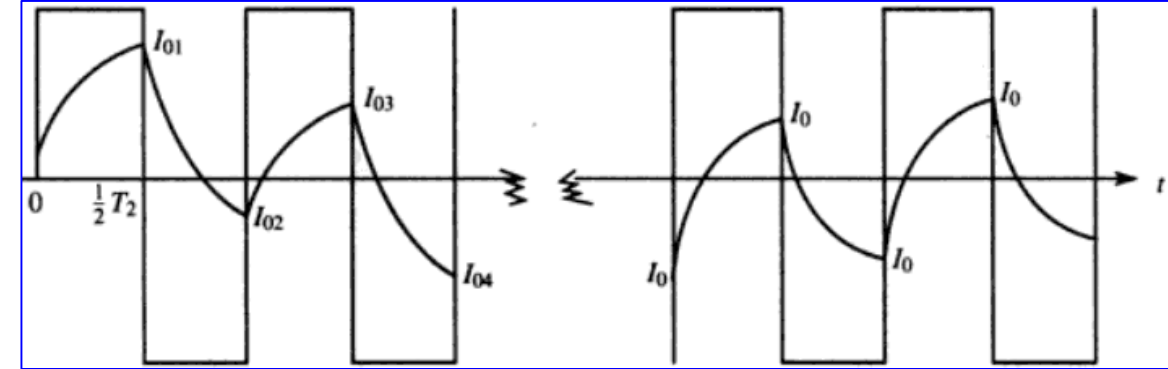After several cycles of switching, the difference in the current waveform between successive cycles become negligible.



The voltage waveform is repetitive from the very beginning, whereas the current waveform needs several cycles of operation to attain repetitive conditions.

Taking $t = 0$ at the instant of turn ON of switching block 1

$$\left. \begin{aligned} L \frac{di}{dt} + Ri &= V_1 \\ i &= -I_0 \text{ at } t = 0 \end{aligned} \right\}$$

The solution of this is

$$i = -I_0 e^{-t/\tau} + \frac{V_1}{R} (1 - e^{-t/\tau})$$



At $t = \frac{1}{2}T$, from symmetry considerations, $i = I_0$. Therefore

$$I_0 = -I_0 e^{-T/2\tau} + \frac{V_1}{R} (1 - e^{-T/2\tau})$$

This gives I_0 and the expression for i as

$$I_0 = \frac{V_1}{R} \frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}}$$

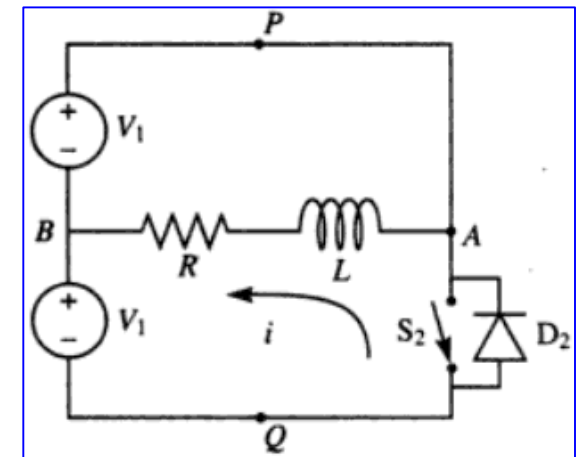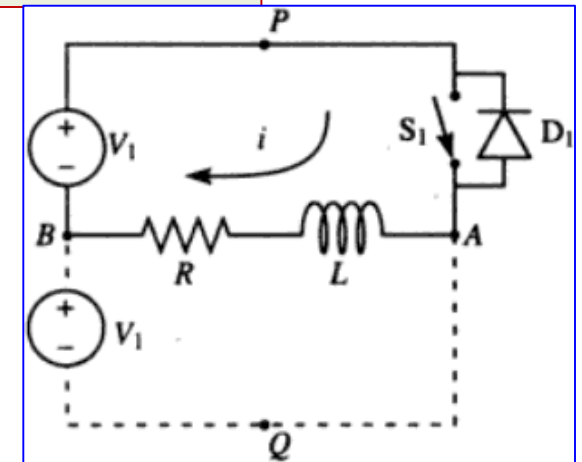
$$i = -\frac{V_1}{R} \frac{1 - e^{-T/2\tau}}{1 + e^{-T/2\tau}} e^{-t/\tau} + \frac{V_1}{R} (1 - e^{-t/\tau}) \quad \text{for } 0 \leq t \leq \frac{1}{2}T$$



Commutation Sequence of Switching Elements

The turn OFF switching of one element and the turn ON switching of another element, by which a transfer of current takes place from one element to another, is called commutation.

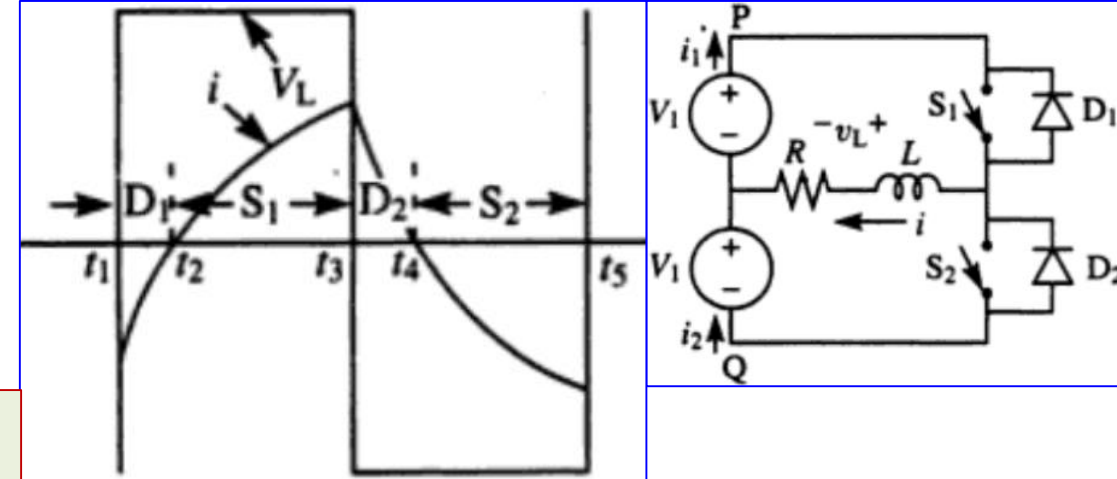The instants at which four commutations take place in a half-bridge inverter are the instants of zero-crossings of the voltage and current waveforms.



The commutations at the zero-crossings of the voltage waveform, namely t_1 and t_3 , are implemented directly by the action of the switching control circuit. For example, the commutation at t_1 takes place when the switching control circuit turns OFF S_2 .

The instant at which the current goes through zero depends on the load circuit time constant, which can be different for different loads. For example, at t_2 , the switching control circuit should be so designed that the control signal to turn ON S_1 must be present at this instant, although t_2 itself is variable and dependent on the load circuit time constant. The practical way in which this can be done is to commence the turn ON switching signal of S_1 after a short 'dead time' after t_1 , even though the switch itself is not ready to turn ON. The signal should continue to be present when the switch is able to turn ON at the current zero-crossing.