

# EE 238

## Power Engineering - II

### Power Electronics



## Lecture 12

Instructor: Prof. Anshuman Shukla

Email: [ashukla@ee.iitb.ac.in](mailto:ashukla@ee.iitb.ac.in)

# BOOST CHOPPER

## Boundary between Cont. and Discont. Modes

$$\frac{V_o}{V_d} = \frac{T_s}{t_{\text{off}}} = \frac{1}{1 - D}$$

$$\frac{I_o}{I_d} = (1 - D)$$




$$I_{LB} = \frac{1}{2} i_{L,\text{peak}}$$

$$= \frac{1}{2} \frac{V_d}{L} t_{\text{on}}$$

$$= \frac{T_s V_o}{2L} D(1 - D)$$

The average output current at the edge of cont. cond. is
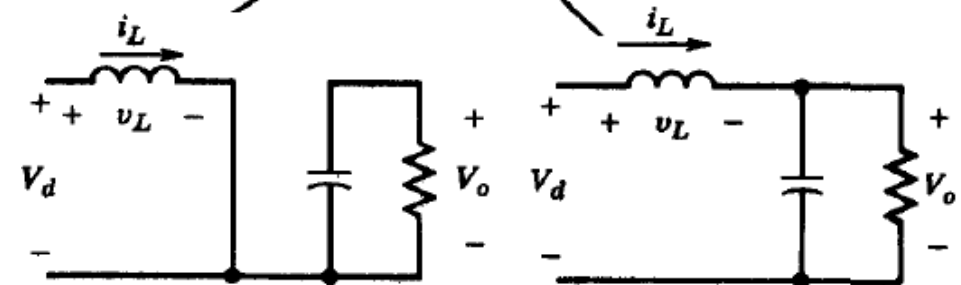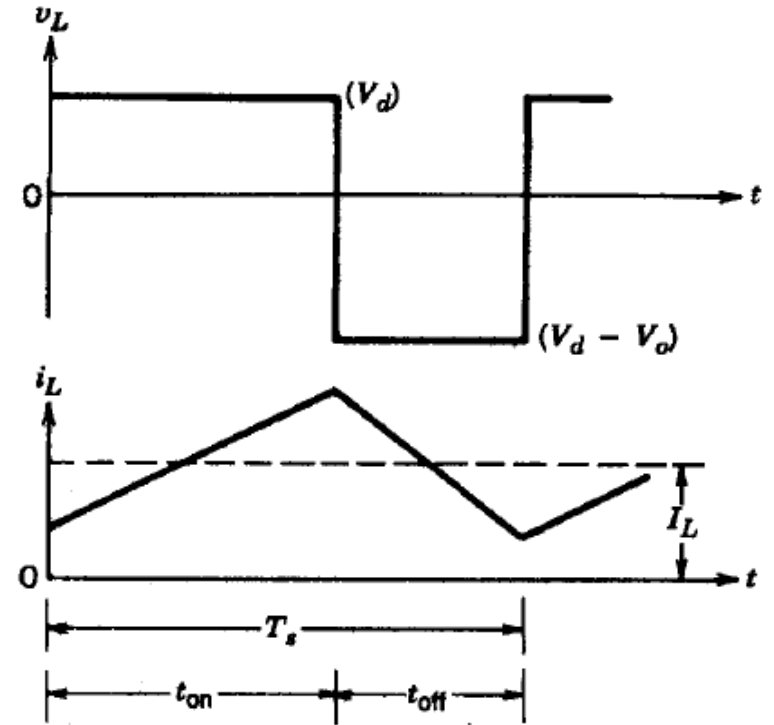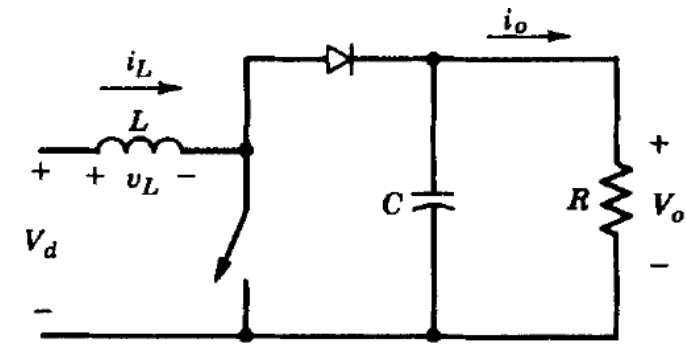
$$I_{oB} = \frac{T_s V_o}{2L} D(1 - D)^2$$



# STEP-UP (BOOST) CONVERTER

## Boundary between Cont. and Discont. Modes

$$I_{LB} = \frac{T_s V_o}{2L} D(1 - D) \frac{I_o}{I_d} = (1 - D) i_d = i_L$$

The average output current at the edge of cont. cond. is

$$I_{oB} = \frac{T_s V_o}{2L} D(1 - D)^2$$

In most Boost converter applications,  $V_o$  is kept constant.

$I_{LB}$  reaches a maximum value at  $D = 0.5$ :

$$I_{LB, \max} = \frac{T_s V_o}{8L}$$

Also,  $I_{oB}$  has its maximum at  $D = 0.333$




$$I_{oB, \max} = \frac{2}{27} \frac{T_s V_o}{L} = 0.074 \frac{T_s V_o}{L}$$

In terms of their maximum values,

$$I_{LB} = 4D(1 - D)I_{LB, \max}$$

$$I_{oB} = \frac{27}{4} D(1 - D)^2 I_{oB, \max}$$

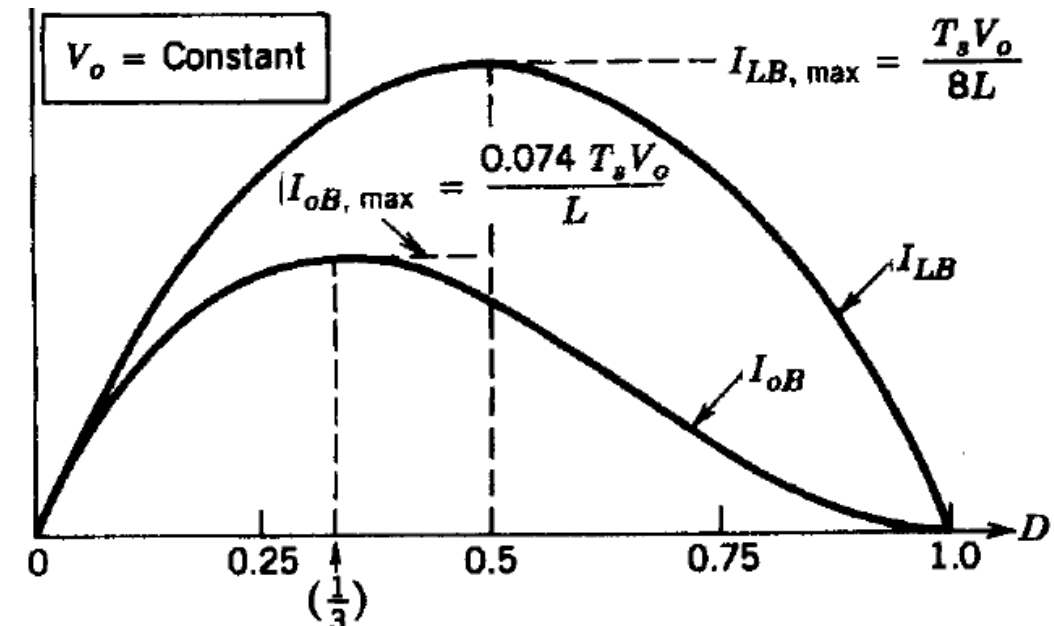
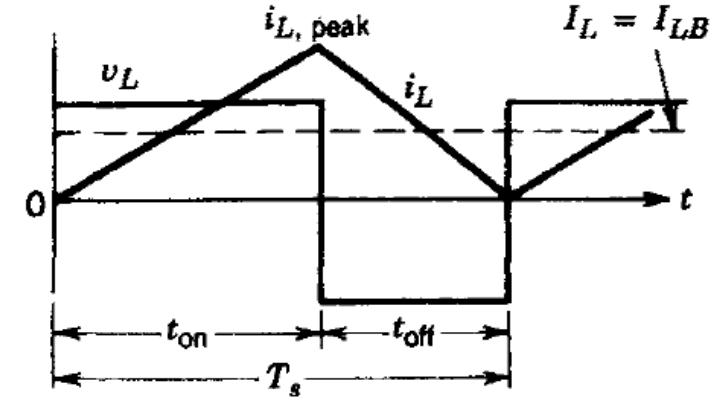
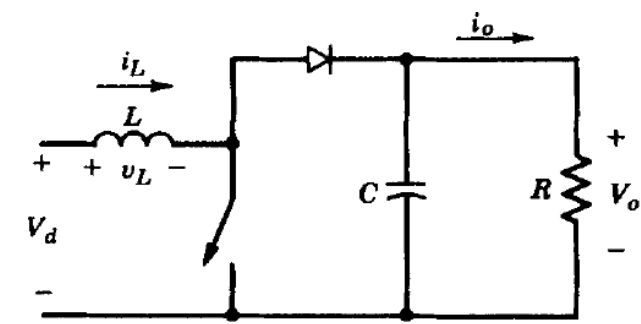
For a given  $D$ , with constant  $V_o$ , if the average load current drops below  $I_{oB}$  (and, hence, the average inductor current below  $I_{LB}$ ), the current conduction will become discontinuous.


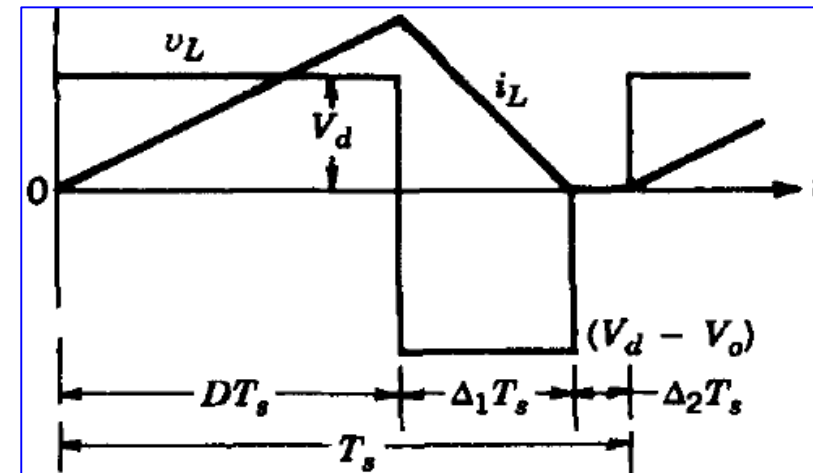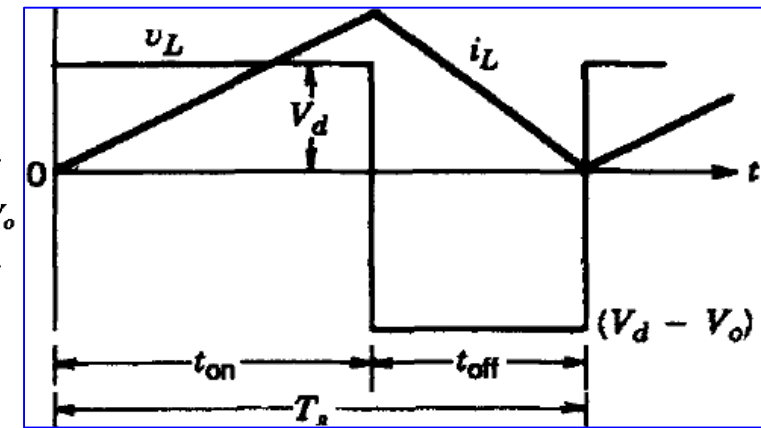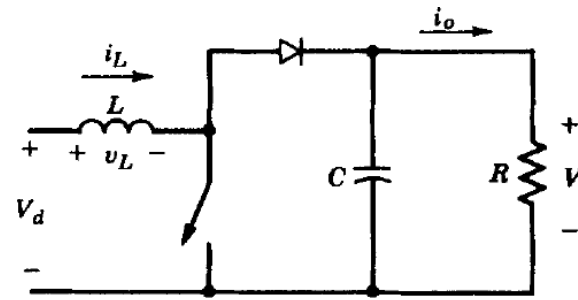
# DISCONTINUOUS-CONDUCTION MODE

Assume that as the output load power decreases,  $V_d$  and  $D$  remain constant (even though, in practice,  $D$  would vary in order to keep  $V_o$  constant).

- The DCM occurs due to decreased  $P_o$  ( $=P_d$ ) and, hence, a lower  $I_L$  ( $=I_d$ ), since  $v_d$  is constant.
- Since  $i_{L\text{peak}}$  is the same in both modes, a lower value of  $I_L$  (and, hence a discontinuous  $I_L$ ) is possible only if  $V_o$  goes up.



If we equate the integral of the inductor voltage over one time period to zero,

$$V_d D T_s + (V_d - V_o) \Delta_1 T_s = 0$$

$$\therefore \frac{V_o}{V_d} = \frac{\Delta_1 + D}{\Delta_1}$$

$$\frac{I_o}{I_d} = \frac{\Delta_1}{\Delta_1 + D} \quad (\text{since } P_d = P_o)$$


The average input current, which is also equal to the inductor current, is

$$I_d = \frac{V_d}{2L} D T_s (D + \Delta_1) \Rightarrow I_o = \left( \frac{T_s V_d}{2L} \right) D \Delta_1$$
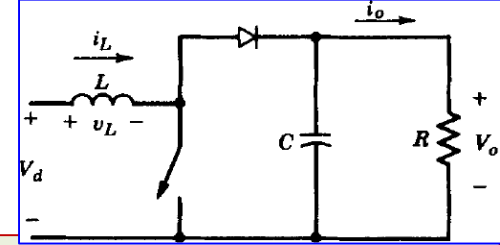
# DISCONTINUOUS-CONDUCTION MODE


$$I_o = \left( \frac{T_s V_d}{2L} \right) D \Delta_1 \therefore \frac{V_o}{V_d} = \frac{\Delta_1 + D}{\Delta_1}$$

$$I_{oB, \max} = \frac{2}{27} \frac{T_s V_o}{L} = 0.074 \frac{T_s V_o}{L}$$



In practice, since  $V_o$  is held constant and  $D$  varies in response to the variation in  $V_d$ , it is more useful to obtain the required duty ratio  $D$  as a function of load current for various values of  $V_o / V_d$ .
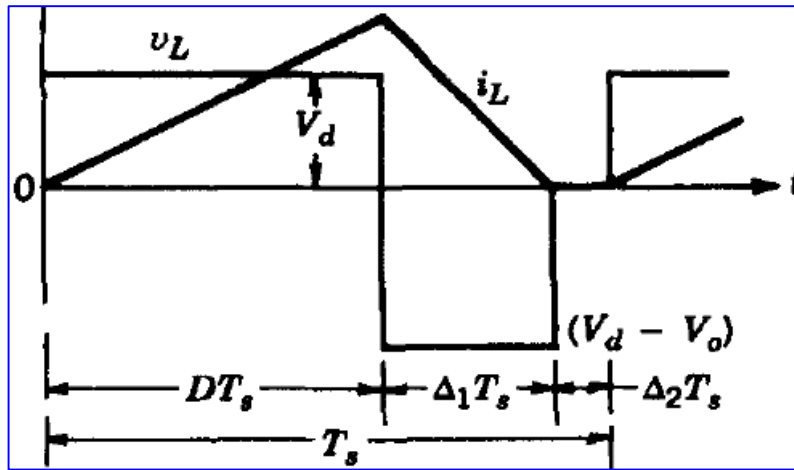
$$D = \left[ \frac{4}{27} \frac{V_o}{V_d} \left( \frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oB, \max}} \right]^{1/2}$$



$D$  is plotted as a function of  $I_o/I_{oB, \max}$  for various values of  $V_d/V_o$ .


In the discontinuous mode, if  $V_o$  is not controlled during each switching time period, at least

$$\frac{L}{2} i_{L, \text{peak}}^2 = \frac{(V_d D T_s)^2}{2L} \quad \text{W-s}$$

are transferred from the input to the output capacitor and to the load.


For constant output voltage and variable input voltage applications
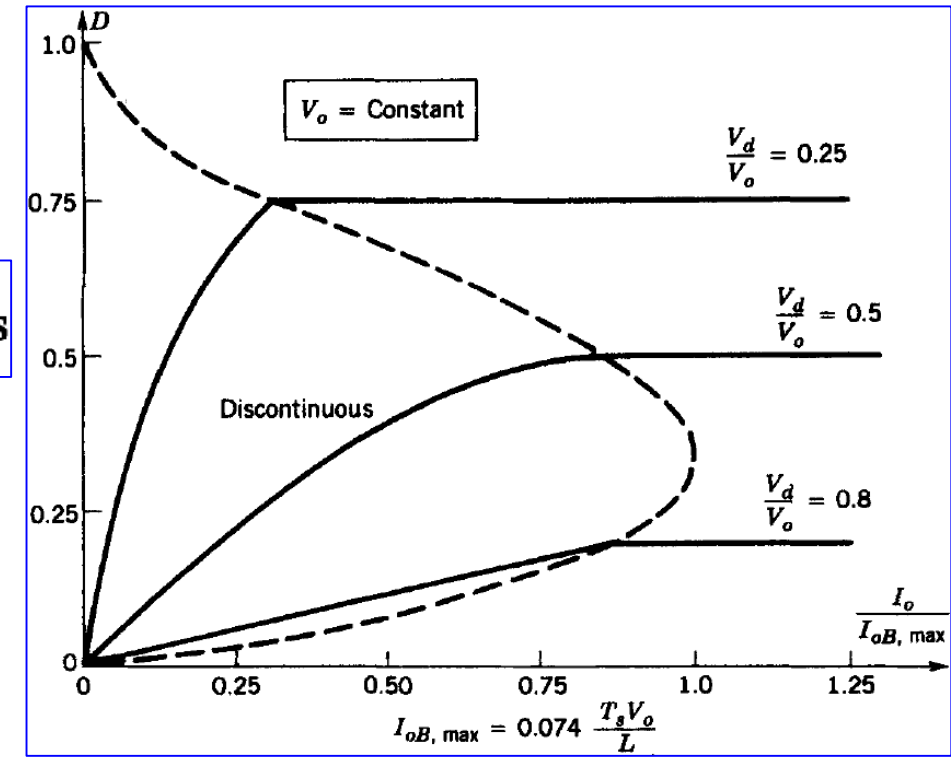
$$\left( 1 - \frac{V_{in, \max}}{V_o} \right) \leq D \leq \left( 1 - \frac{V_{in, \min}}{V_o} \right)$$



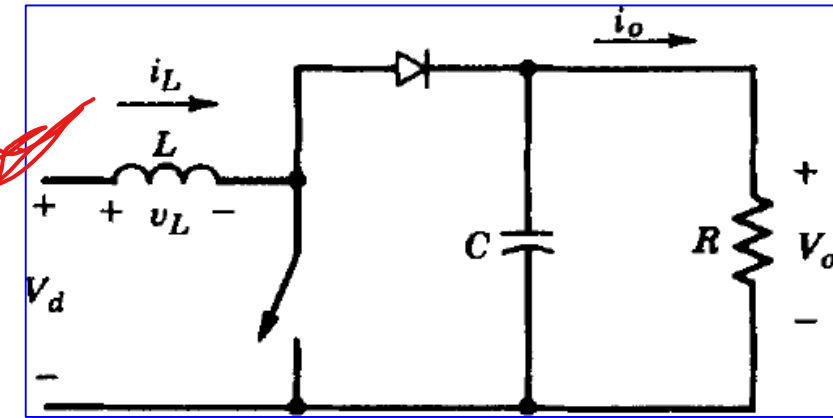
## STEP-UP (BOOST) CONVERTER EFFECT OF PARASITIC ELEMENTS

The parasitic elements in a step-up converter are due to the losses associated with the inductor, the capacitor, the switch, and the diode.



Unlike the ideal characteristic, in practice,  $V_o/V_d$  declines as  $D$  approaches unity.

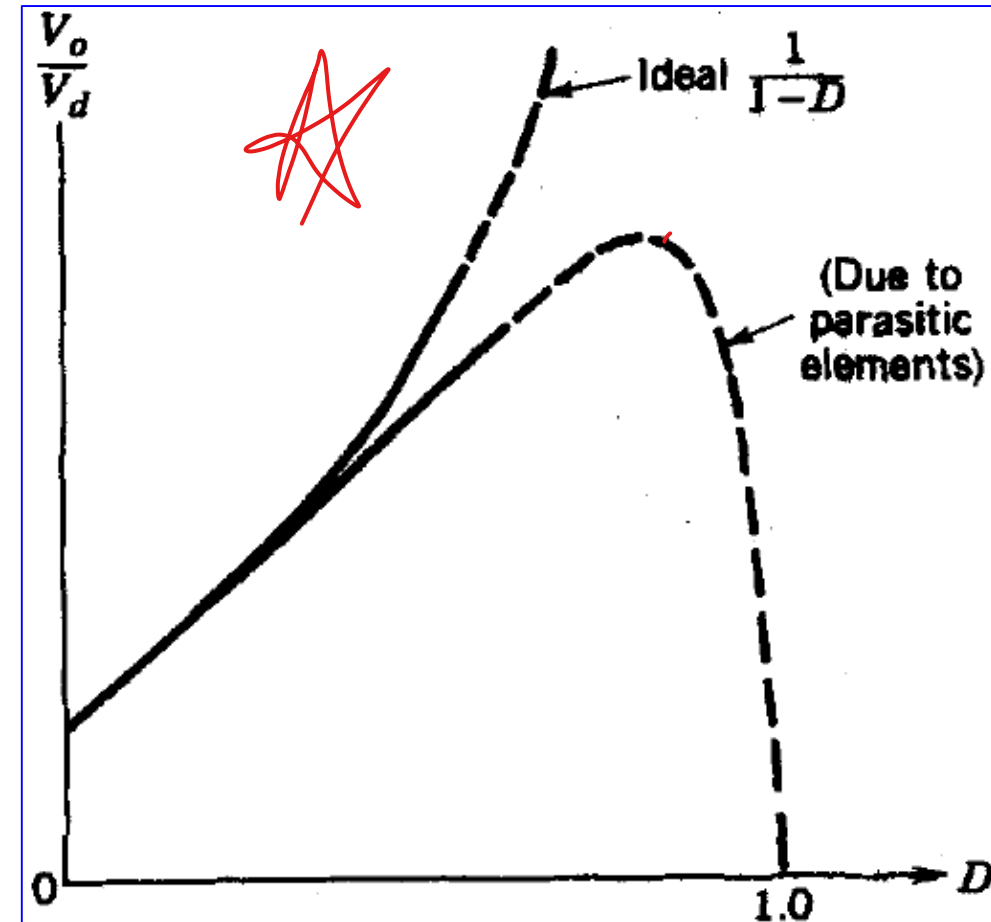These parasitic elements can be incorporated into circuit simulation programs on computers for designing such converters.



# Inductor Resistance

- L should be designed to have small resistance to minimize power loss and maximize efficiency.
- The existence of a small inductor resistance does not substantially change the buck converter analysis.
- ~~However~~, inductor resistance affects performance of the boost converter, especially at high duty ratios.

$$V_o = \frac{V_s}{1 - D}$$

For analysis purpose, assume that  $i_L$  is approximately constant.

Neglecting other losses. And applying power balance:

$$\begin{aligned} P_s &= P_o + P_{r_L} \\ V_s I_L &= V_o I_D + I_L^2 r_L \end{aligned}$$

$r_L$  is the series resistance of  $L$ .



The diode current is equal to the inductor current when the switch is off and is zero when the switch is on. Therefore, the average diode current is  $I_D = I_L(1 - D)$

$$\Rightarrow I_L = \frac{I_D}{1 - D} = \frac{V_o/R}{1 - D}$$

From above,  $V_s I_L = V_o I_L(1 - D) + I_L^2 r_L$

$$\Rightarrow V_s = V_o(1 - D) + I_L r_L$$
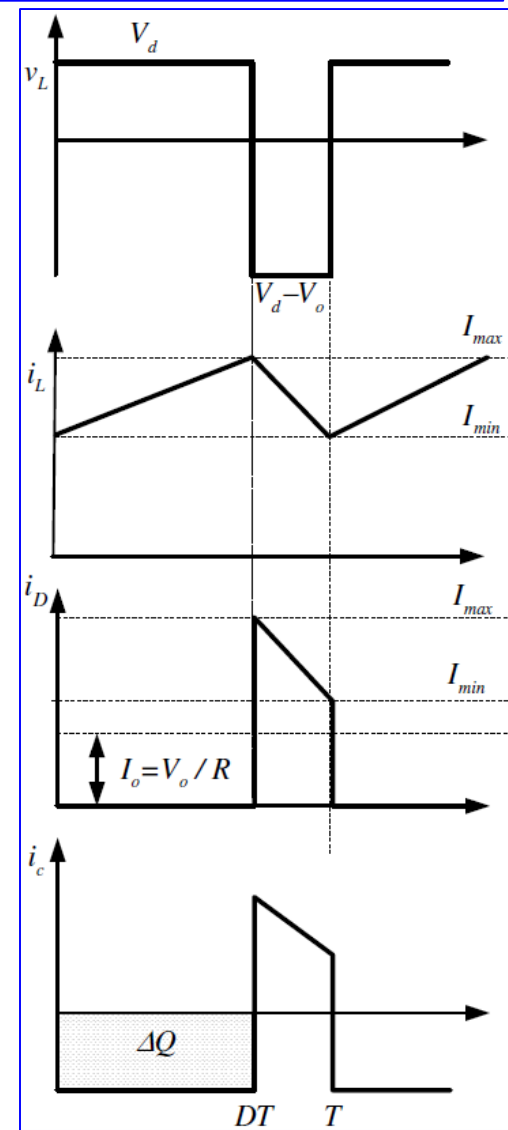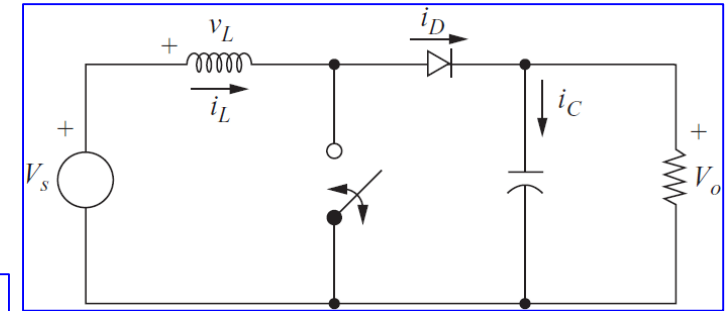
$$\text{Also, } I_L = \frac{I_D}{1 - D} = \frac{V_o/R}{1 - D} \Rightarrow V_s = \frac{V_o r_L}{R(1 - D)} + V_o(1 - D)$$



# Inductor Resistance

$$V_s = \frac{V_o r_L}{R(1 - D)} + V_o(1 - D)$$

Solving for  $V_o$ ,

$$V_o = \left( \frac{V_s}{1 - D} \right) \left( \frac{1}{1 + r_L/[R(1 - D)^2]} \right)$$


This eqn. is similar to that for an ideal converter but includes a correction factor to account for  $r_L$ .

The inductor resistance also has an effect on the power efficiency of converters. Efficiency is the ratio of output power to output power plus losses. For the boost converter


$$\eta = \frac{P_o}{P_o + P_{\text{loss}}} = \frac{V_o^2/R}{V_o^2/R + I_L^2 r_L}$$

$$\eta = \frac{V_o^2/R}{V_o^2/R + (V_o/R)^2/(1 - D)r_L} = \frac{1}{1 + r_L[R(1 - D)^2]}$$

Efficiency vs.  $D$

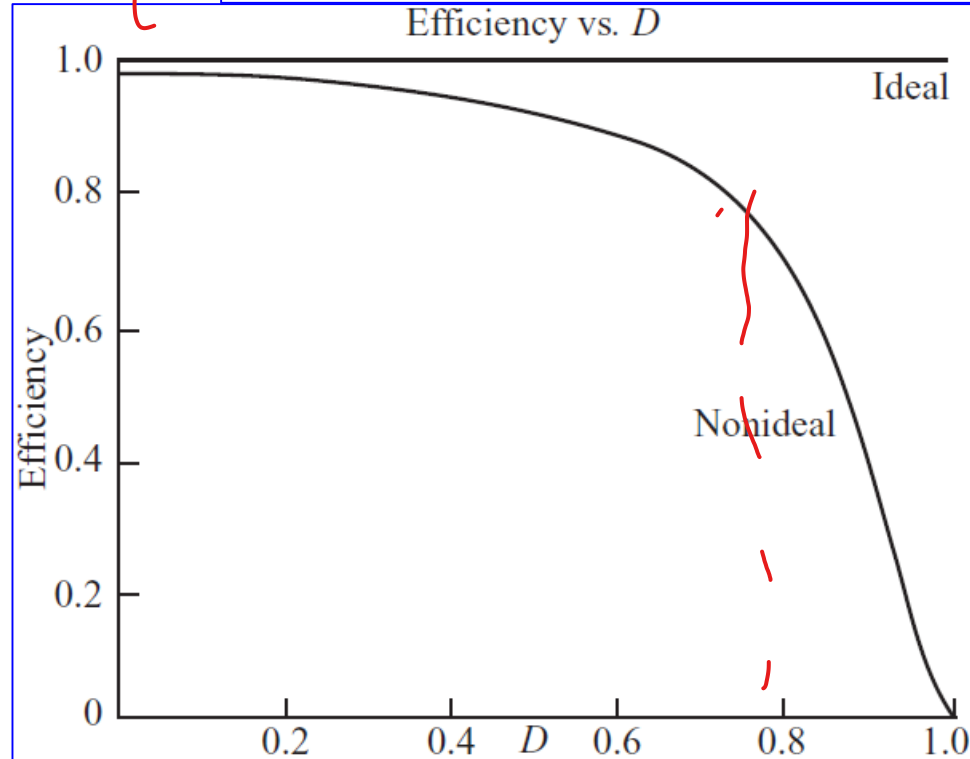

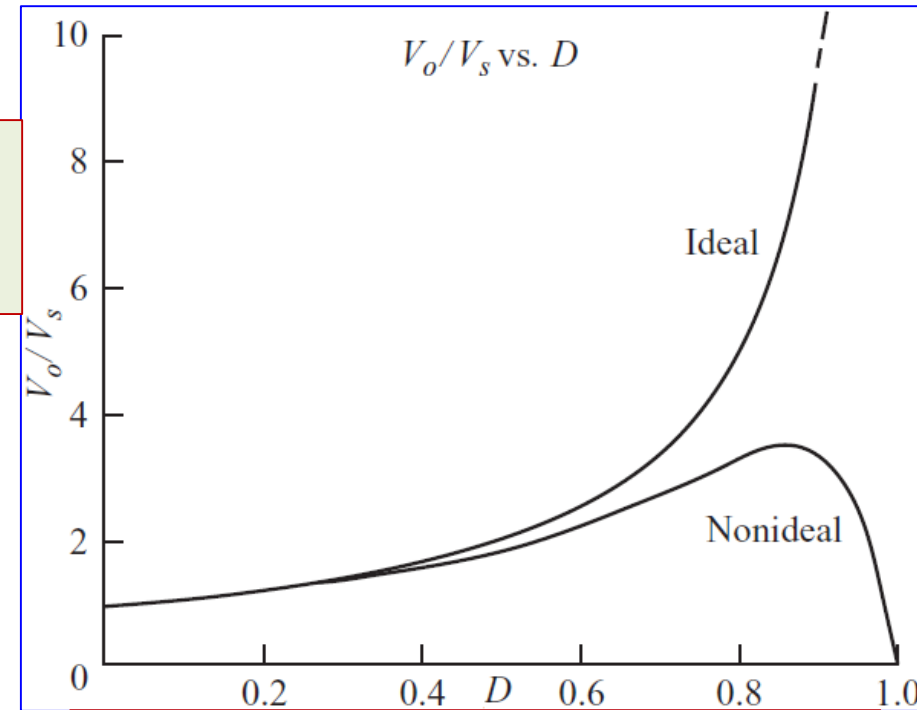As  $D$  increases, the converter efficiency decreases.



Output voltage of the boost converter with and without inductor resistance.

- Effect is dominant at high  $D$
- Difficult to achieve large conversion ratios ( $> 10$ )
- No power transfer at  $D = 1$






# OUTPUT VOLTAGE RIPPLE ( $\Delta V_o$ )

CCM: Assuming that all the ripple component  $i_D$  flows through C and its average value flows through the load resistor, the shaded area represents charge  $\Delta Q$ .

Current-sec. balance principle:

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{I_o DT_s}{C} = \frac{V_o}{R} \frac{DT_s}{C}$$

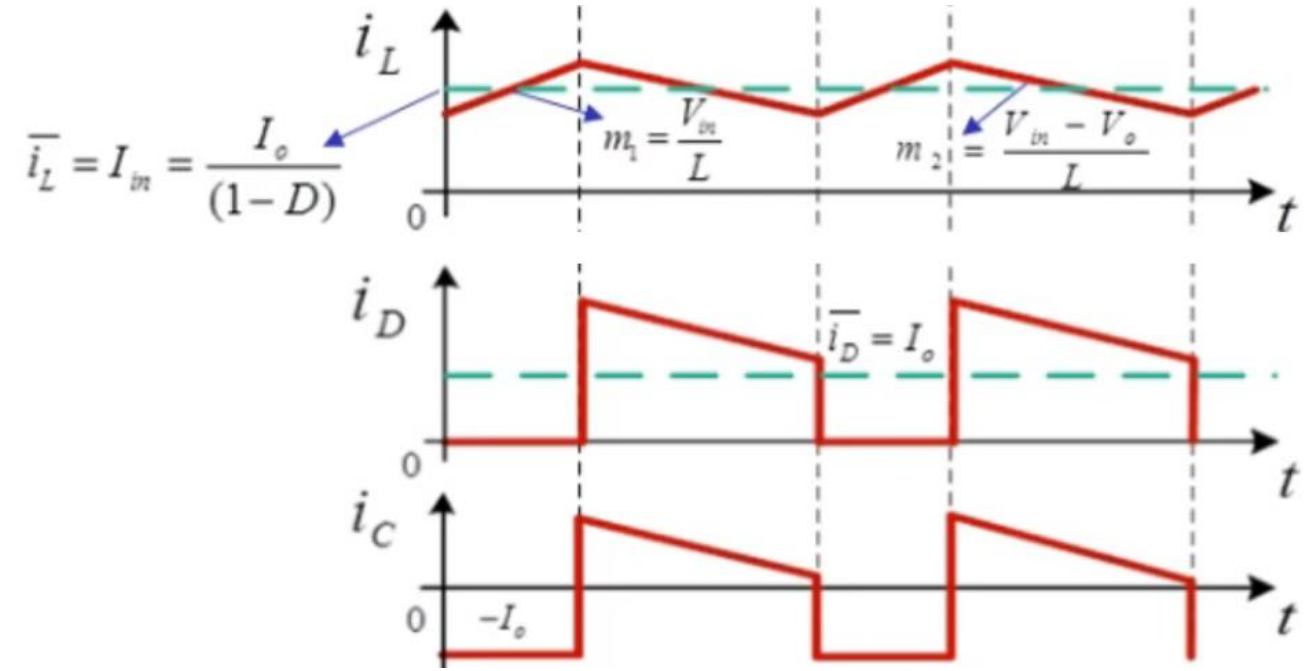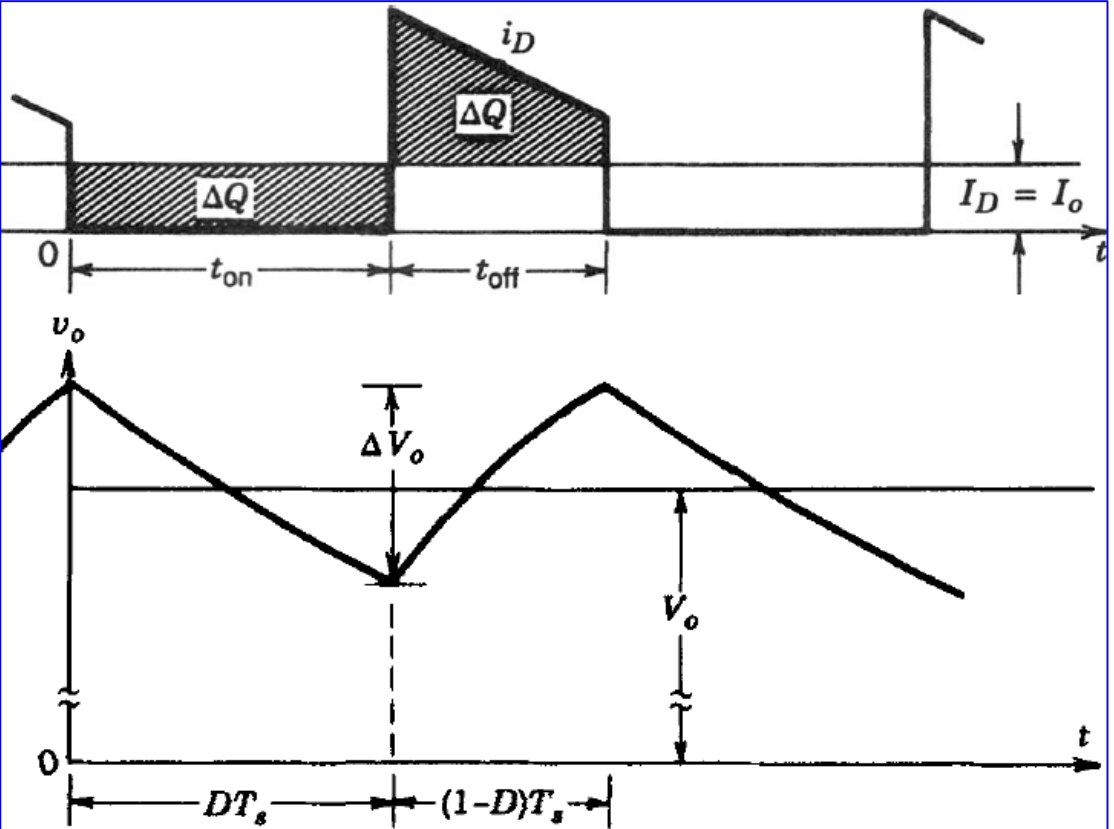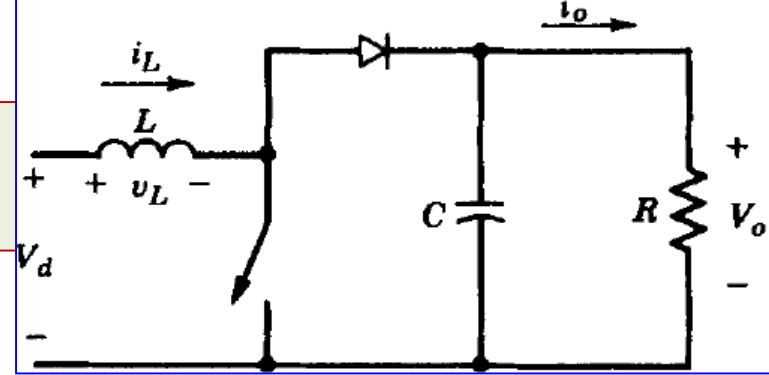
$$\therefore \frac{\Delta V_o}{V_o} = \frac{DT_s}{RC} = D \frac{T_s}{\tau} \quad (\text{where } \tau = RC \text{ time constant})$$



A similar analysis can be performed for the discontinuous mode of conduction.
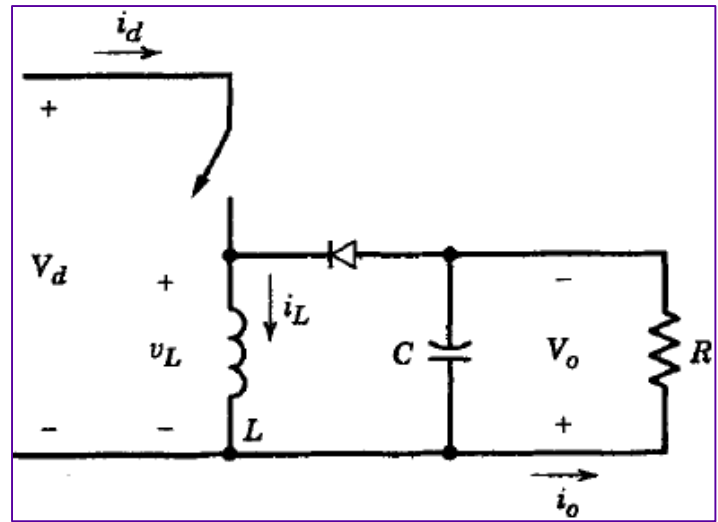
# Buck-Boost Converter

The main application of a buck-boost converter is in regulated dc power supplies, where a negative-polarity output may be desired with respect to the common terminal of the input voltage, and the output voltage can be either higher or lower than the input voltage.




## Buck-boost applications

### Industrial PCs


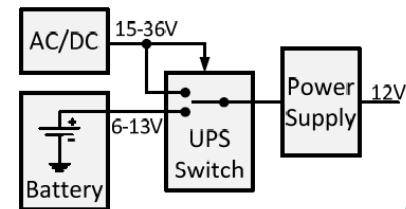
#### Application needs

- 6 V-36 V<sub>IN</sub> from AC-powered supply or battery
- 12 V output, 60 W-200 W




### Automotive start/stop & DVRs


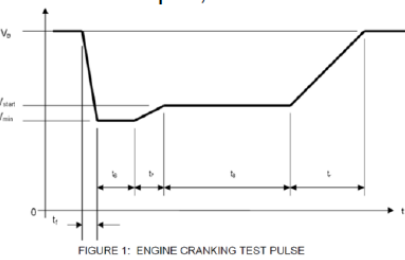
#### Application needs

- 9 V-16 V<sub>IN</sub>, 3.5 V during start
- ~12 V output, 60 W-120 W



### USB power delivery



#### Application needs

- 12 V bus or battery, 9V-16 V<sub>IN</sub>
- 5/12/20 V<sub>OUT</sub>, 10 W-100 W



USB Power Delivery profiles			
Profile	+5 V	+12 V	+20 V
1	2.0 A, 10 W	N/A	N/A
2		1.5 A, 18 W	N/A
3		3.0 A, 36 W	N/A
4			3.0 A, 60 W
5		5.0 A, 60 W	5.0 A, 100 W

### Industrial & battery chargers


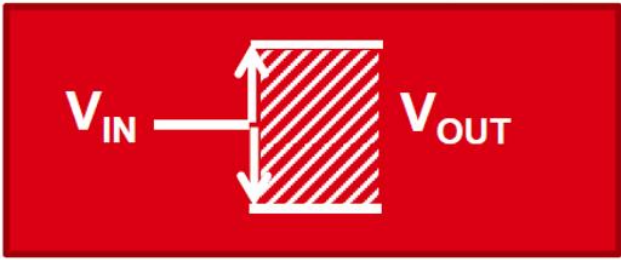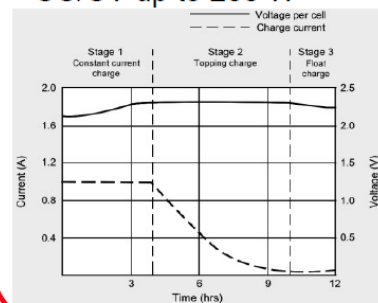
#### Application needs


- 12 V or 24 V<sub>IN</sub> or DC adapter
- CC/CV up to 200 W+




# BUCK-BOOST CONVERTER

A buck-boost converter can be obtained by the cascade connection of the two basic converters: the step-down converter and the step-up converter.


Buck

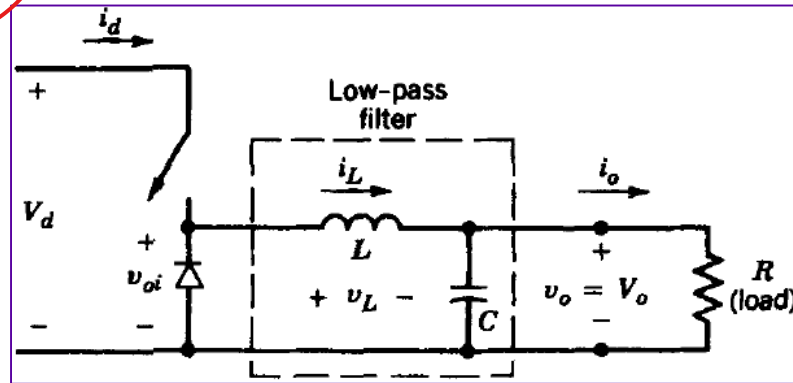

Boost

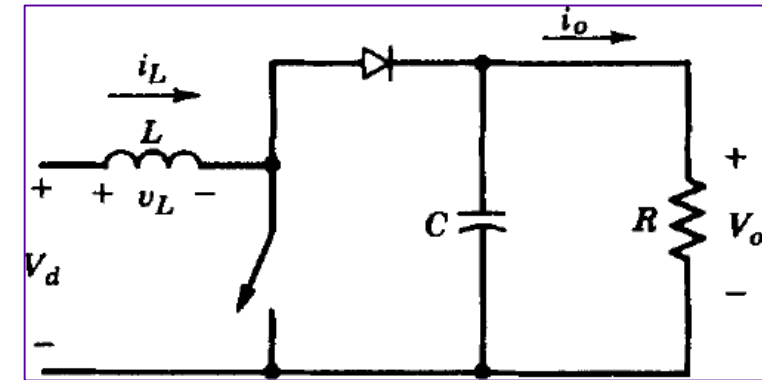

Buck-Boost


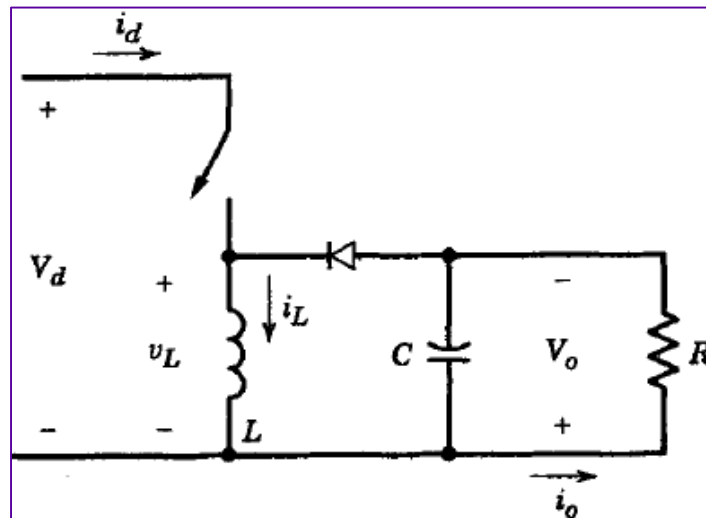


In steady state, the output-to-input voltage conversion ratio is the product of the conversion ratios of the two converters in cascade (assuming that switches in both converters have the same  $D$ ):


This allows the output voltage to be higher or lower than the input voltage, based on the duty ratio  $D$ .

$$\frac{V_o}{V_d} = D \frac{1}{1 - D}$$



# BUCK-BOOST CONVERTER

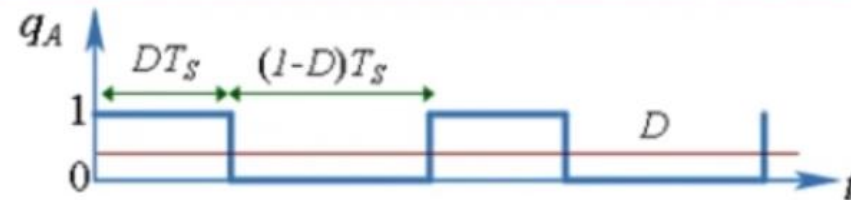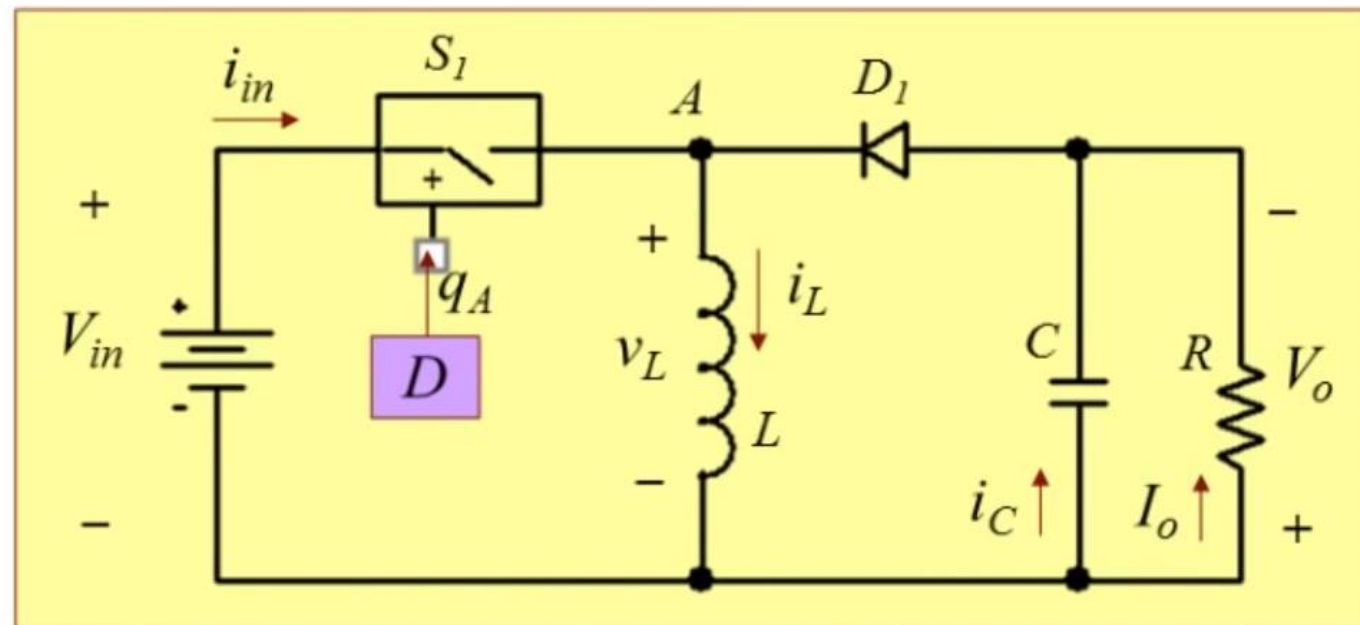


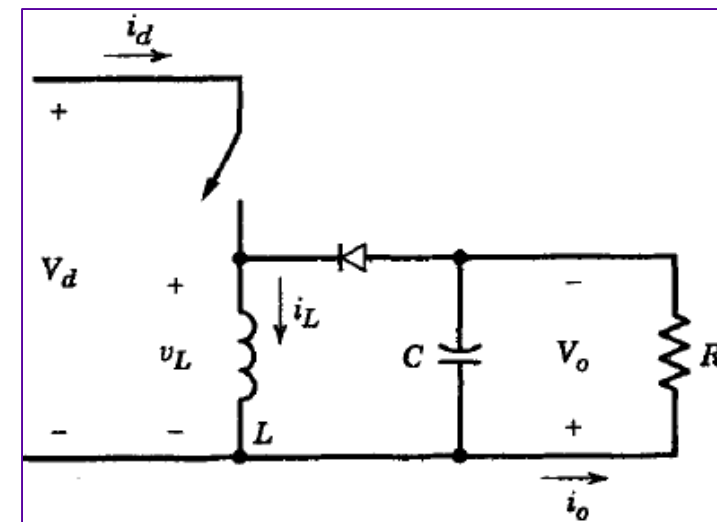
- Step up as well as step down depending on  $D$
- Negative output (with respect to input ground)
- Isolated version – flyback converter quite popular at low ( $\sim 100$  W) power level




# BUCK-BOOST CONVERTER

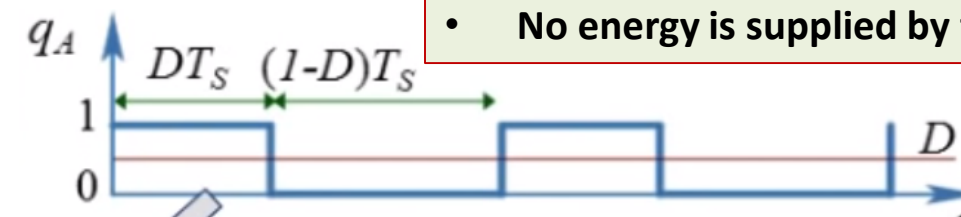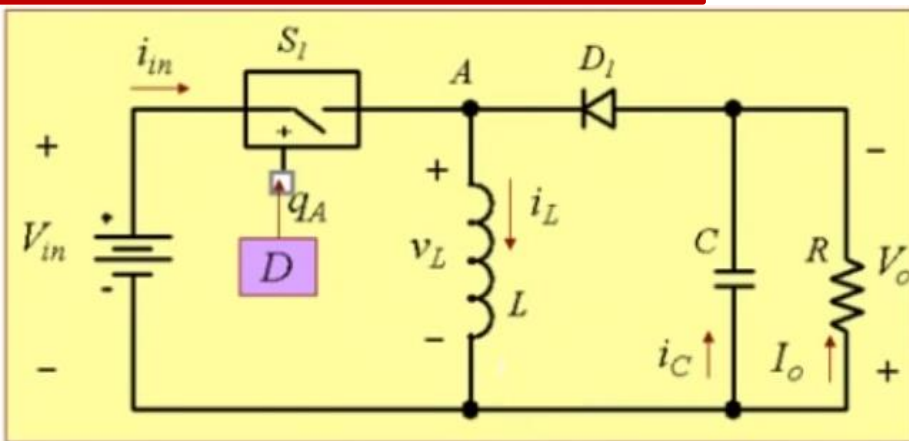

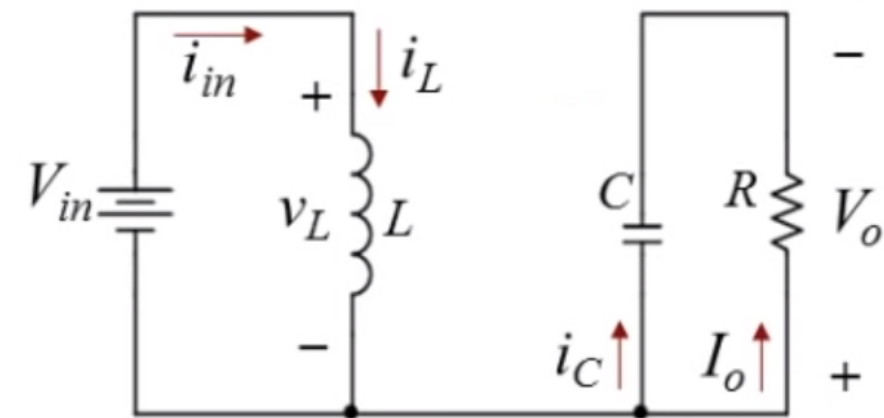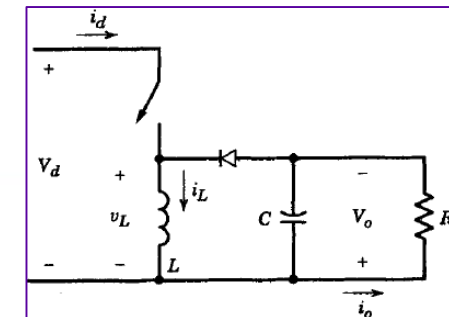- When the switch is closed, the input provides energy to the inductor and the diode is reverse biased.
- When the switch is open, the energy stored in the inductor is transferred to the output.
- No energy is supplied by the input during this interval.



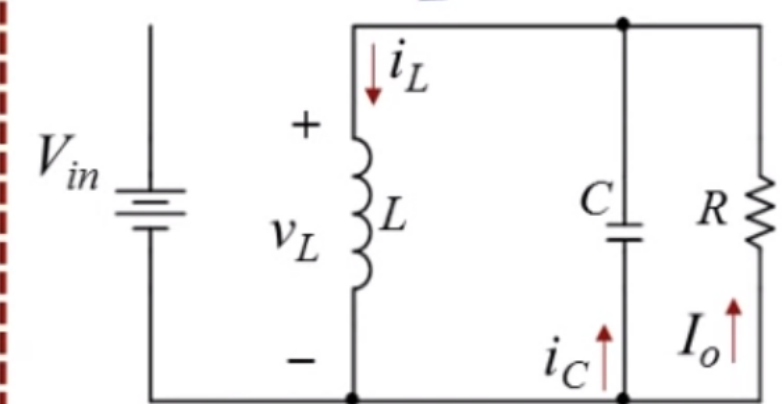
- $v_L = V_{in}$
- $i_L$  and energy stored in L increase
- C supports load and discharges
- C large enough to maintain voltage almost constant (small ripple)



- $v_L = -V_o$
- $i_L$  and energy stored in L decrease, energy fed to C and R
- $i_C$  positive and C charges up
- C large enough to maintain voltage almost constant (small ripple)




# BUCK-BOOST CONVERTER

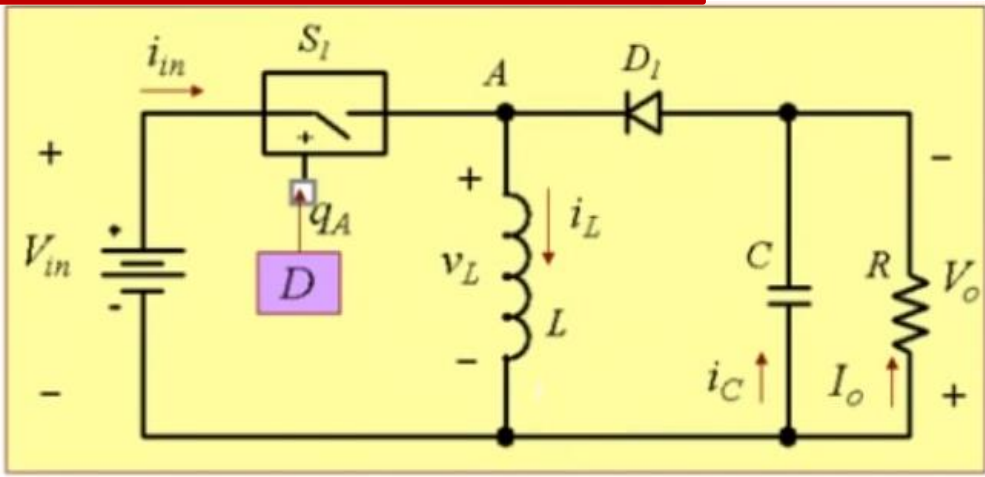

Buck operation for  
 $D \leq 0.5$

Boost operation for  
 $D \geq 0.5$

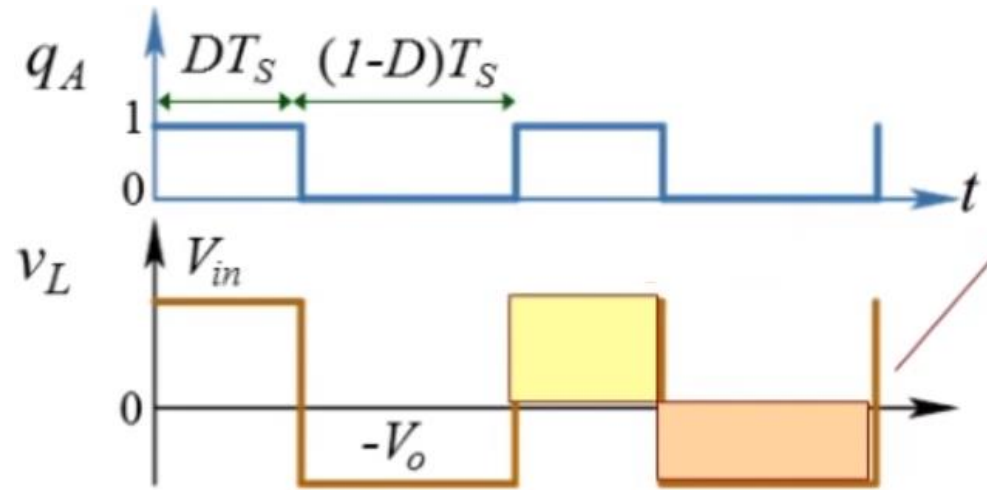

$$V_{in}DT_s + (-V_o)(1-D)T_s = 0$$
$$V_{in}D = V_o(1-D)$$

$$\frac{V_o}{V_{in}} = \frac{D}{1-D}$$

Input-output voltage relationship for buck-boost

$$\frac{I_{in}}{I_o} = \frac{D}{1-D}$$

Input-output current relationship using power balance

Switch closed

$$v_L = V_d = L \frac{di_L}{dt}$$

$$\Rightarrow \frac{di_L}{dt} = \frac{V_d}{L}$$

$$\frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_d}{L}$$

$$\Rightarrow (\Delta i_L)_{closed} = \frac{V_d DT}{L}$$



Switch opened

$$v_L = V_o = L \frac{di_L}{dt}$$


$$\Rightarrow \frac{di_L}{dt} = \frac{V_o}{L}$$

$$\frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_o}{L}$$

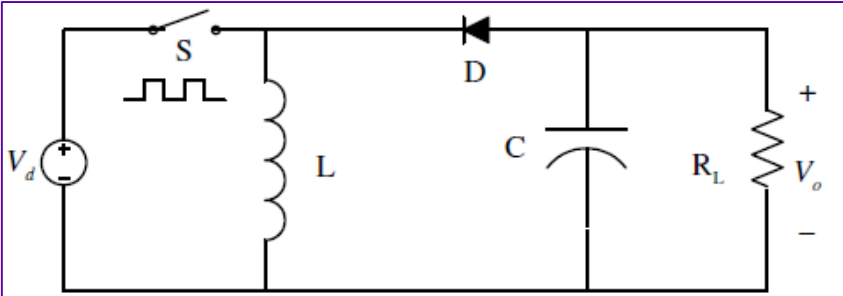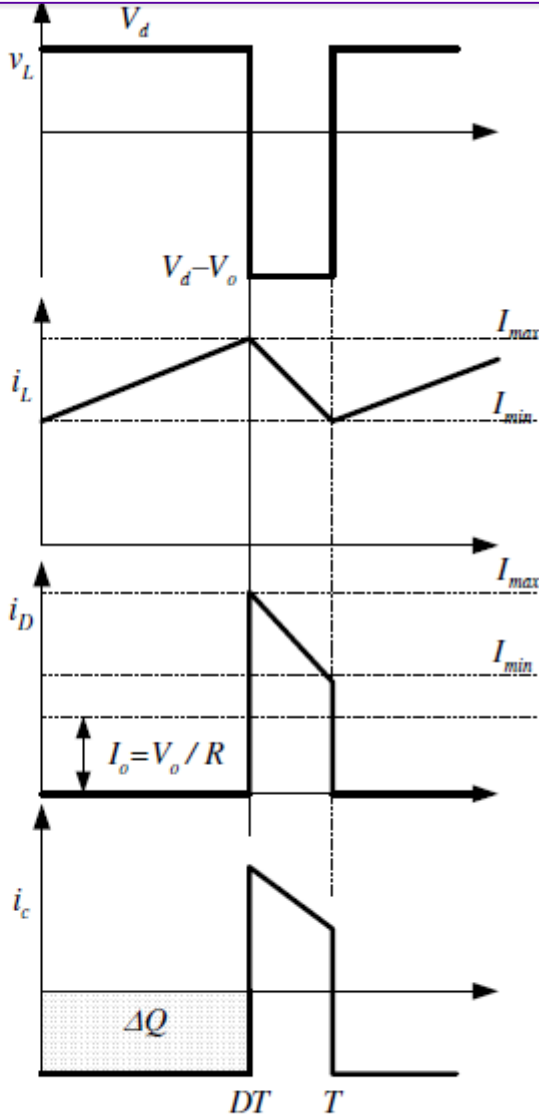
$$\Rightarrow (\Delta i_L)_{opened} = \frac{V_o (1-D)T}{L}$$



CIRCUIT OF BUCK-BOOST CONVERTER

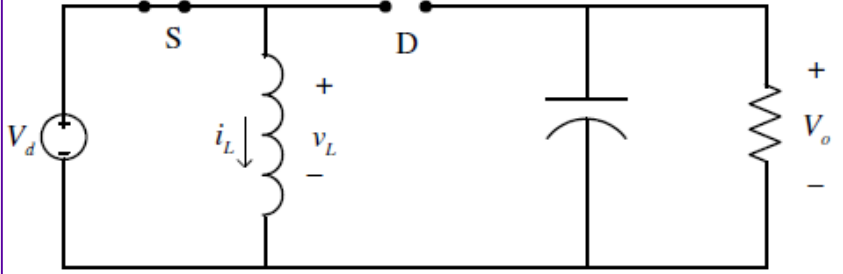

CIRCUIT WHEN SWITCH IS CLOSED

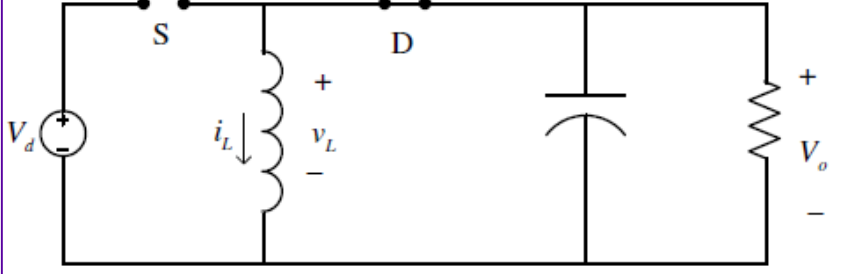

CIRCUIT WHEN SWITCH IS OPENED

# Buck-boost analysis CONTINUOUS-CONDUCTION MODE

## The $\Delta I$ method

Steady state operation :



$$\Delta i_{L(closed)} + \Delta i_{L(opened)} = 0$$

$$\Rightarrow \frac{V_d DT}{L} + \frac{V_o(1-D)T}{L} = 0$$

Output voltage :

$$\Rightarrow V_o = -V_s \left( \frac{D}{1-D} \right)$$

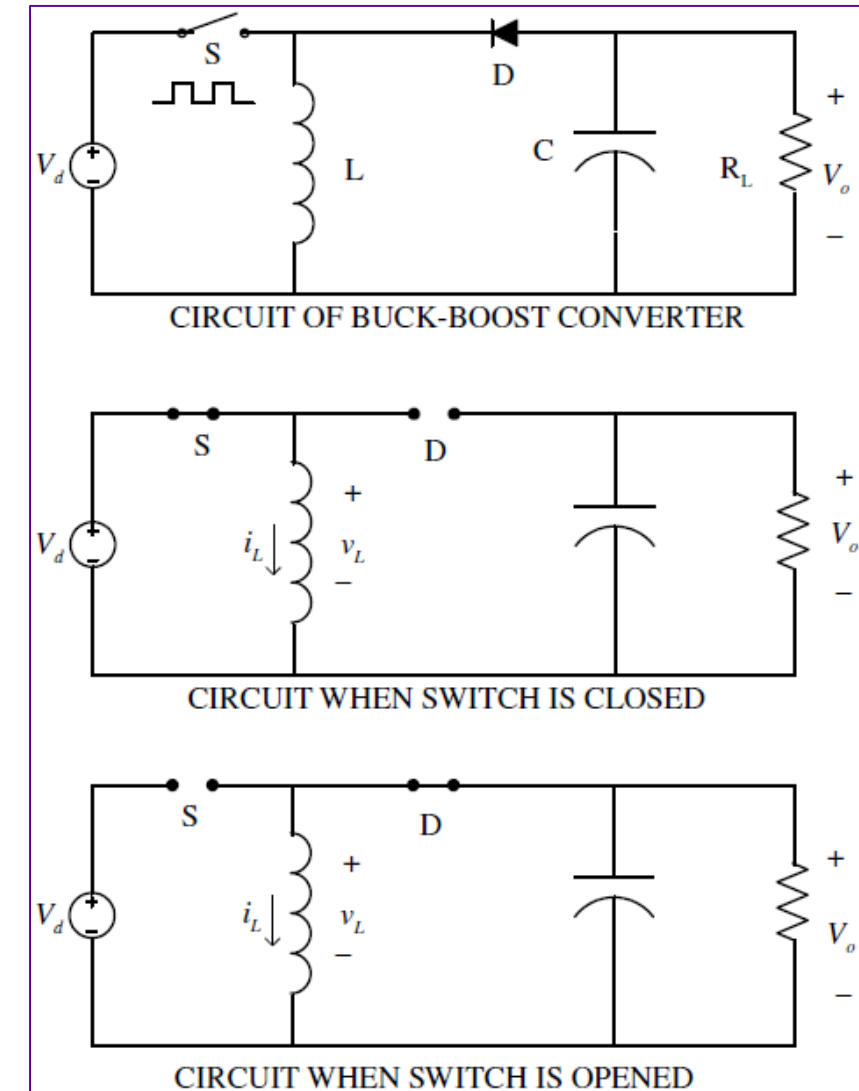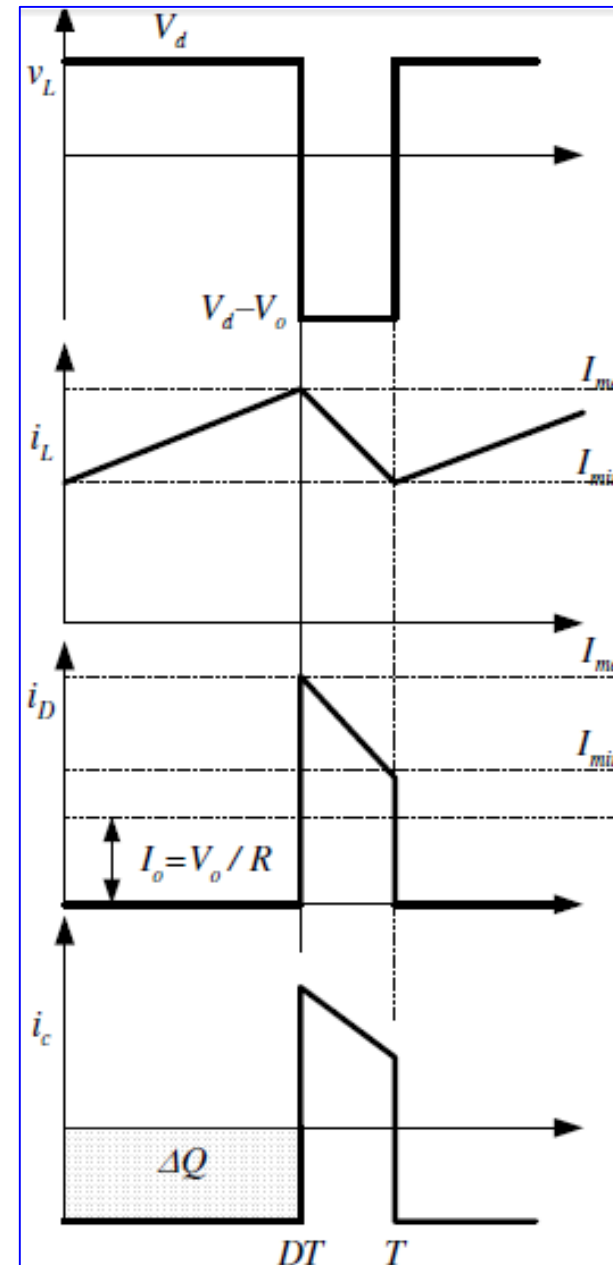
- NOTE: Output of a buck-boost converter either be higher or lower than input.
  - If  $D > 0.5$ , output is higher than input
  - If  $D < 0.5$ , output is lower input
- Output voltage is always negative.
- Note that output is never directly connected to load.
- Energy is stored in inductor when switch is closed and transferred to load when switch is opened.






# Comparison of $v_L$ in Buck, Boost and Buck-Boost


Buck

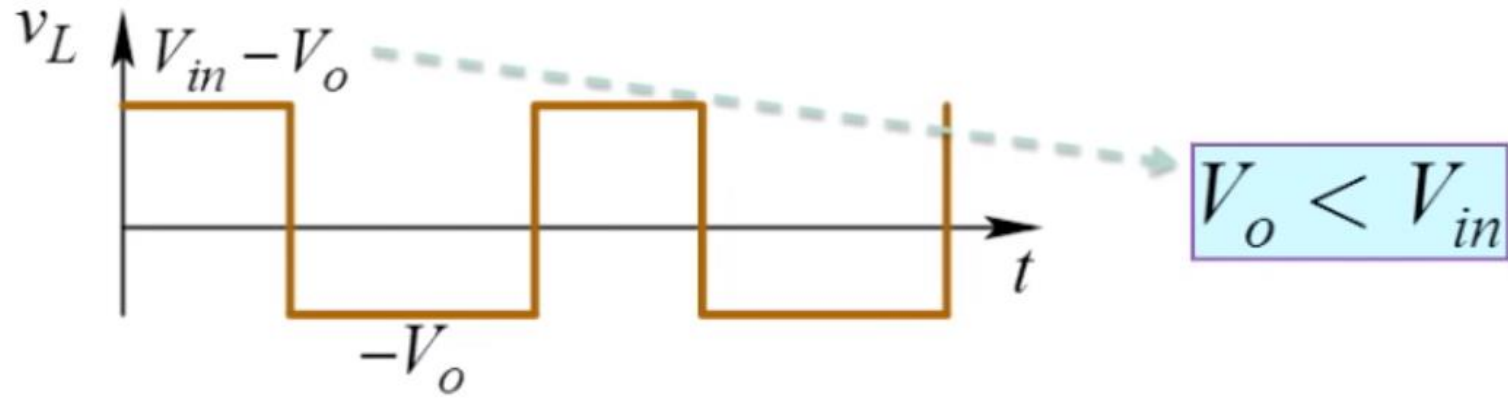

Boost

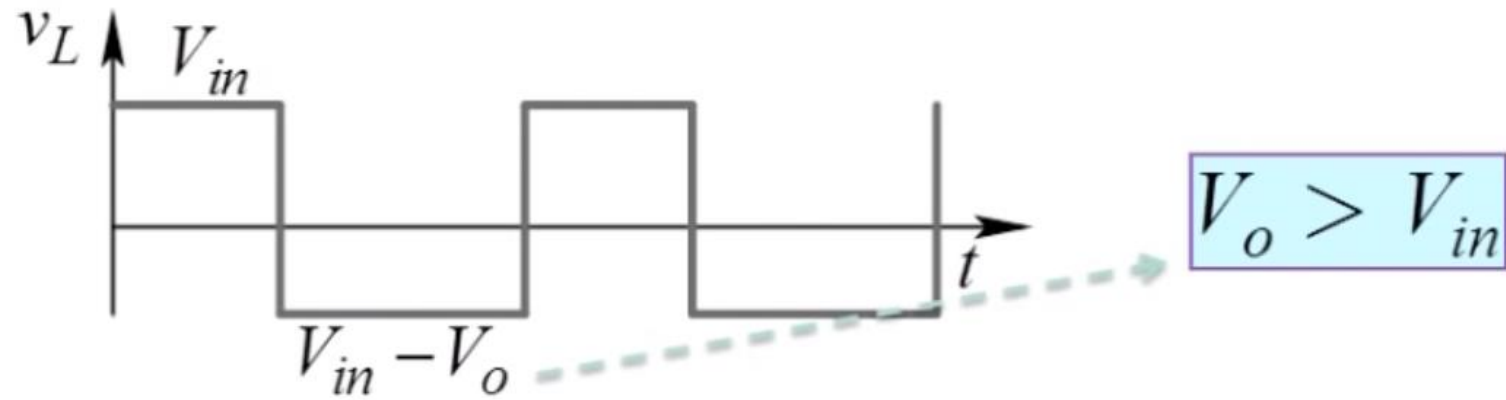

Buck-boost

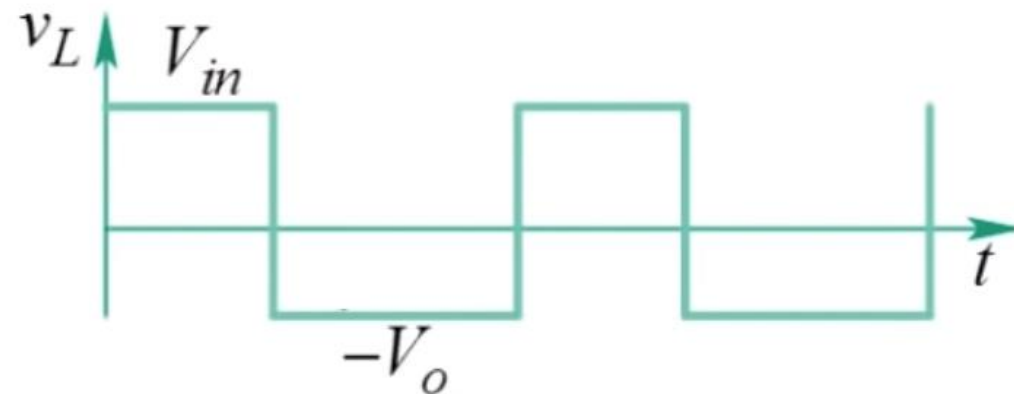

Step-up and  
Step-down